



Fundamentals of Logic Circuit Design

Part 2: Sequential Logic





HUMAN CAPITAL
HUMAN – BEST INVESTMENT!

EUROPEAN UNION
EUROPEAN
SOCIAL FUND





Project is co-financed by European Union within European Social Fund

X'mas tree lights

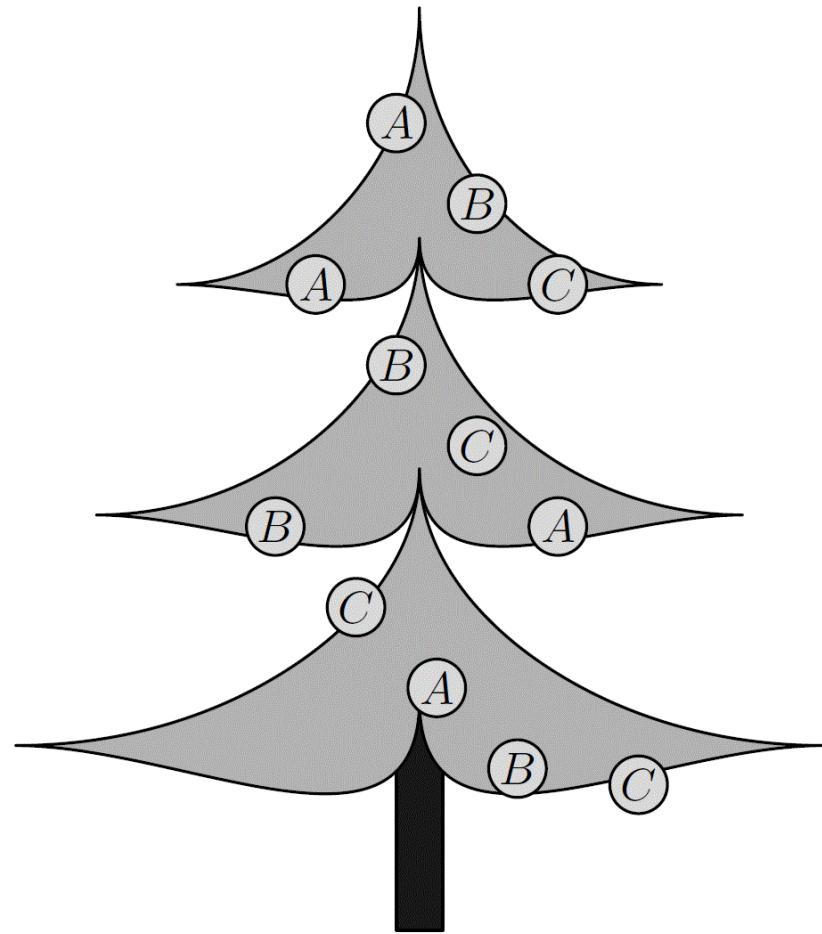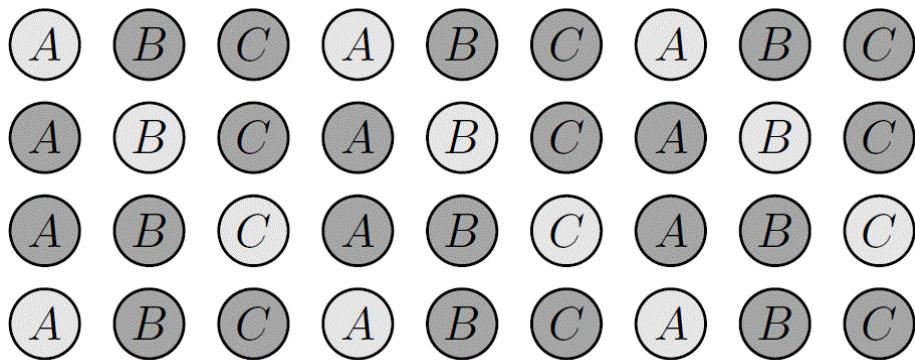

x_1	x_2	action
0	0	all off
0	1	$ABCABC\dots$
1	0	$CBACBA\dots$
1	1	not permitted

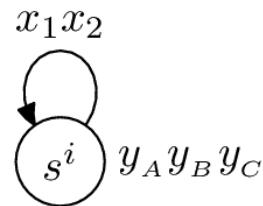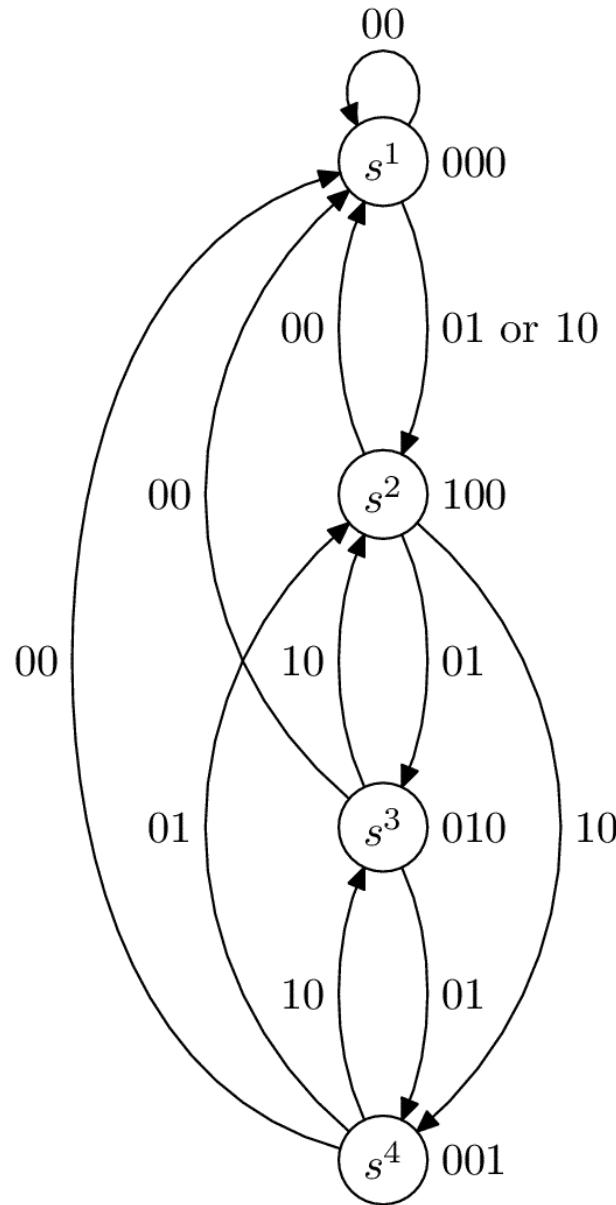

state	x_1x_2				$y_A y_B y_C$
	00	01	11	10	
s^1	s^1	s^2	—	s^2	000
s^2	s^1	s^3	—	s^4	100
s^3	s^1	s^4	—	s^2	010
s^4	s^1	s^2	—	s^3	001

$state' / y$

State transition and output table for the X'mas tree automaton

Coded state transition and output table for the X'mas tree automaton

<i>state</i>	q_1	q_2
s^1	0	0
s^2	0	1
s^3	1	0
s^4	1	1

State assignment: $state \rightarrow code$

x_1x_2	00	01	11	10	$y_Ay_By_C$
q_1q_2	00	01	—	01	000
	00	10	—	11	100
	00	11	—	01	010
	00	01	—	10	001

NB code

$q'_1 q'_2 / y$

x_1x_2	00	01	11	10	$y_Ay_By_C$
q_1q_2	00	01	—	01	000
	00	10	—	11	100
	00	01	—	10	001
	00	11	—	01	010

Gray's code

$q'_1 q'_2 / y$

		x_1x_2	00	01	11	10
		q_1q_2	00	01	—	01
q_1q_2	x_1x_2	00	00	01	—	01
01	00	00	10	—	11	
11	00	00	01	—	10	
10	00	00	11	—	01	

$q'_1 q'_2$

		x_1x_2	00	01	11	10	
		q_1q_2	00	0	0	—	0
q_1q_2	x_1x_2	00	0	0	—	0	
01	00	0	1	—	1		
11	00	0	0	—	1		
10	00	0	1	—	0		

q'_1

		x_1x_2	00	01	11	10	
		q_1q_2	00	0	1	—	1
q_1q_2	x_1x_2	00	0	1	—	1	
01	00	0	0	—	1		
11	00	0	1	—	0		
10	00	0	1	—	1		

q'_2

q_1	q_2	y_A	y_B	y_C
0	0	0	0	0
0	1	1	0	0
1	1	0	0	1
1	0	0	1	0

q_1	q_2	0	1
0	0	0	1
1	0	0	0

y_A

q_1	q_2	0	1
0	0	0	0
1	1	0	0



y_B

q_1	q_2	0	1
0	0	0	0
1	0	0	1


y_C

D-type flip-flop

Q	\rightarrow	Q'	$ D$
0	\rightarrow	0	0
0	\rightarrow	1	1
1	\rightarrow	0	0
1	\rightarrow	1	1

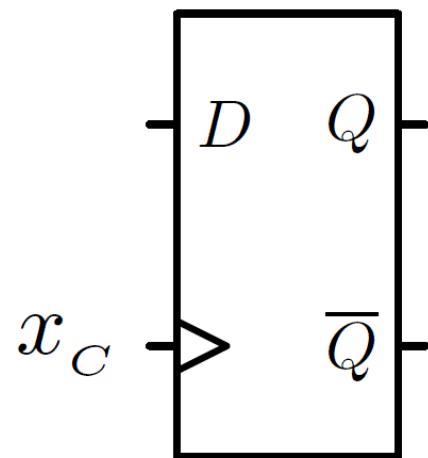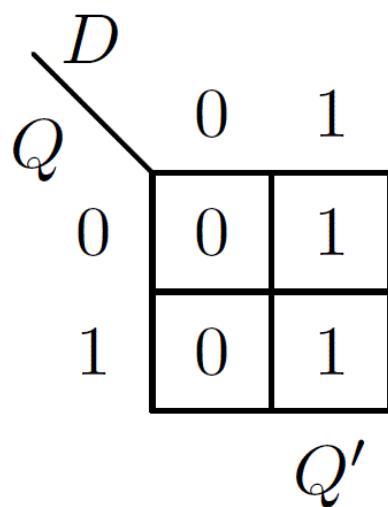

positive
edge
triggered

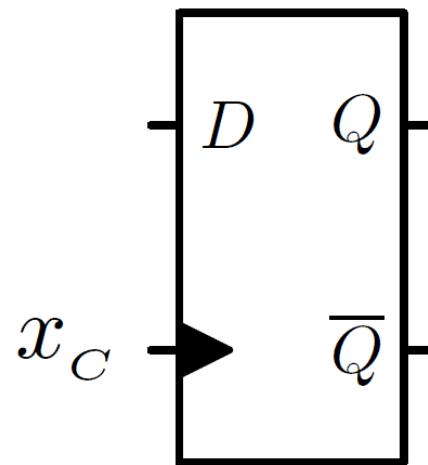

negative
edge
triggered

$x_1 x_2$	00	01	11	10
$q_1 q_2$	00	0	-	0
00	0	1	-	1
01	0	-	1	0
11	0	0	-	1
10	0	1	-	0

$$D_1 = q'_1$$

$x_1 x_2$	00	01	11	10
$q_1 q_2$	00	0	1	-
00	0	0	-	1
01	0	-	1	0
11	0	1	-	0
10	0	1	-	1

$$D_2 = q'_2$$

$$\left\{ \begin{array}{l} q'_1 = \bar{q}_1 q_2 x_2 + q_1 \bar{q}_2 x_2 + q_2 x_1 \\ q'_2 = \bar{q}_1 x_1 + q_1 x_2 + \bar{q}_2 x_2 + \bar{q}_2 x_1 \\ y_A = \bar{q}_1 q_2 \\ y_B = q_1 \bar{q}_2 \\ y_C = q_1 q_2 \end{array} \right.$$

q_2	0	1
q_1	0	0
0	0	1
1	0	0


 y_A

q_2	0	1
q_1	0	0
0	0	0
1	1	0

 y_B

q_2	0	1
q_1	0	0
0	0	0
1	0	1

 y_C

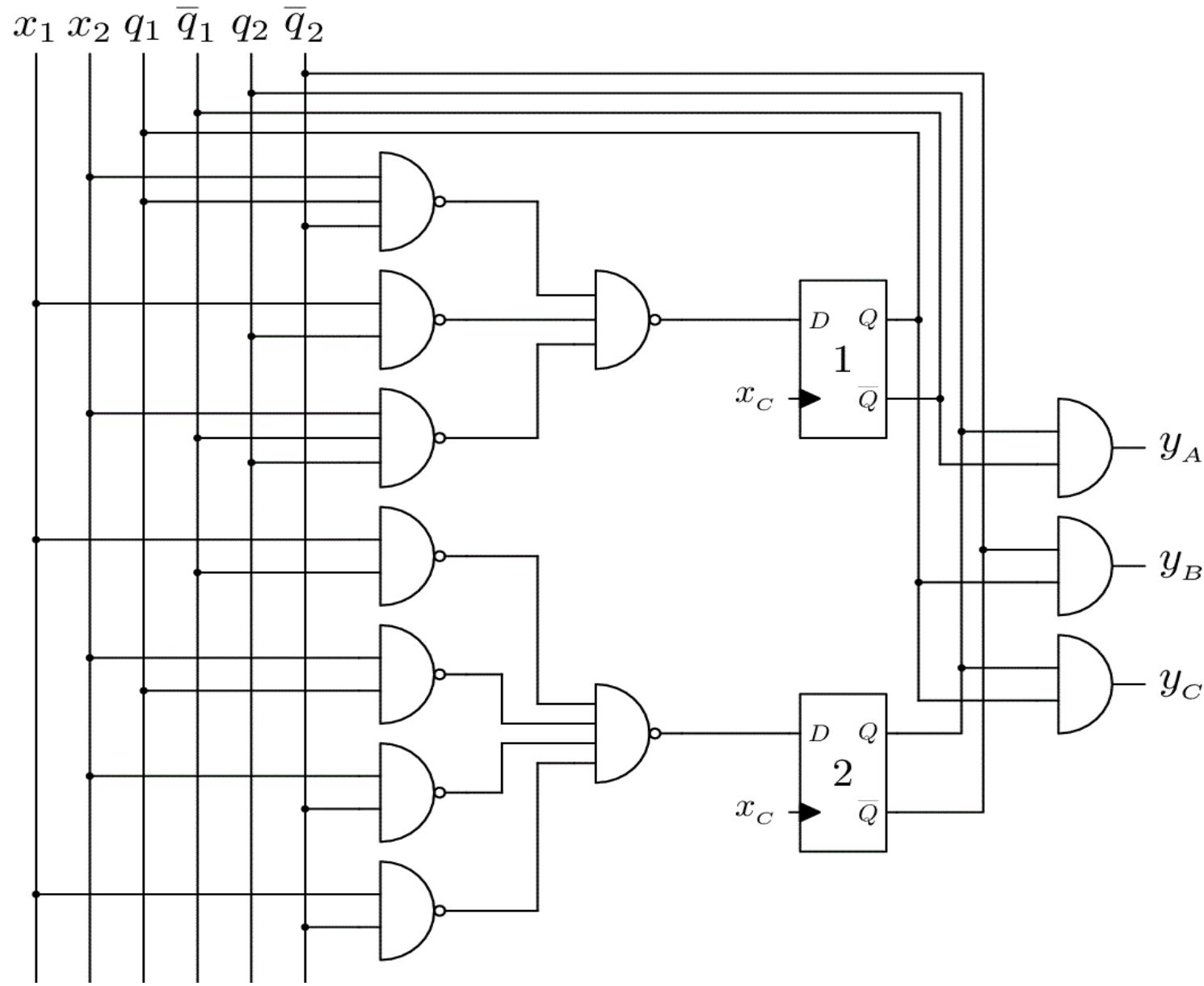

Version 2 of the X'mas tree automaton

$x_1 x_2$	00	01	11	10
$q_1 q_2$	0	0	-	0
00	0	1	-	1
01	0	-	1	1
11	0	0	-	1
10	0	1	-	0


$$D_1 = q'_1$$

$x_1 x_2$	00	01	11	10
$q_1 q_2$	0	1	-	1
00	0	0	-	1
01	0	-	1	1
11	0	1	-	0
10	0	1	-	1


$$D_2 = q'_2$$

$$\left\{ \begin{array}{l} q'_1 = \overline{q}_1 q_2 x_2 + q_2 x_1 + q_1 \overline{q}_2 x_2 \\ q'_2 = x_2 \overline{q}_1 q_2 x_2 + x_1 \overline{q}_1 q_2 \\ y_A = \overline{q}_1 q_2 \\ y_B = q_1 \overline{q}_2 \\ y_C = q_1 q_2 \end{array} \right.$$

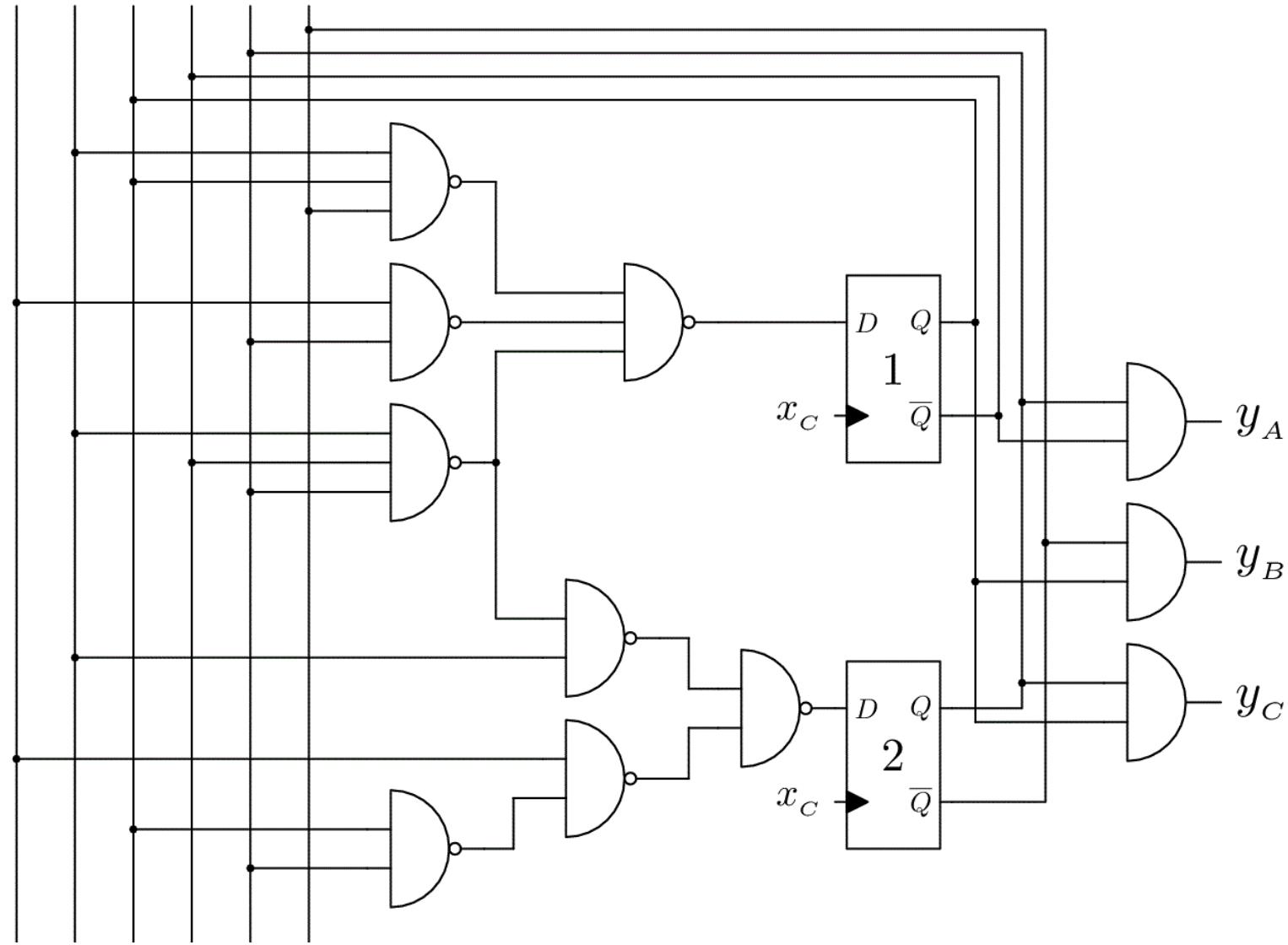$x_1 \ x_2 \ q_1 \ \bar{q}_1 \ q_2 \ \bar{q}_2$




Structure of synchronous Moore automaton

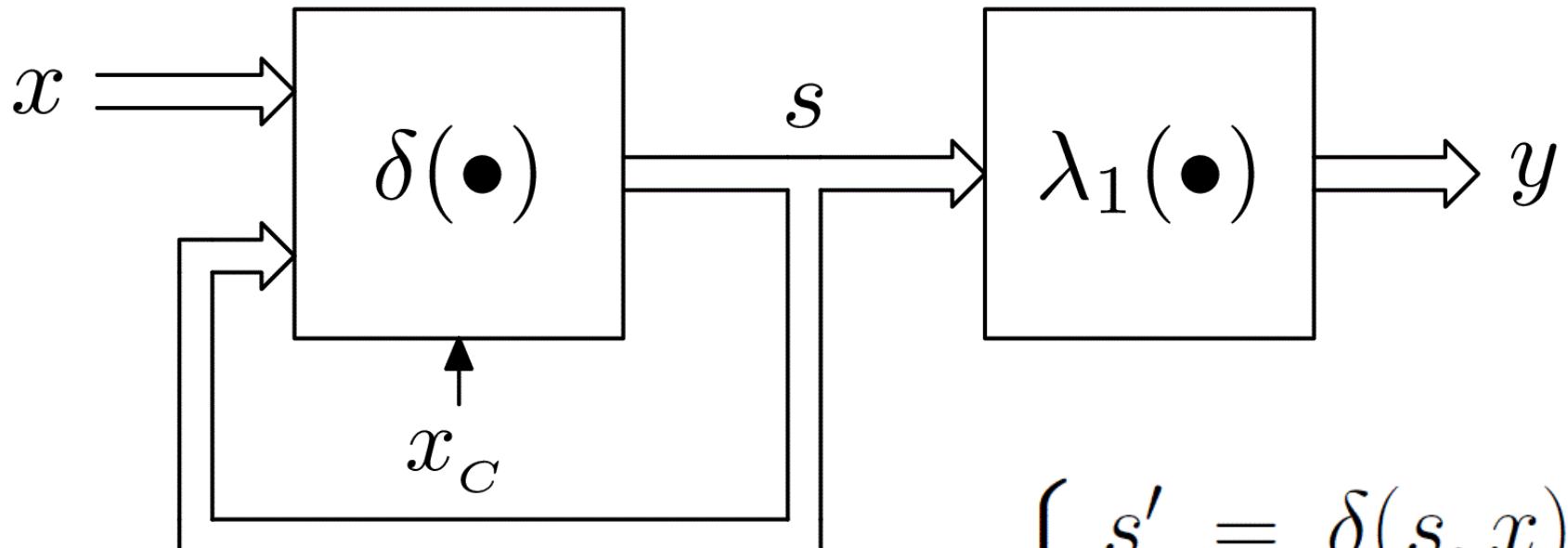

$$\begin{cases} s' = \delta(s, x) \\ y = \lambda_1(s) \end{cases}$$

Structure of synchronous Mealy automaton

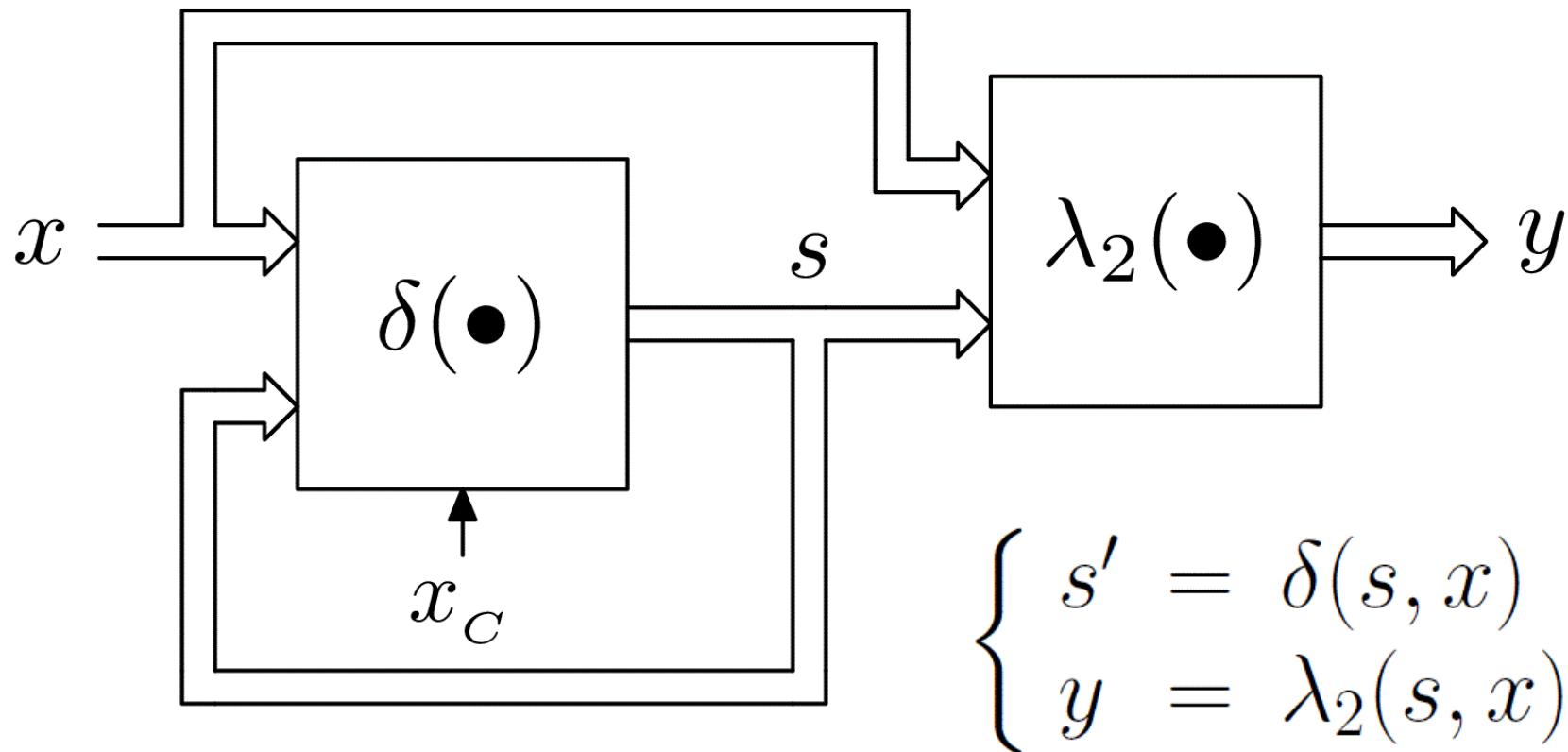

Basic definitions

input:	x	input set:	X	$x \in X$
output:	y	output set:	Y	$y \in Y$
state:	s	state set:	S	$s \in S$

Def: automaton

$$A = (S, X, Y, \delta, \lambda)$$

Def: completely specified automaton

If functions δ and λ for an automaton A are defined for each pair (s, x) from the set $S \times X$ the automaton is called complete (fully defined). Otherwise the automaton is considered incompletely specified (not fully defined).

Mathematical formulation for a Moore automaton:

Automaton $A = (S, X, Y, \delta, \lambda_1)$ is completely specified if

$$\forall (s, x) \in S \times X \quad \exists \delta(s, x) \quad \bigwedge \quad \exists \lambda_1(s)$$

otherwise it is incompletely specified.




Mathematical formulation for a Mealy automaton:

Automaton $A = (S, X, Y, \delta, \lambda_2)$ is completely specified if

$$\forall (s, x) \in S \times X \quad \exists \delta(s, x) \quad \bigwedge \quad \exists \lambda_2(s, x)$$

otherwise it is incompletely specified.

Equivalence of states of automata

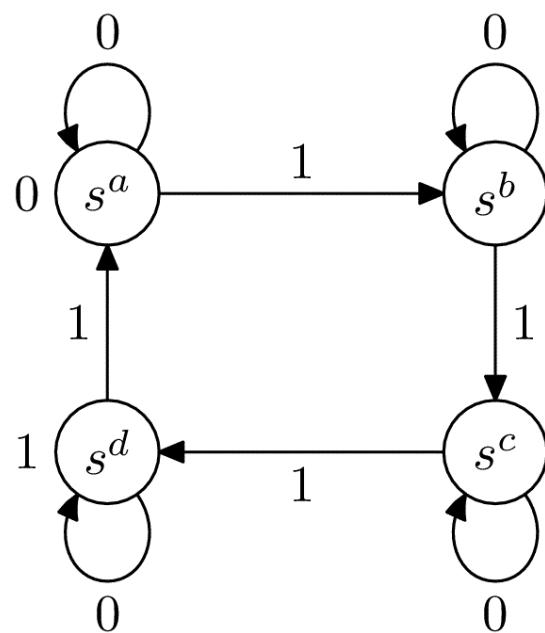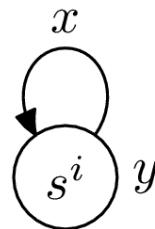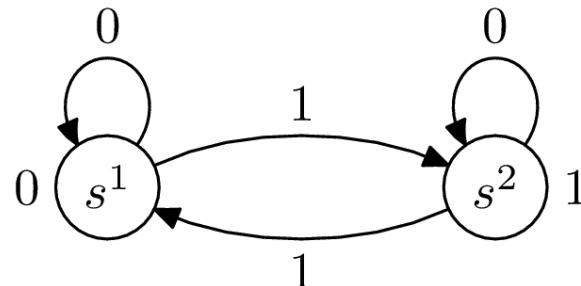
 $s^i/y \xrightarrow{x}$
 $s^1/0 \xrightarrow{0} s^1/0 \xrightarrow{1} s^2/1 \xrightarrow{0} s^2/1 \xrightarrow{1} s^1/0 \xrightarrow{1} s^2/1 \xrightarrow{1} s^1/0$
 $s^a/0 \xrightarrow{0} s^a/0 \xrightarrow{1} s^b/1 \xrightarrow{0} s^b/1 \xrightarrow{1} s^c/0 \xrightarrow{1} s^d/1 \xrightarrow{1} s^a/0$
 $\Rightarrow s^1 \equiv s^a$

Equivalence of states of automatons

Input sequence: $x^* = {}^1x {}^2x {}^3x \dots; {}^k x \in X$

Output sequence: $y^* = {}^1y {}^2y {}^3y \dots; {}^k y \in Y$

State sequence: $s^* = {}^1s {}^2s {}^3s \dots; {}^k s \in S$

Def.1: Two states s^i and s^j of a completely specified automaton are equivalent, if for any input sequence x^* applied to each of them the same output sequence y^* will result in both cases.

Mathematical formulation for a completely specified Moore automaton:

$$s^i \equiv s^j \iff \forall x^* \quad \lambda_1^*(\delta^*(s^i, x^*)) = \lambda_1^*(\delta^*(s^j, x^*))$$

where:

$$\delta^*(s, x^*) = s \ \delta(s, {}^1x) \ \delta(\delta(s, {}^1x), {}^2x) \dots = {}^1s \ {}^2s \dots$$

$$\lambda_1^*(s^*) = \lambda_1(s) \ \lambda_1({}^1s) \ \lambda_1({}^2s) \dots = {}^0y \ {}^1y \ {}^2y \dots$$

Mathematical formulation for a completely specified Mealy automaton:

$$s^i \equiv s^j \iff \forall x^* \quad \lambda_2^{**}(\delta^*(s^i, x^*), x^*) = \lambda_2^{**}(\delta^*(s^j, x^*), x^*)$$

where:

$$\delta^*(s, x^*) = s \quad \delta(s, {}^1x) \quad \delta(\delta(s, {}^1x), {}^2x) \dots = {}^1s \quad {}^2s \dots$$

$$\lambda_2^{**}(s^*, x^*) = \lambda_2^*(s, x^{*1}) \quad \lambda_2^*({}^1s, x^{*2}) \dots = y^{*0} \quad y^{*1} \dots$$

$$y^{*k} = {}^{k_1}y \dots {}^{k_m}y$$

$$\lambda_2^*({}^k s, x^{*k}) = \lambda_2({}^k s, {}^{k_1}x) \dots \lambda_2({}^k s, {}^{k_m}x) = {}^{k_1}y \dots {}^{k_m}y$$

$$x^* = x^{*1} \quad x^{*2} \quad x^{*3} \dots$$

$$x^{*k} = {}^{k_1}x \dots {}^{k_n}x$$

$${}^k x = {}^{k_n}x$$

Equivalence of states of automatons

Def.2: Two states s^i and s^j of completely specified automatons are equivalent, if for any input $x \in X$:

- outputs in both states are equal
- next states are the same or equivalent


Mathematical formulation for completely specified Moore automatons:

$$s^i \equiv s^j \iff \forall x \left(\lambda_1(s^i) = \lambda_1(s^j) \right) \wedge \\ \left((\delta(s^i, x) = \delta(s^j, x)) \vee (\delta(s^i, x) \equiv \delta(s^j, x)) \right)$$

Mathematical formulation for completely specified Mealy automatons:

$$s^i \equiv s^j \iff \forall x \left(\lambda_2(s^i, x) = \lambda_2(s^j, x) \right) \wedge \\ \left((\delta(s^i, x) = \delta(s^j, x)) \vee (\delta(s^i, x) \equiv \delta(s^j, x)) \right)$$

Initial graph and state transition table

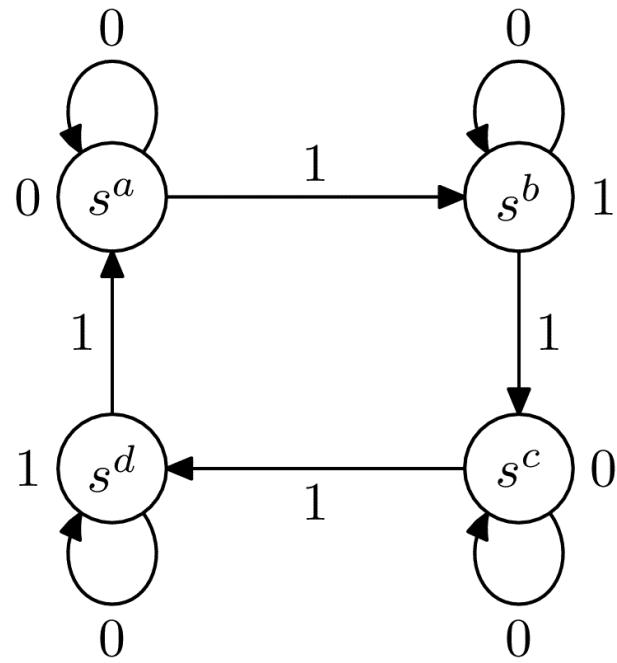

x	0	1	y
s	s^a	s^b	0
s^a	s^a	s^b	0
s^b	s^b	s^c	1
s^c	s^c	s^d	0
s^d	s^d	s^a	1
s' / y			

Implication matrix

s^b		
s^c	s^a, s^c s^b, s^d	\times
s^d	\times	s^b, s^d s^a, s^c
	s^a	s^b

conditions

⇒ looped conditions are fulfilled

$$y = \lambda_1(s^a) = \lambda_1(s^c) = 0$$


$$\begin{cases} \delta(s^a, 0) = s^a, & y = \lambda_1(s^a) = 0 \\ \delta(s^c, 0) = s^c, & y = \lambda_1(s^c) = 0 \end{cases}$$

$$\begin{cases} \delta(s^a, 1) = s^b, & y = \lambda_1(s^b) = 1 \\ \delta(s^c, 1) = s^d, & y = \lambda_1(s^d) = 1 \end{cases}$$


$$\begin{cases} \delta(s^b, 0) = s^b, & y = \lambda_1(s^b) = 1 \\ \delta(s^d, 0) = s^d, & y = \lambda_1(s^d) = 1 \end{cases}$$

$$\begin{cases} \delta(s^b, 1) = s^c, & y = \lambda_1(s^c) = 0 \\ \delta(s^d, 1) = s^a, & y = \lambda_1(s^a) = 0 \end{cases}$$

Equivalence graph

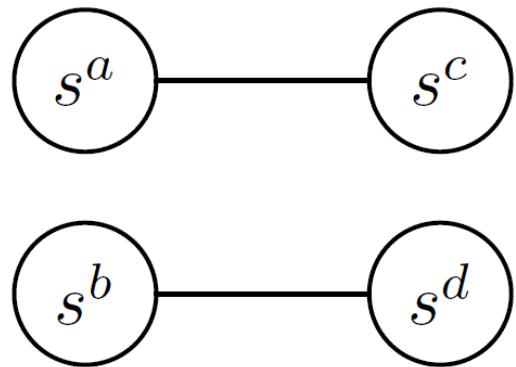

Graph of the
minimized automaton

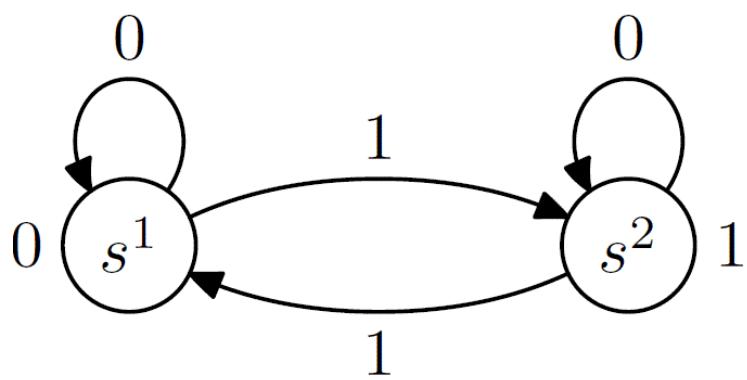

State equivalence

$$\{s^a, s^c\} \rightarrow s^1$$


$$\{s^b, s^d\} \rightarrow s^2$$

Its state
transition table

x	0	1	y
s	s^1	s^2	0
s^1	s^1	s^2	0
s^2	s^2	s^1	1

s'/y

Mealy automaton

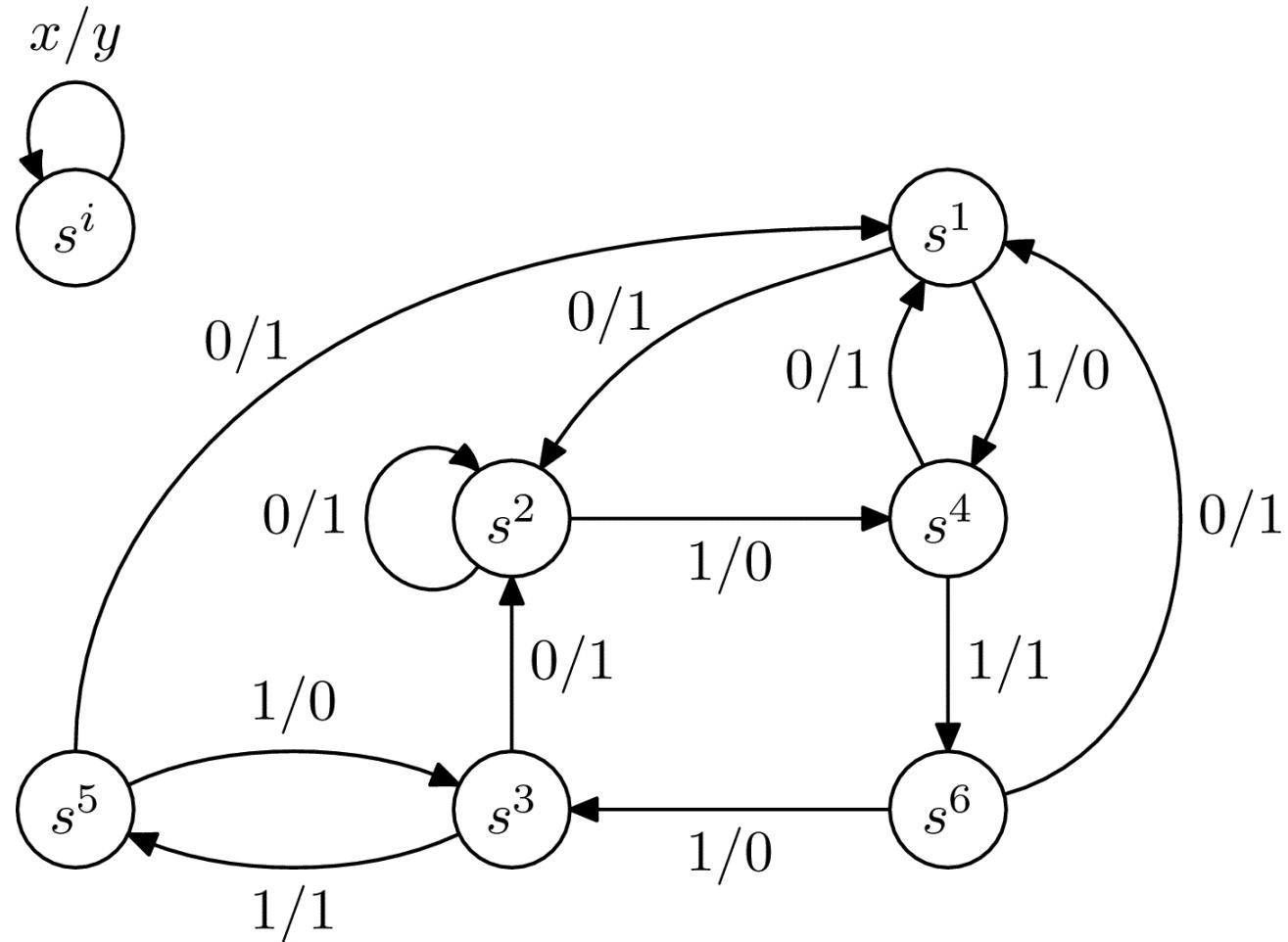

State transition and output table

x	0	1
s		
s^1	$s^2/1$	$s^4/0$
s^2	$s^2/1$	$s^4/0$
s^3	$s^2/1$	$s^5/1$
s^4	$s^1/1$	$s^6/1$
s^5	$s^1/1$	$s^3/0$
s^6	$s^1/1$	$s^3/0$
s'/y		


s^2	
s^3	
s^4	
s^2	
s^3	
s^4	
s^5	
s^6	
s^2	
s^3	
s^4	
s^5	
s^6	

Implication matrix:

	s^1	s^2	s^3	s^4	s^5
s^2	X	X			
s^3	X	X			
s^4	X	X			s^1, s^2 s^5, s^6
s^5	s^1, s^2 s^3, s^4	s^1, s^2 s^3, s^4	X	X	
s^6	s^1, s^2 s^3, s^4	s^1, s^2 s^3, s^4	X	X	

Equivalence graph


State equivalence

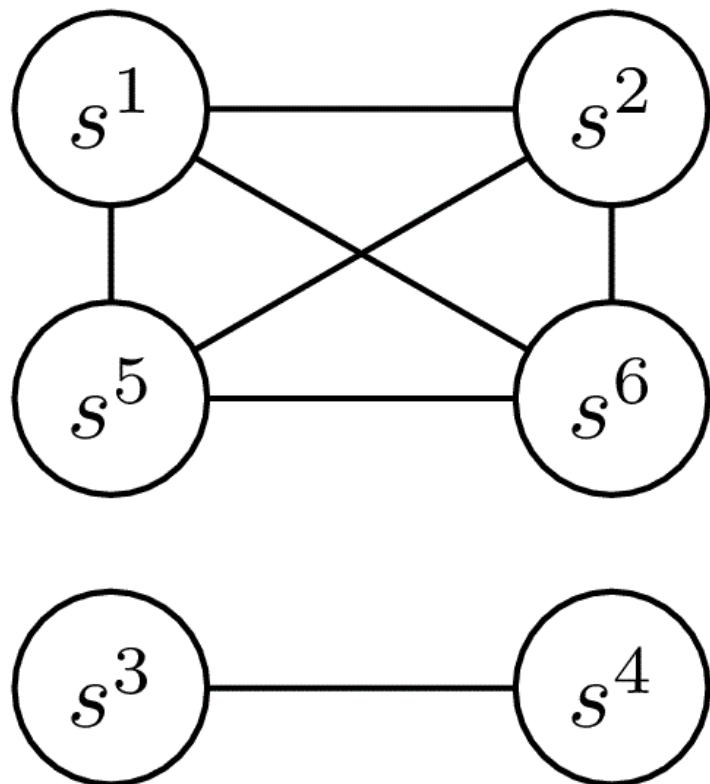

$$\{s^1, s^2, s^5, s^6\} \rightarrow s^a$$

$$\{s^3, s^4\} \rightarrow s^b$$


Graph of minimized automation

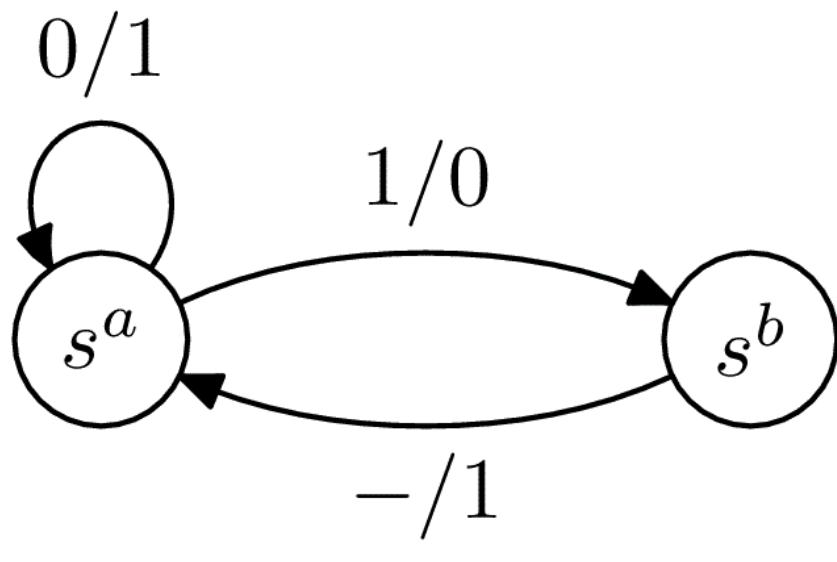


Its state
transition table

x	0	1
s	$s^a/1$	$s^b/0$
s^a	$s^a/1$	$s^a/1$
s^b	s'/y	


Moore automaton

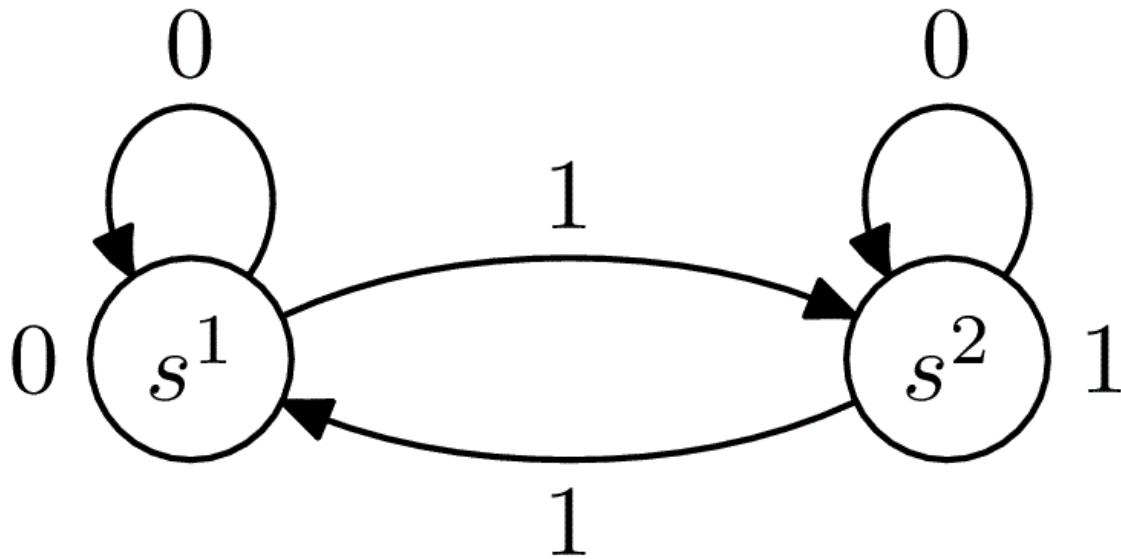




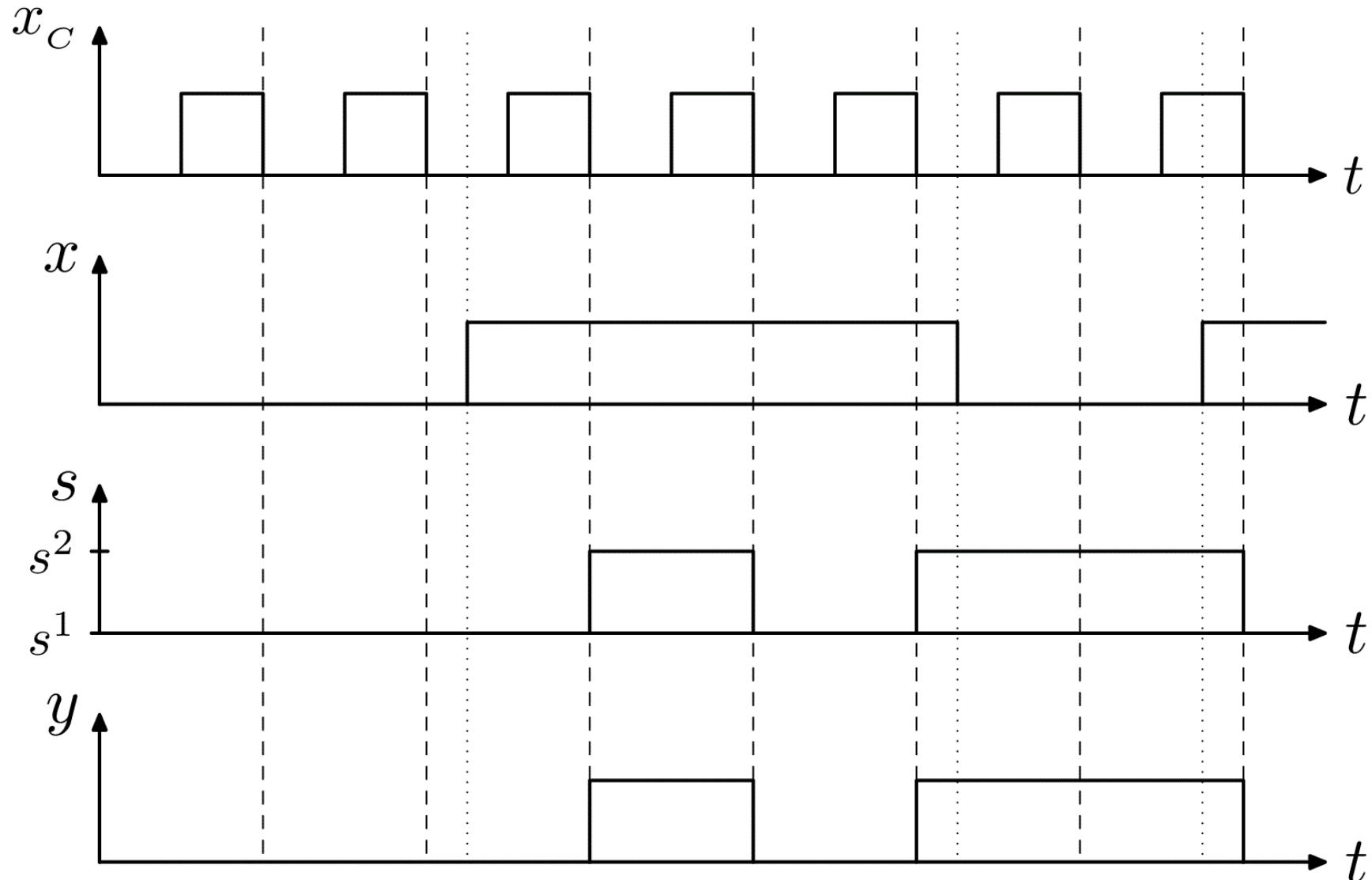
outputs change synchronously with the state changes
(on the active edge of the clock signal)



Mealy automaton

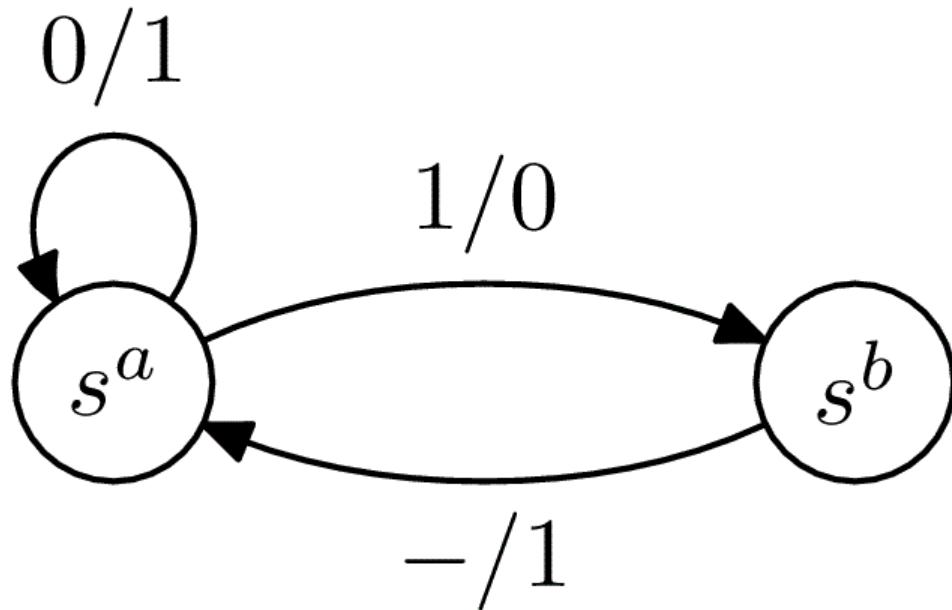

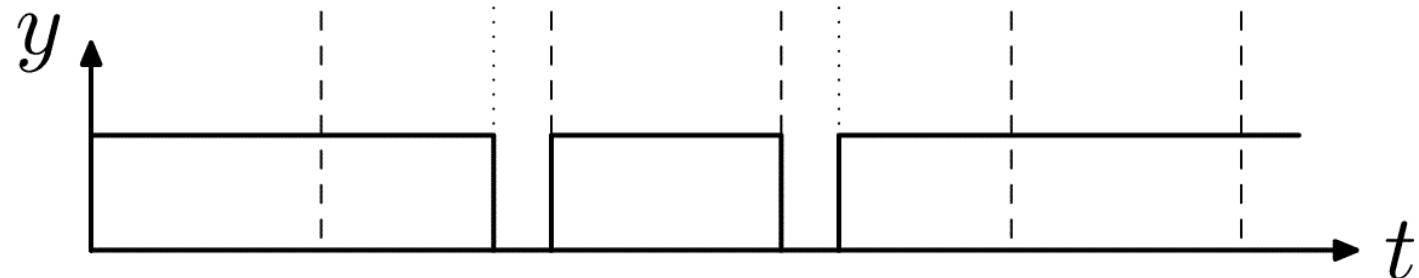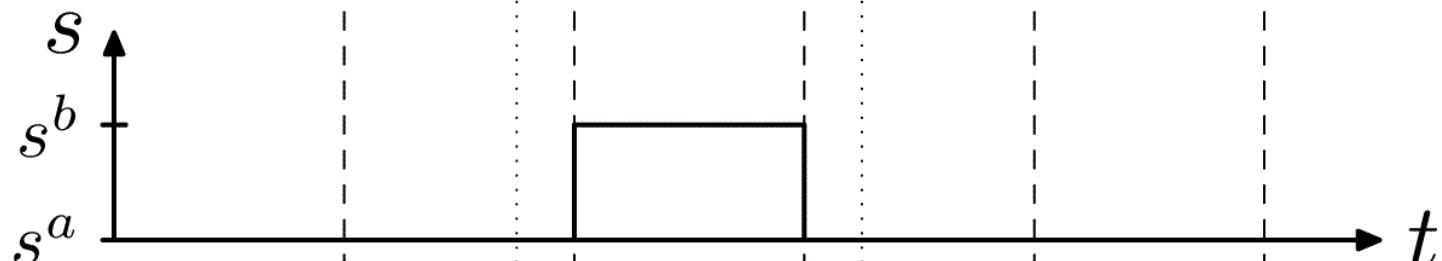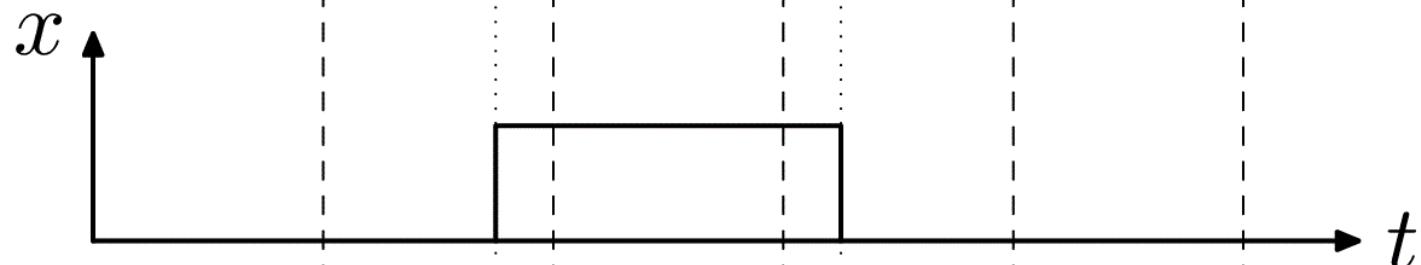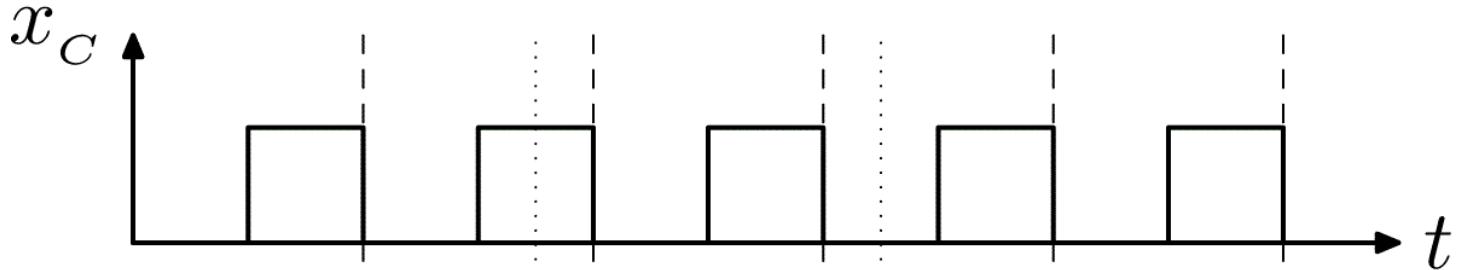outputs do not change synchronously with the state changes,
but change between active edges of the clock signal



Compatibility of states of automatons

An input x is applicable in state s if there exists $\delta(s, x)$ and $\lambda_1(s)$ (Moore) or $\lambda_2(s, x)$ (Mealy).

⇒ no “–” in state transition & output table element (s, x)

Input sequence x^{a^*} is said to be applicable if each of the inputs in the sequence is applicable in its respective state.

Def.3 Two states s^i and s^j of an incompletely specified automaton are compatible, if for any applicable input sequence x^{a^*} applied to each of them the same output sequence y^* will result in both cases.

Mathematical formulation for an incompletely specified Moore automaton:

$$s^i \cong s^j \iff \forall x^{a*} \quad \lambda_1^*(\delta^*(s^i, x^{a*})) = \lambda_1^*(\delta^*(s^j, x^{a*}))$$

where:

$$\begin{aligned} \delta^*(s, x^{a*}) &= s \ \delta(s, {}^1x) \ \delta(\delta(s, {}^1x), {}^2x) \dots = {}^1s \ {}^2s \dots \\ \lambda_1^*(s^*) &= \lambda_1(s) \ \lambda_1({}^1s) \ \lambda_1({}^2s) \dots = {}^0y \ {}^1y \ {}^2y \dots \\ x^{a*} &= {}^1x \ {}^2x \ {}^3x \dots \end{aligned}$$

Mathematical formulation for an incompletely specified Mealy automaton:

$$s^i \cong s^j \iff \forall x^{a*} \quad \lambda_2^{**}(\delta^*(s^i, x^{a*}), x^{a*}) = \lambda_2^{**}(\delta^*(s^j, x^{a*}), x^{a*})$$

where:

$$\delta^*(s, x^{a*}) = s \quad \delta(s, {}^1x) \quad \delta(\delta(s, {}^1x), {}^2x) \dots = {}^1s \quad {}^2s \dots$$

$$\lambda_2^{**}(s^*, x^{a*}) = \lambda_2^*(s, x^{a*1}) \quad \lambda_2^*({}^1s, x^{a*2}) \dots = y^{*0} \quad y^{*1} \dots$$

$$y^{a*k} = {}^{k_1}y \dots {}^{k_m}y$$

$$\lambda_2^*(s^k, x^{a*k}) = \lambda_2({}^k s, {}^{k_1}x) \dots \lambda_2({}^k s, {}^{k_m}x) = {}^{k_1}y \dots {}^{k_m}y$$

$$x^{a*} = x^{a*1} \quad x^{a*2} \quad x^{a*3} \dots$$

$$x^{a*k} = {}^{k_1}x \dots {}^{k_n}x$$

$${}^k x$$

Outputs $y^i = y_1^i \dots y_r^i$ and $y^j = y_1^j \dots y_r^j$ are non-contradictory (denoted as: $y^i \simeq y^j$), if for each pair $y_d^i, y_d^j, d = 1, \dots, r$, $y_d^i = y_d^j$ or $y_d^i = -$ or $y_d^j = -$

Non-contradictory: $0 = 0, 1 = 1, 0 = -, 1 = -$

Next states produced by input x from states s^i and s^j are non-contradictory (denoted as: $\delta(s^i, x) \simeq \delta(s^j, x)$), if $\delta(s^i, x) = \delta(s^j, x)$ or $\delta(s^i, x) = -$ or $\delta(s^j, x) = -$

Def.4 Two states s^i and s^j of incompletely specified automatons are compatible (denoted as: $s^i \approx s^j$), if for any applicable input $x \in X$:

- outputs in both states are non-contradictory
- next states are non-contradictory or compatible

Mathematical formulation for incompletely specified Moore automatons:

$$s^i \approx s^j \iff \forall x \left(\lambda_1(s^i) \simeq \lambda_1(s^j) \right) \wedge \\ \left((\delta(s^i, x) \simeq \delta(s^j, x)) \vee (\delta(s^i, x) \cong \delta(s^j, x)) \right)$$

Mathematical formulation for incompletely specified Mealy automatons:

$$s^i \approx s^j \iff \forall x \left(\lambda_2(s^i, x) \simeq \lambda_2(s^j, x) \right) \wedge \\ \left((\delta(s^i, x) \simeq \delta(s^j, x)) \vee (\delta(s^i, x) \cong \delta(s^j, x)) \right)$$


State transition and output table of an incompletely specified Mealy automaton

Implication matrix

$x_1 x_2$	00	01	11	10
s	$s^2/1$	$s^6/1$	$s^4/0$	—
s^1	—	—	—	$s^5/1$
s^2	$s^2/1$	$s^3/1$	—	$s^3/1$
s^3	$s^5/1$	$s^3/0$	$s^1/1$	—
s^4	—	—	$s^2/0$	—
s^5	$s^3/1$	—	$s^2/1$	$s^6/1$
s^6	—	—	—	—
		s'/y		

s^2				
s^3	s^3, s^6	s^3, s^5		
s^4	X		X	
s^5	s^2, s^4			X
s^6	X	s^5, s^6	s^2, s^3	s^3, s^5 s^1, s^2
	s^1	s^2	s^3	s^4
				s^5

Compatibility graph

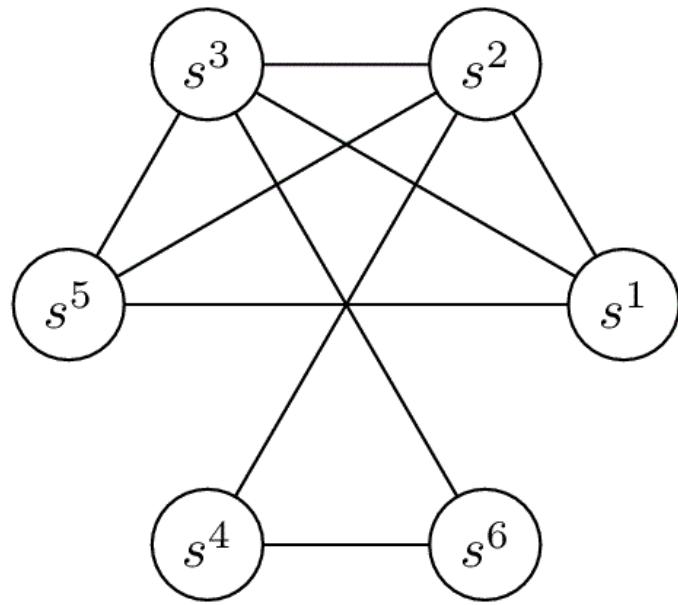

Implication matrix


s^2					
s^3	s^3, s^6	s^3, s^5			
s^4			\times		
s^5	s^2, s^4			\times	
s^6	\times	\times	\times	\times	
	s^1	s^2	s^3	s^4	s^5

$$\{s^1, s^2, s^3, s^5\} \rightarrow s^a$$

State substitution

$$\{s^4, s^6\} \rightarrow s^b$$


Problem with state substitution

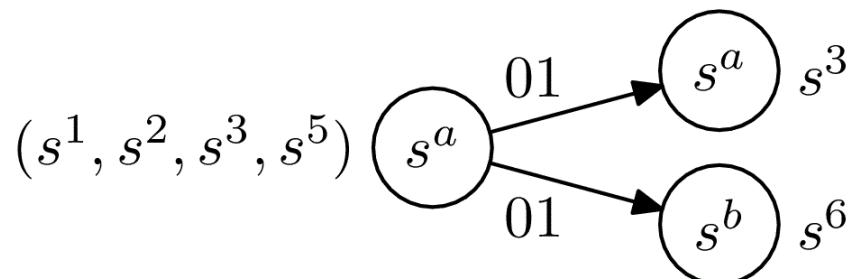

x_1x_2

	00	01	11	10
s	$s^a/1$?/1		
s^a	$s^a/1$	$s^a/0$	$s^a/1$	$s^b/1$
s^b	$s^a/1$	$s^a/0$	$s^a/1$	$s^b/1$

s'/y

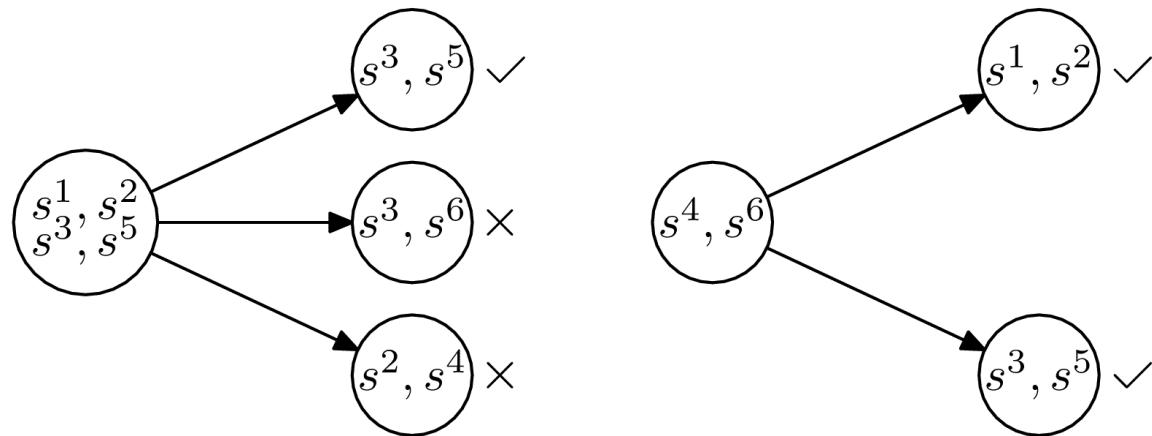

Conclusion

States of the minimized incompletely specified automaton must fulfill the following conditions:

- include all the states of the initial automaton (cover condition)
- for all the states of the initial automaton forming a single state of a minimized automaton and for each input all the next states of the initial automaton must be covered by a single state of the minimized automaton (closure condition)

States of the minimized completely specified automaton must fulfill the following condition:

- include all the states of the initial automaton
(cover condition)

Minimisation of the number of states of a completely specified automaton – mathematical formulation

${}_{A_1}S$ – set of states of the initial automaton A_1

${}_{A_1}S^k$ – k th set of equivalent states of automaton A_1 ,

$${}_{A_1}S^k \subset {}_{A_1}S$$

${}_{A_1}S^{k'}$ – k' th set of equivalent states of automaton A_1 ,

$${}_{A_1}S^{k'} \subset {}_{A_1}S$$

${}_{A_2}S$ – set of states of minimal automaton A_2

$2^{A_1}S$ – set (family) of all the subsets of states of automaton A_1

${}_{A_1}\hat{S}$ – family of subsets of states of automaton A_1 ,

$${}_{A_1}\hat{S} \subset 2^{A_1}S$$

n – minimal number of equivalent state subsets of automaton A_1 .

Moreover $k, k' \in \{1, \dots, n\}$.

We are looking for a minimal family ${}_{A_1}\hat{S}$ of subsets of the set of states of automaton A_1 , i.e.:

$$n = \min_{\text{card}({}_{A_1}\hat{S})} \left({}_{A_1}\hat{S} \subset 2^{A_1} S \right)$$

of which the sets ${}_{A_1}S^k, {}_{A_1}S^{k'} \in {}_{A_1}\hat{S}$ fulfil the conditions:

$$\left({}_{A_1}S^k \subset {}_{A_1}S \right) : \left(\forall \left({}_{A_1}s^{k_i}, {}_{A_1}s^{k_j} \in {}_{A_1}S^k \right) \left({}_{A_1}s^{k_i} \equiv {}_{A_1}s^{k_j} \right) \right)$$

$$(k \neq k') \Rightarrow \left({}_{A_1}S^k \cap {}_{A_1}S^{k'} = \emptyset \right)$$

$$\left(\bigcup_{k=1}^n {}_{A_1}S^k \right) = {}_{A_1}S$$

Then with each of those subsets a state of the minimal automaton A_2 can be associated in the following manner:

$${}_{A_1}S^k \rightarrow {}_{A_2}s^k, \quad {}_{A_2}s^k \in {}_{A_2}S$$

In short, we are looking for a least numerous family of subsets of the set of states of automaton A_1 . The elements of this family must fulfil the following conditions:

1. This are the sets of equivalent states.
2. None of the states of the initial automaton belongs to two different sets.
3. Those sets fulfil the cover condition.

Minimisation of the number of states of an incompletely specified automaton – mathematical formulation

${}_{A_1}S$ – set of states of the initial automaton A_1

${}_{A_1}S^k$ – k th set of compatible states of automaton A_1 ,

$${}_{A_1}S^k \subset {}_{A_1}S$$

${}_{A_1}S^{k'}$ – k' th set of compatible states of automaton A_1 ,

$${}_{A_1}S^{k'} \subset {}_{A_1}S$$

${}_{A_2}S$ – set of states of the minimal automaton A_2

$2^{A_1}S$ – set (family) of all the subsets of states of automaton A_1

${}_{A_1}\hat{S}$ – family of subsets of states of automaton A_1 ,

$${}_{A_1}\hat{S} \subset 2^{A_1}S$$

n – minimal number of compatible state subsets of automaton A_1 .

Moreover $k, k' \in \{1, \dots, n\}$.

We are looking for a minimal family ${}_{A_1}\hat{S}$ of subsets of the set of states of automaton A_1 , i.e.:

$$n = \min_{\text{card}({}_{A_1}\hat{S})} \left({}_{A_1}\hat{S} \subset 2^{A_1} S \right)$$

of which the sets ${}_{A_1}S^k, {}_{A_1}S^{k'} \in {}_{A_1}\hat{S}$ fulfil the following conditions:

$$({}_{A_1}S^k \subset {}_{A_1}S) : \left(\forall \left({}_{A_1}s^{k_i}, {}_{A_1}s^{k_j} \in {}_{A_1}S^k \right) \left({}_{A_1}s^{k_i} \approx {}_{A_1}s^{k_j} \right) \right)$$

$$(k \neq k') \Rightarrow \left({}_{A_1}S^k \cap {}_{A_1}S^{k'} = \emptyset \right)$$

$$\left(\bigcup_{k=1}^n {}_{A_1}S^k \right) = {}_{A_1}S$$

$$\left(\forall \left({}_{A_1}s^{k_i}, {}_{A_1}s^{k_j}, x \right) : \left({}_{A_1}s^{k_i}, {}_{A_1}s^{k_j} \in {}_{A_1}S^k \right) \right)$$

$$\Rightarrow \left(\exists {}_{A_1}S^{k'} : \left(\delta({}_{A_1}s^{k_i}, x), \delta({}_{A_1}s^{k_j}, x) \in {}_{A_1}S^{k'} \right) \right)$$

Then with each of those subsets a state of the minimal automaton A_2 can be associated in the following manner:

$${}_{A_1}S^k \rightarrow {}_{A_2}s^k, \quad {}_{A_2}s^k \in {}_{A_2}S$$

In short, we are looking for a least numerous family of subsets of the set of states of automaton A_1 . The elements of this family must fulfil the following conditions:

1. These are the sets of equivalent states.
2. None of the states of the initial automaton belongs to two different sets.
3. Those sets must fulfil the cover condition.
4. Those sets must fulfil the closure condition.

$x_1 x_2 \backslash s$	00	01	11	10
s	$s^2/1$	$s^6/1$	$s^4/0$	—
s^1	—	—	—	$s^5/1$
s^2	$s^2/1$	$s^3/1$	—	$s^3/1$
s^3	$s^5/1$	$s^3/0$	$s^1/1$	—
s^4	—	—	$s^2/0$	—
s^5	$s^3/1$	—	$s^2/1$	$s^6/1$

s'/y

$$\{s^1, s^2\} \rightarrow s^\alpha$$

$$\{s^3, s^5\} \rightarrow s^\beta$$

$$\{s^4, s^6\} \rightarrow s^\gamma$$

$x_1 x_2 \backslash s$	00	01	11	10
s	$s^\alpha/1$	$s^\gamma/1$	$s^\gamma/0$	$s^\beta/1$
s^α	$s^\alpha/1$	$s^\beta/1$	$s^\alpha/0$	$s^\beta/1$
s^β	$s^\beta/1$	$s^\beta/0$	$s^\alpha/1$	$s^\gamma/1$
s^γ	—	—	—	—

s'/y

$$\frac{s}{s^\alpha} \rightarrow q_1 \quad q_2$$

$$0 \quad 0$$

$$0 \quad 1$$

$$1 \quad 1$$

x_1x_2	00	01	11	10
q_1q_2	00/1	11/1	11/0	01/1
00	00/1	01/1	00/0	01/1
01	00/1	01/1	00/0	01/1
11	01/1	01/0	00/1	11/1
10	—	—	—	—

$q'_1 q'_2 / y$

x_1x_2	00	01	11	10
q_1q_2	0	1	1	0
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	—	—	—	—

q'_1

x_1x_2	00	01	11	10
q_1q_2	1	1	0	1
00	1	1	0	1
01	1	1	0	1
11	1	0	1	1
10	—	—	—	—

y

x_1x_2	00	01	11	10
q_1q_2	0	1	1	1
00	0	1	1	1
01	0	1	0	1
11	1	1	0	1
10	—	—	—	—

q'_2

D type flip-flop realisation

$x_1 x_2$	00	01	11	10	
$q_1 q_2$	00	0	1	1	0
	01	0	0	0	0
	11	0	0	0	1
	10	—	—	—	—

$$D_1 = q'_1$$


$x_1 x_2$	00	01	11	10	
$q_1 q_2$	00	0	1	1	1
	01	0	1	0	1
	11	1	1	0	1
	10	—	—	—	—

$$D_2 = q'_2$$

$x_1 x_2$	00	01	11	10	
$q_1 q_2$	00	1	1	0	1
	01	1	1	0	1
	11	1	0	1	1
	10	—	—	—	—

$$y$$
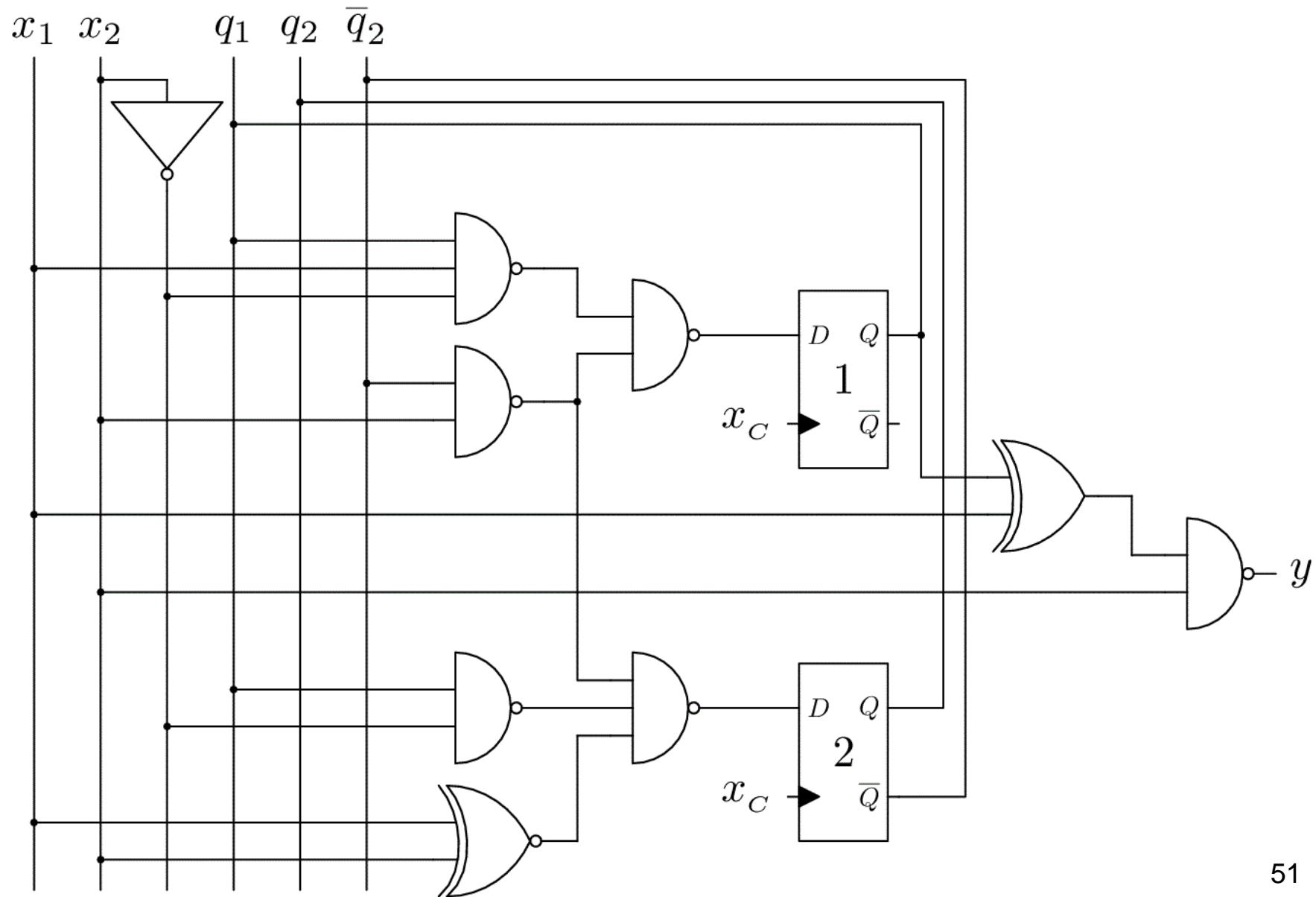
$$\left\{ \begin{array}{l} D_1 = q_1 x_1 \bar{x}_2 + \bar{q}_2 x_2 \\ D_2 = \bar{x}_1 x_2 + x_1 \bar{x}_2 + q_1 \bar{x}_2 + \bar{q}_2 x_2 = x_1 \oplus x_2 + q_1 \bar{x}_2 + \bar{q}_2 x_2 \\ y = \bar{x}_2 + \bar{q}_1 \bar{x}_1 + q_1 x_1 = \bar{x}_2 + \overline{q_1 \oplus x_1} \\ = \overline{x_2(q_1 \oplus x_1)} \end{array} \right.$$




JK-type flip-flop


Q	JK	00	01	11	10
0	0	0	1	1	1
1	1	0	0	1	0
		Q'			

Q	JK	00	01	11	10
0	0	0	1	1	1
1	1	0	0	1	0
		Q'			

Q	\rightarrow	Q'	J	K
0	\rightarrow	0	0	-
0	\rightarrow	1	1	-
1	\rightarrow	0	-	1
1	\rightarrow	1	-	0

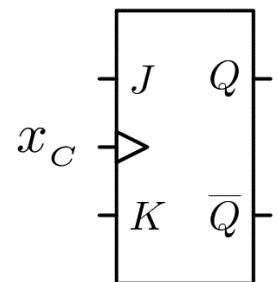

positive
edge
triggered

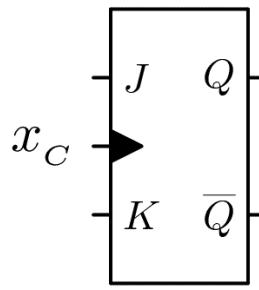

negative
edge
triggered

Coded state transition tables for the JK-type flip-flop

		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	0	1	1	0
00	00	0	0	0	0	0
01	01	0	0	0	0	0
11	11	0	0	0	1	0
10	10	—	—	—	—	—

		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	0	1	1	1
00	00	0	1	0	1	1
01	01	0	1	0	1	1
11	11	1	1	0	1	1
10	10	—	—	—	—	—

q'_1

q'_2

		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	—	—	—	—
00	00	—	—	—	—	—
01	01	—	—	—	—	—
11	11	1	1	1	0	—
10	10	—	—	—	—	—

		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	—	—	—	—
00	00	—	—	—	—	—
01	01	1	0	1	0	—
11	11	0	0	1	0	—
10	10	—	—	—	—	—

K_1

K_2


		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	0	1	1	0
00	00	0	0	0	0	0
01	01	—	—	—	—	—
11	11	—	—	—	—	—
10	10	—	—	—	—	—

		$x_1 x_2$	00	01	11	10
		$q_1 q_2$	00	01	11	10
$q_1 q_2$	$x_1 x_2$	00	0	1	1	1
00	00	0	—	—	—	—
01	01	—	—	—	—	—
11	11	—	—	—	—	—
10	10	—	—	—	—	—

J_1


J_2
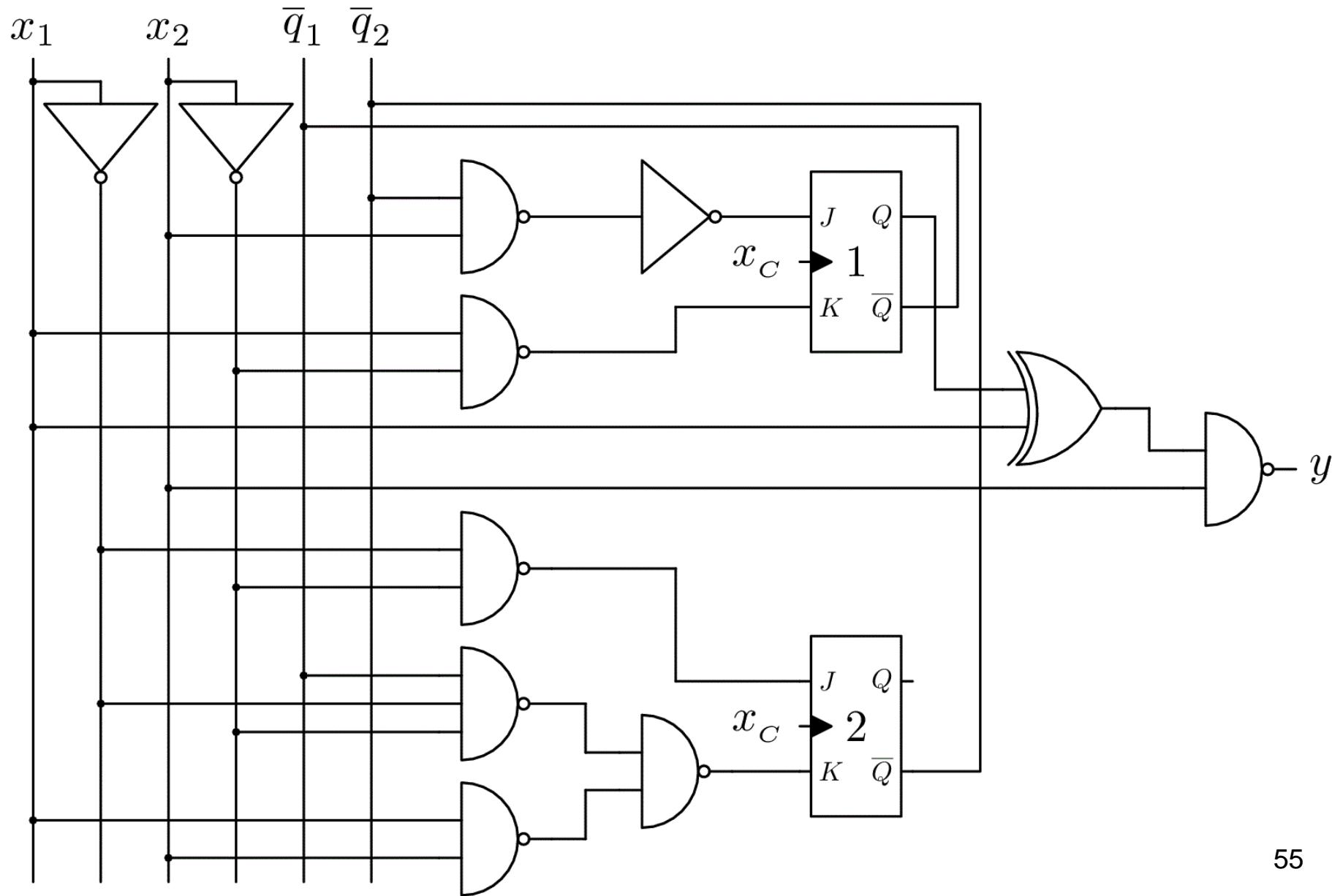
$$\begin{cases} J_1 = \bar{q}_2 x_2 \\ K_1 = \bar{x}_1 + x_2 = \overline{x_1 \bar{x}_2} \\ J_2 = x_1 + x_2 = \overline{\bar{x}_1 \bar{x}_2} \\ K_2 = x_1 x_2 + \bar{q}_1 \bar{x}_1 x_2 \end{cases}$$



Transformation of a Moore automaton into a partially equivalent Mealy automaton

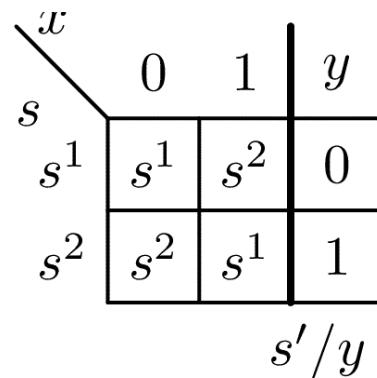Moore automaton state
transition and output table



A diagram illustrating the transformation of a Moore automaton state transition and output table into a Mealy automaton state transition and output table. On the left, a Moore automaton table is shown with states s^1 and s^2 , inputs 0 and 1, and outputs 0 and 1. An arrow points to the right, leading to a Mealy automaton table. The Mealy automaton table has the same structure but includes the current state s as part of the input vector (s, x) and shows the output y as part of the next state s'/y . The Mealy automaton table also includes transitions labeled with the next state s' .


		0	1	y
x	s	s^1	s^2	
s	s^1	s^1	s^2	0
	s^2	s^2	s^1	1

s'/y



Mealy automaton state
transition and output table

		0	1	
x	s	0	1	
s	s^1	$s^1/0$	$s^2/1$	
	s^2	$s^2/1$	$s^1/0$	

s'/y

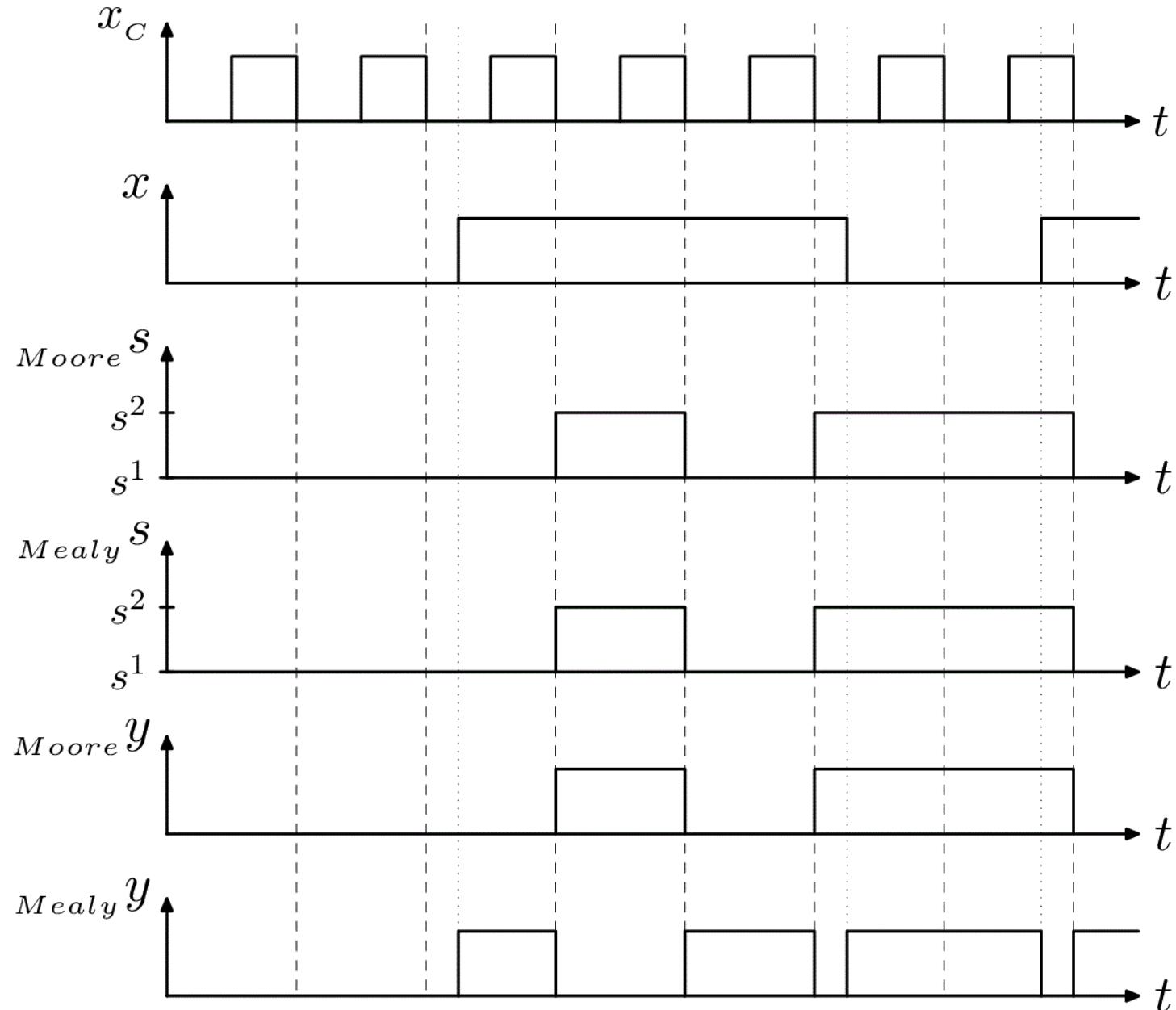

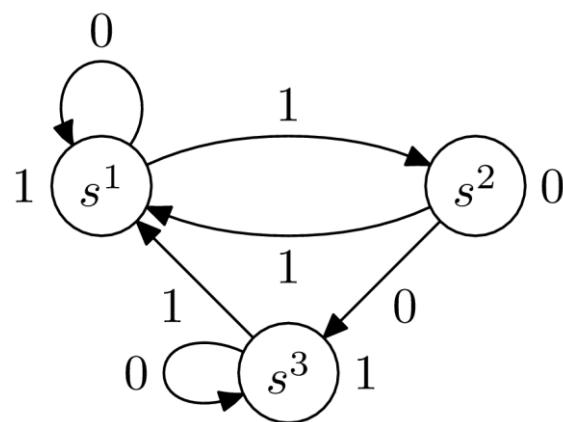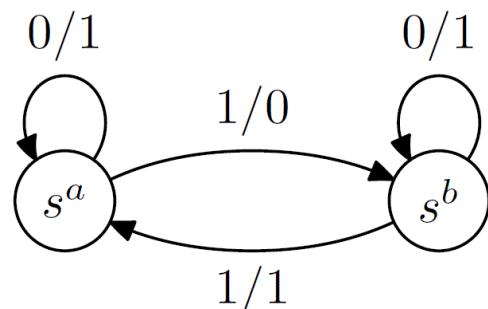Transformation of a Mealy automaton into a partially equivalent Moore automaton



$$\begin{aligned}
 s^a/1 &\rightarrow s^1 \\
 s^b/0 &\rightarrow s^2 \\
 s^b/1 &\rightarrow s^3
 \end{aligned}$$

x


s	0	1
s^a	$s^a/1$	$s^b/0$
s^b	$s^b/1$	$s^a/1$

s'/y



x

s	0	1	y
s^1	s^1	s^2	1
s^2	s^3	s^1	0
s^3	s^3	s^1	1

s'/y

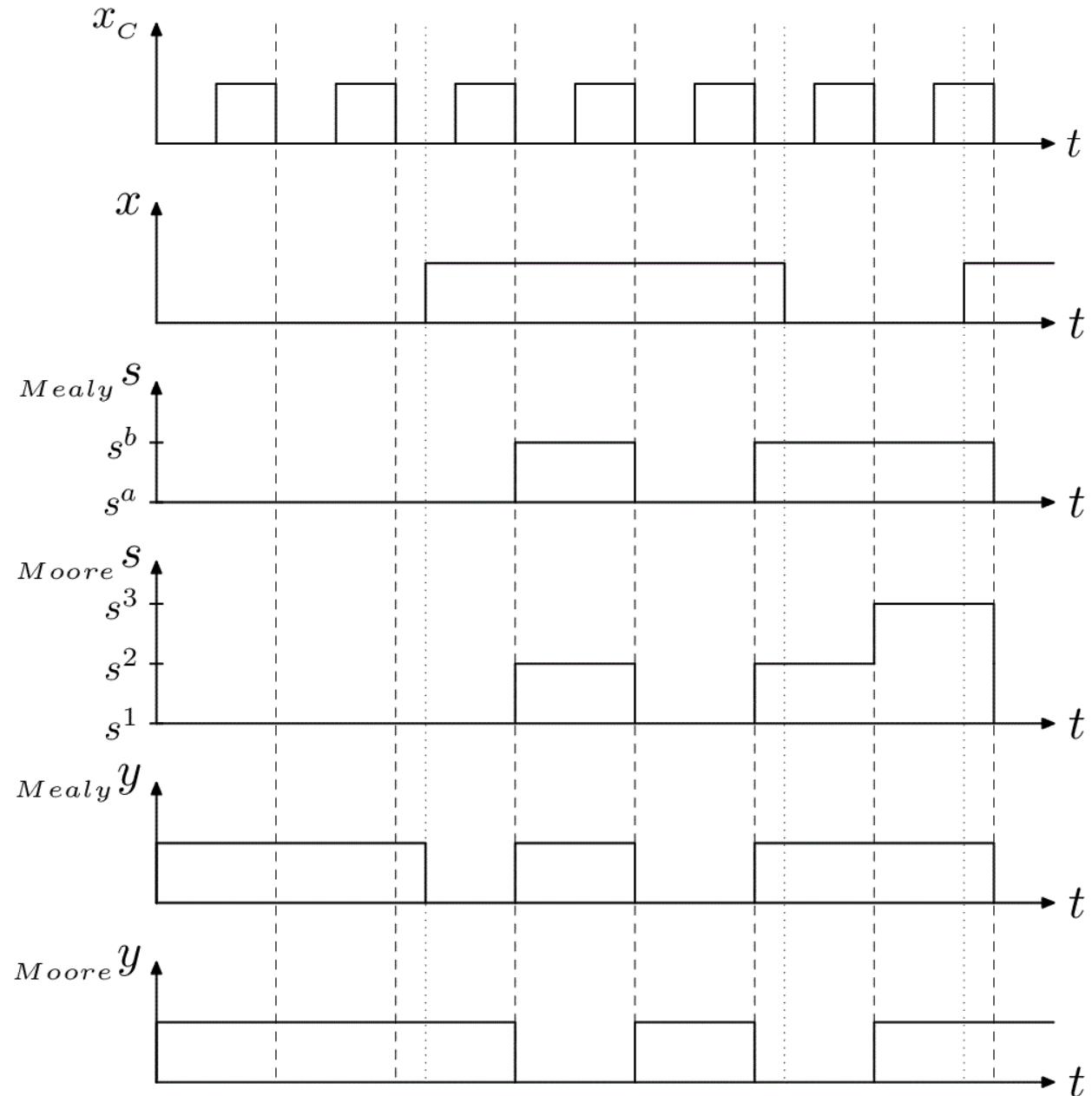

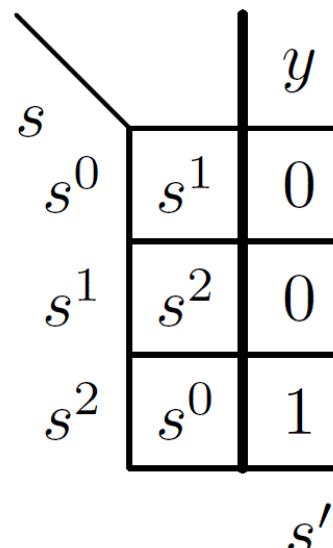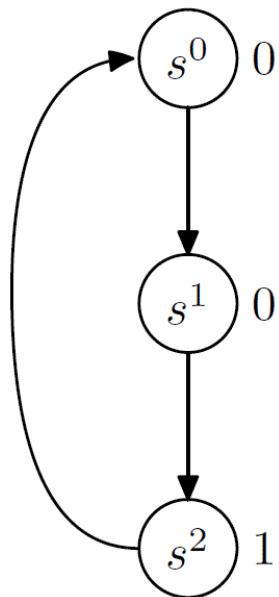Frequency divider by 3 (inputless circuit)




$$\begin{array}{c}
 \begin{array}{ccc}
 s & \rightarrow & q_1 & q_0 \\
 \hline
 s^0 & \rightarrow & 0 & 0 \\
 s^1 & \rightarrow & 0 & 1 \\
 s^2 & \rightarrow & 1 & 0
 \end{array}
 \end{array}$$

		y
$q_1 q_0$		
00	01	0
01	10	0
11	—	—
10	00	1


q_0	0	1
q_1	0	0
1	0	—

q_0	0	1
q_1	0	1
1	0	—


q_0	0	1
q_1	0	0
1	1	—

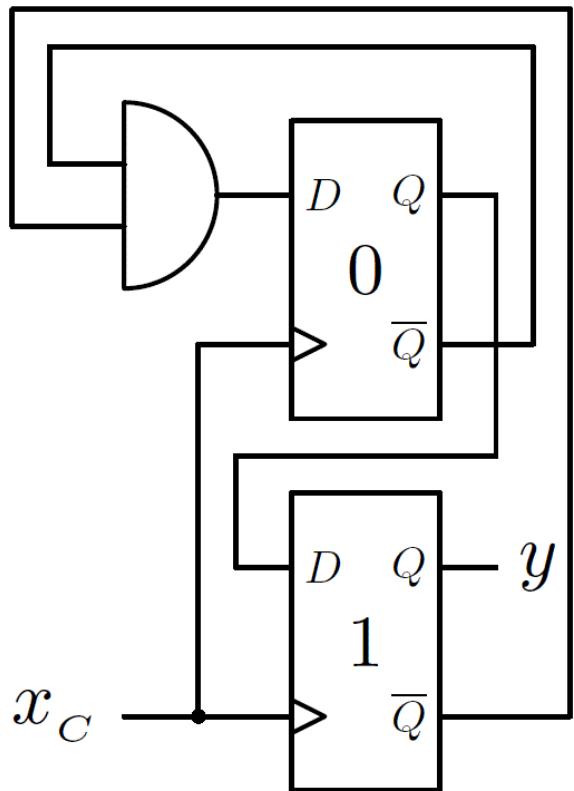

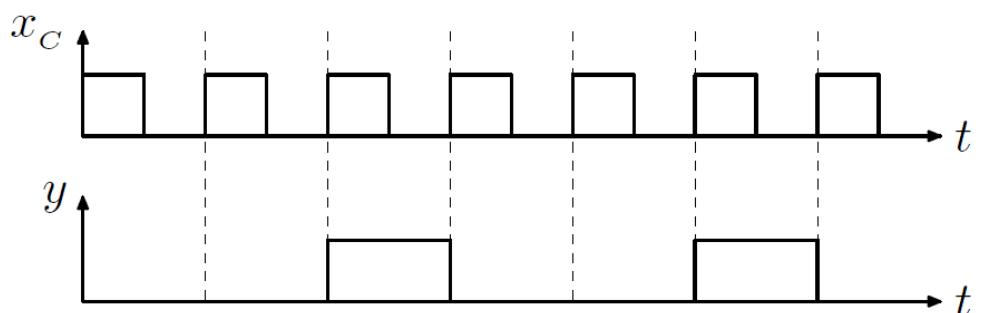
$$\begin{cases} q'_0 = \bar{q}_1 \bar{q}_0 \\ q'_1 = q_0 \\ y = q_1 \end{cases}$$



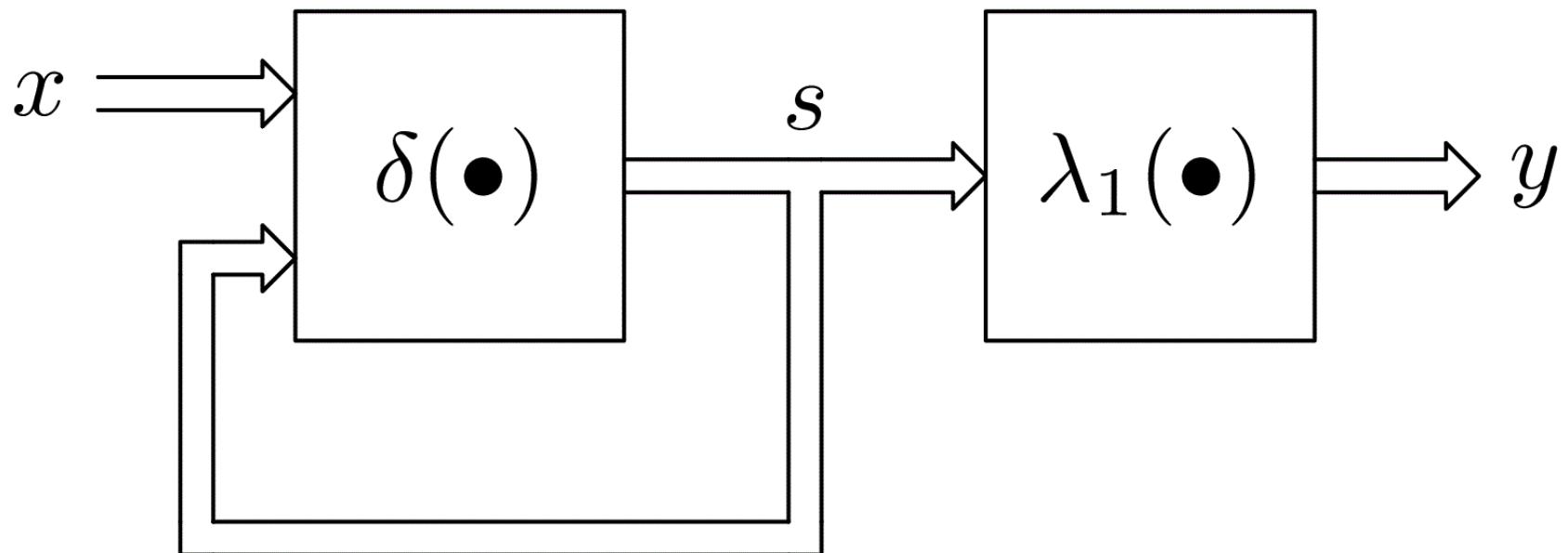Structure of asynchronous Moore automaton



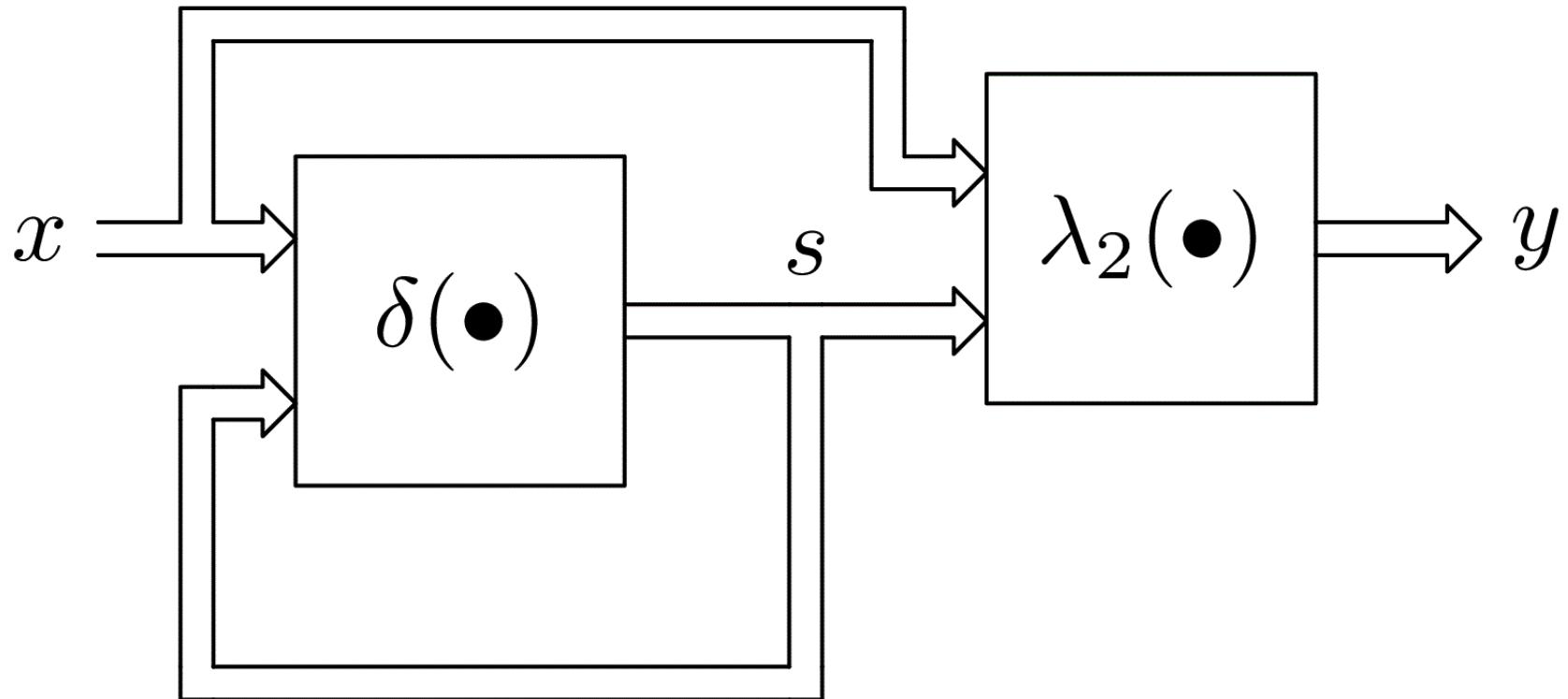
Structure of asynchronous Mealy automaton



Definitions


Stable state under the influence of input x

$$\delta(s^k, x) = s^k$$

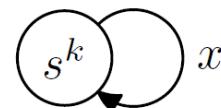

Unstable state under the influence of input x

$$\delta(s^k, x) = s^j, \quad j \neq k$$


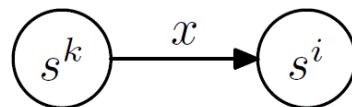



- ★ Each of the above transitions takes τ

Limitations imposed on the design of asynchronous automata:

- when an input x changes only one signal x_j changes
 $x = [x_1, \dots, x_j, \dots, x_n]$
- the next input change may take place only when the time (τ), necessary for the internal state to become stable, has elapsed

Non-overreacting aircon controller

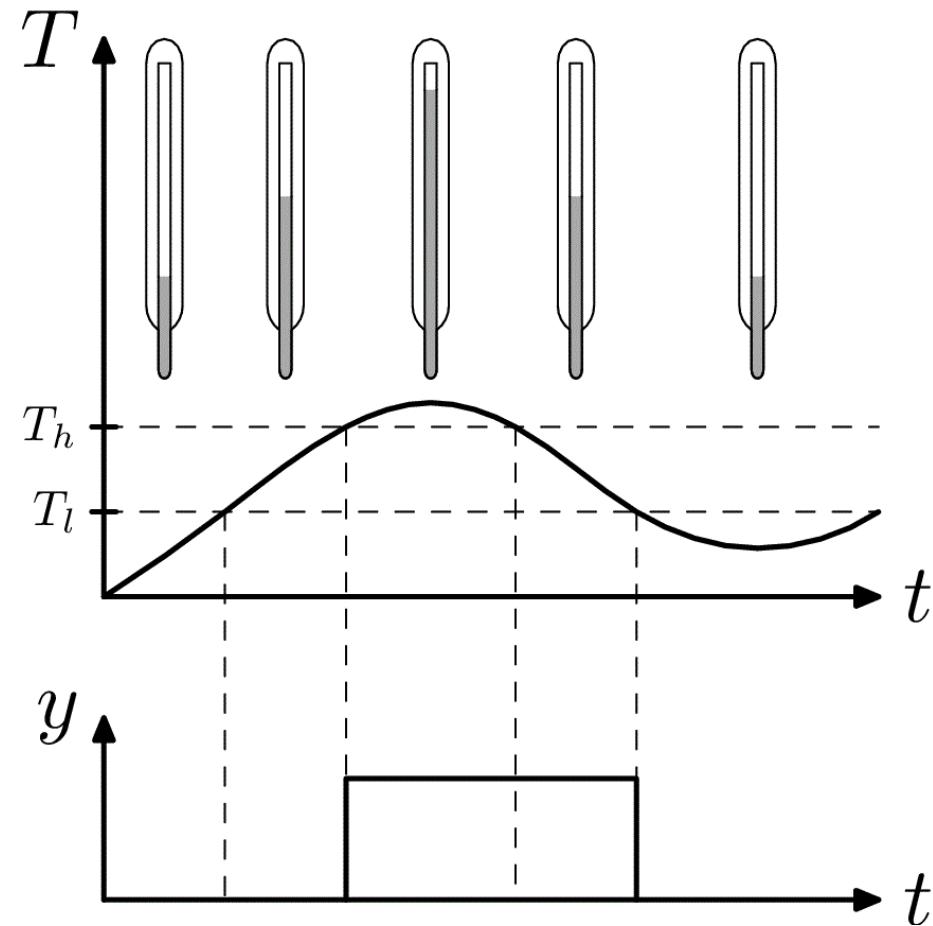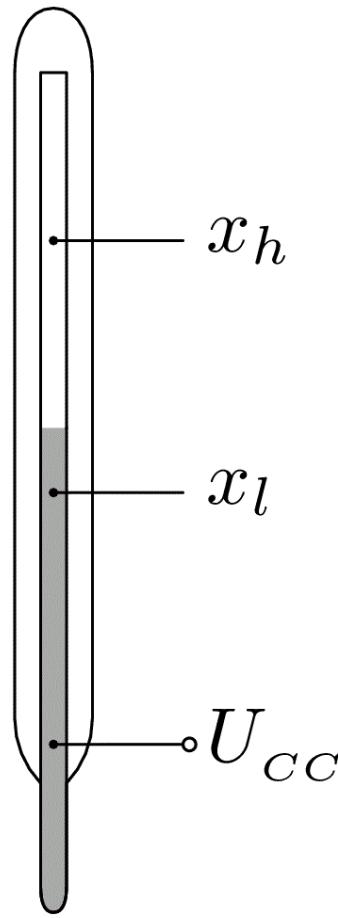


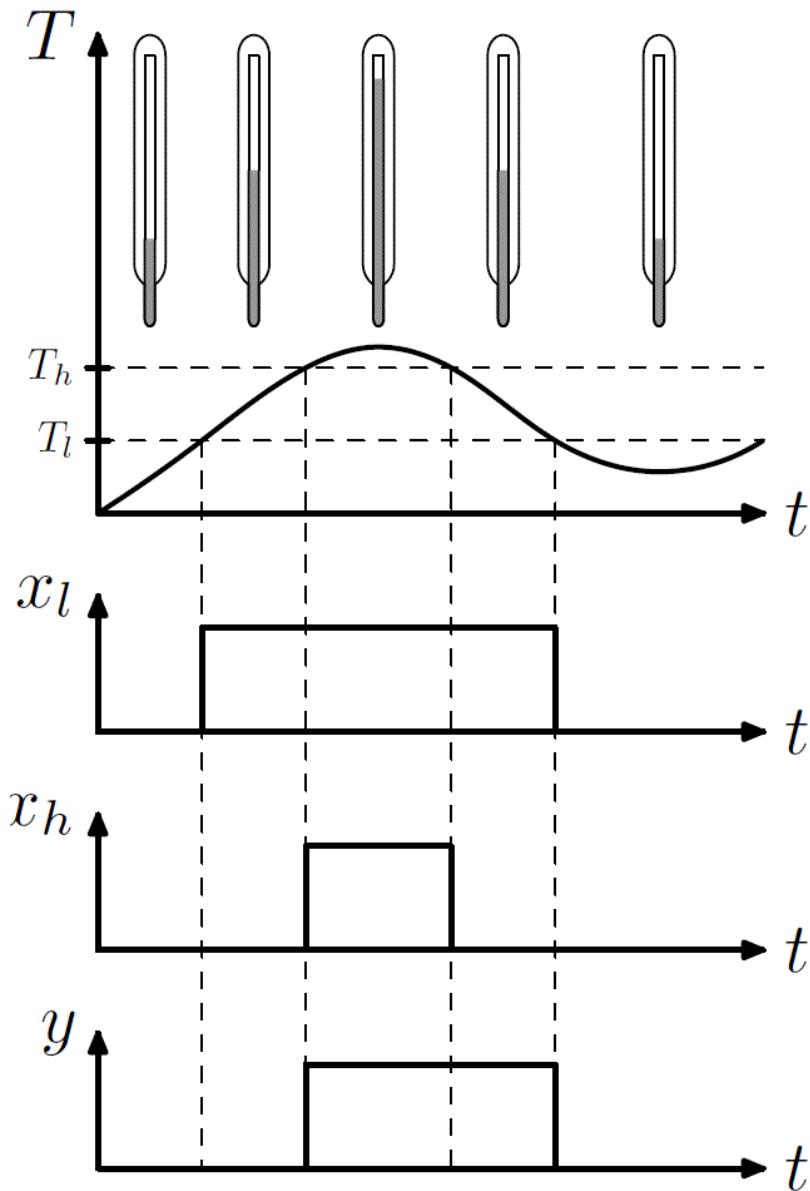

T	x_h	x_l
$T < T_l$	0	0
$T_l \leq T < T_h$	0	1
$T \geq T_h$	1	1
—	1	0

$x_h x_l = 01 \Rightarrow y = 0 \text{ or } y = 1$
 \Rightarrow this is not a combinational problem
 \Rightarrow memory is needed

Graph of the aircon controller

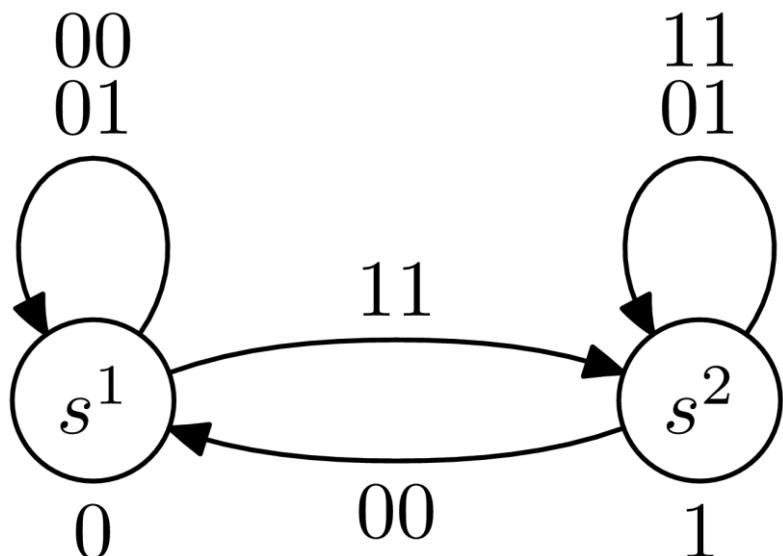

Its state transition
and output table

$x_h x_l$

s	00	01	11	10	y
s^1	s^1	s^1	s^2	-	0
s^2	s^1	s^2	s^2	-	1
s' / y					

Coding

s	\rightarrow	q	y
s_1	\rightarrow	0	0
s_2	\rightarrow	1	1

$$\Rightarrow y = q$$

$$q' = x_h + qx_l$$


Coded state transition table

$x_h x_l$




q	00	01	11	10
0	0	0	1	-
1	0	1	1	-







$$q'$$

Circuit diagram

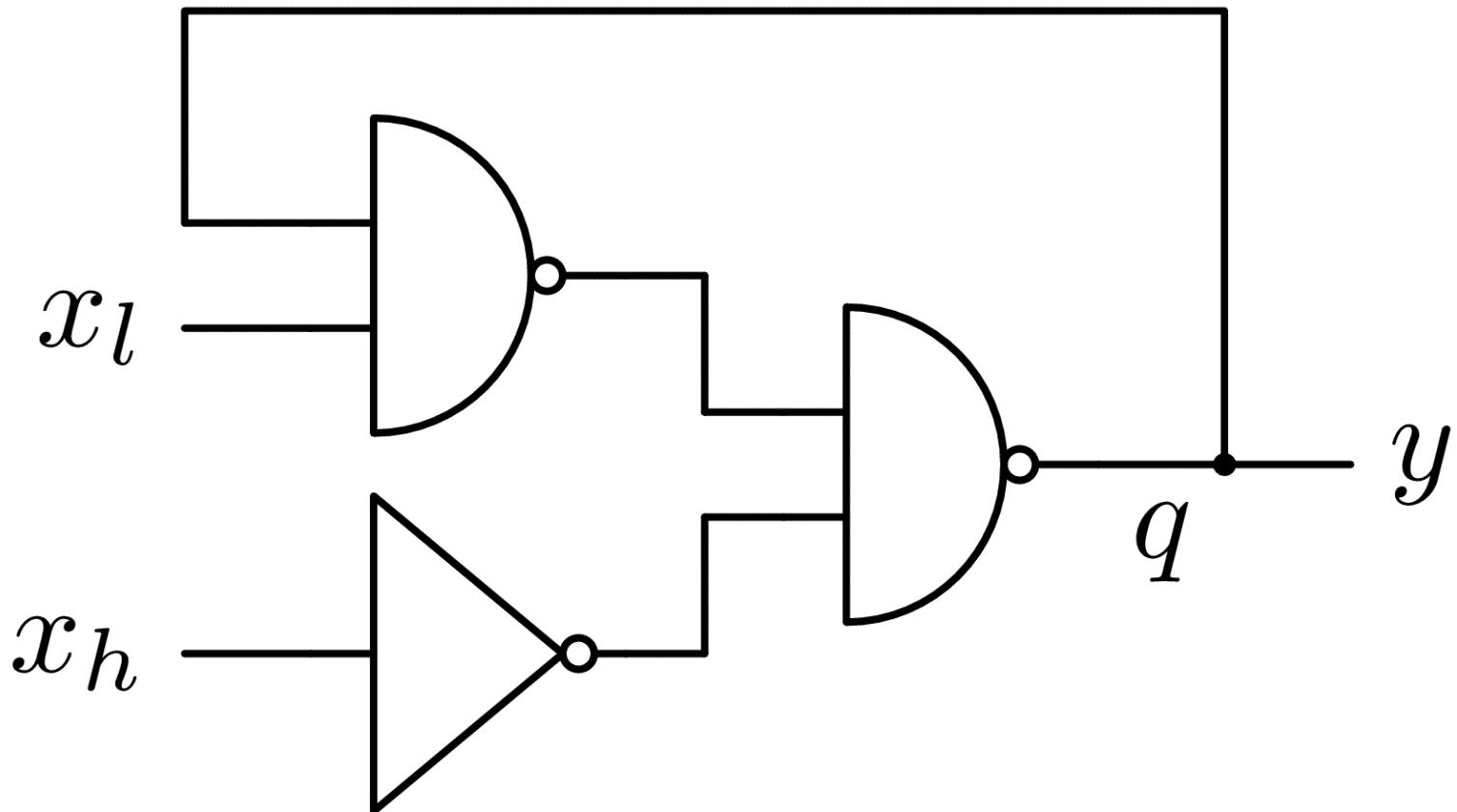

Negative-edge triggered D-type flip-flop

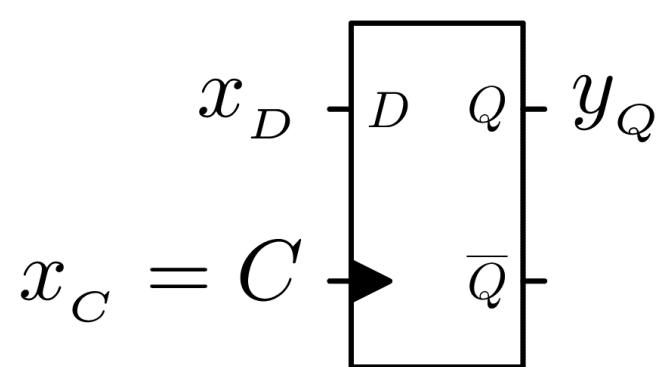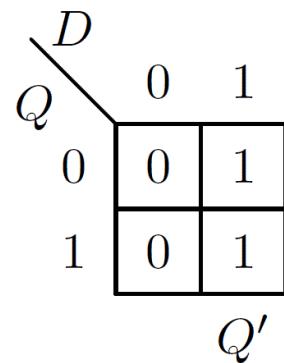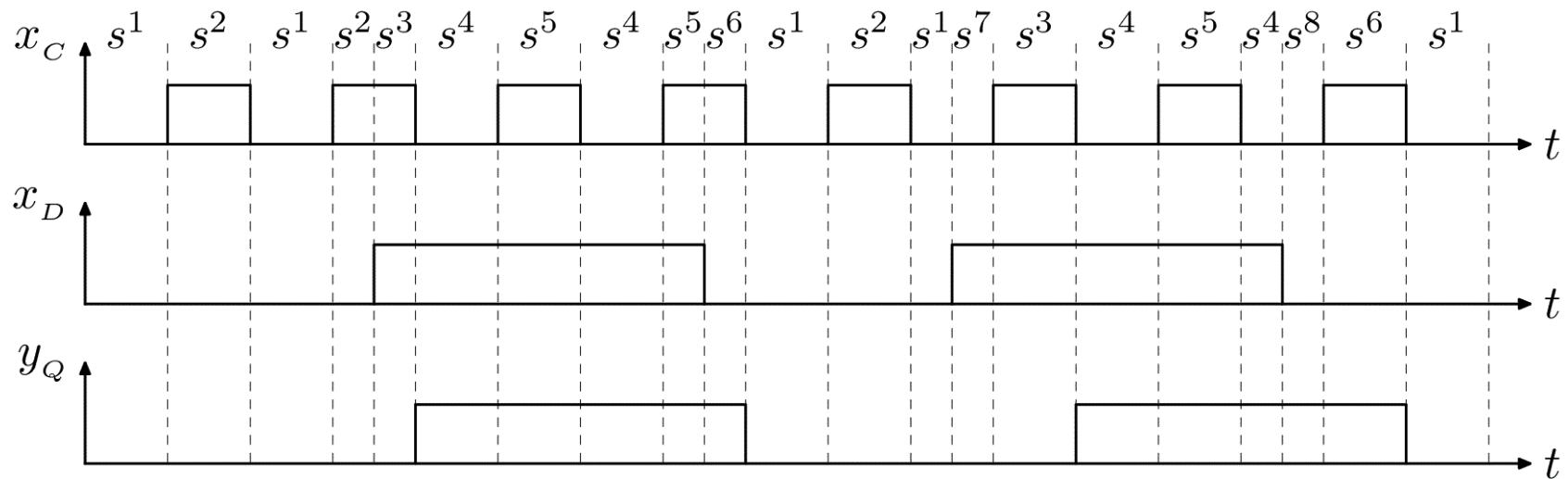

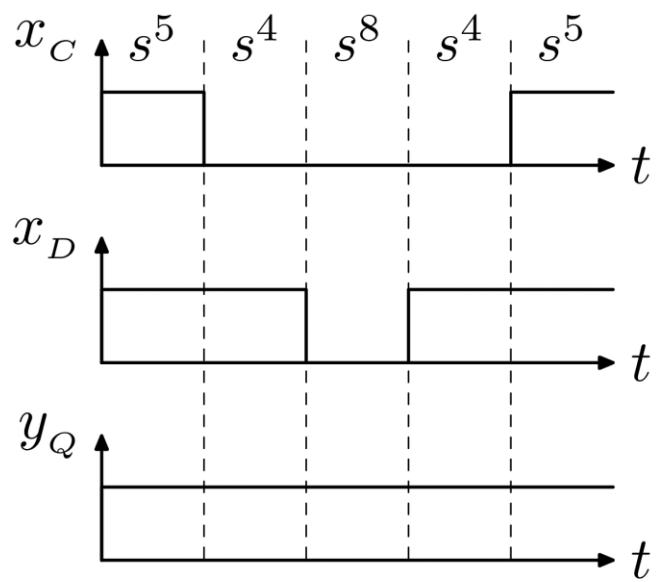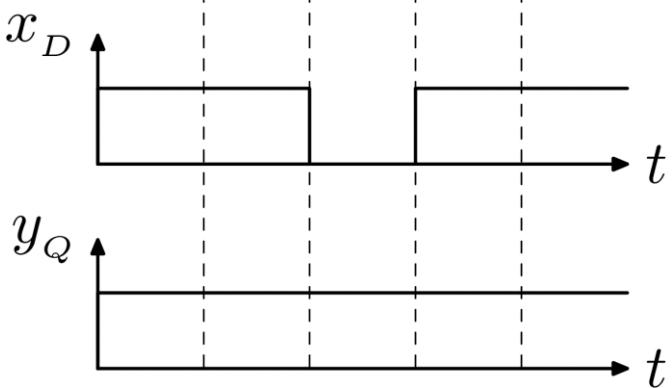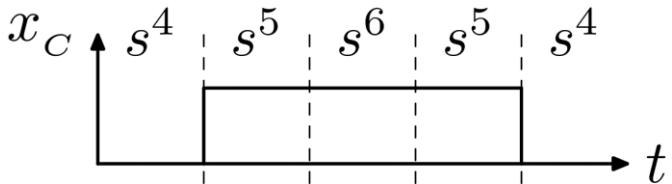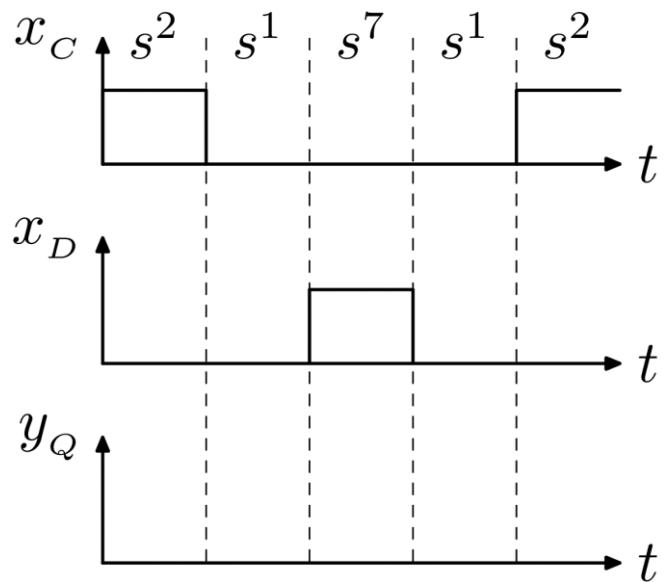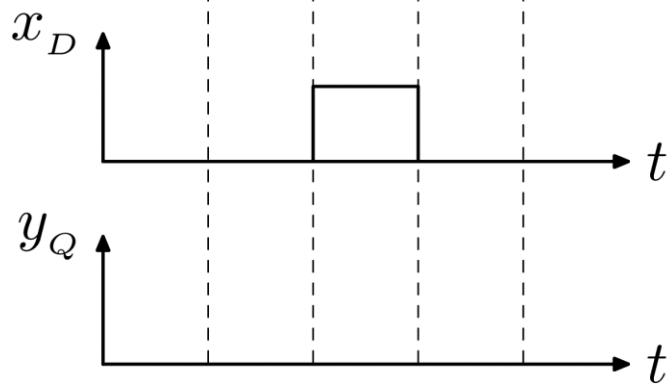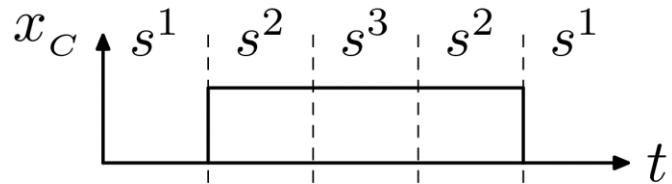

	x_C	x_D	00	01	11	10	y_Q
s							
s^1	s^1		s^7	—		s^2	0
s^2	s^1	—		s^3	s^2		0
s^3	—		s^4	s^3			0
s^4	s^8	s^4		s^5	—		1
s^5	—		s^4	s^5		s^6	1
s^6	s^1	—			s^6		1
s^7				s^7	s^3	—	0
s^8	s^8			—		s^6	1

s'/y_Q

	x_C	x_D	00	01	11	10	y_Q
s							
s^1	s^1		s^7	—		s^2	0
s^2	s^1	—		s^3	s^2		0
s^3	—		s^4	s^3	s^2		0
s^4	s^8	s^4		s^5	—		1
s^5	—		s^4	s^5		s^6	1
s^6	s^1	—			s^5	s^6	1
s^7	s^1	s^7		s^3	—		0
s^8	s^8			s^4	—	s^6	1


s'/y_Q

Minimization

Triangular table

s^2							
s^3	s^4 , s^7						
s^4							
s^5							
s^6				s^1 , s^8			
s^7			s^4 , s^7				
s^8					s^1 , s^8		
	s^1	s^2	s^3	s^4	s^5	s^6	s^7

Compatibility graph

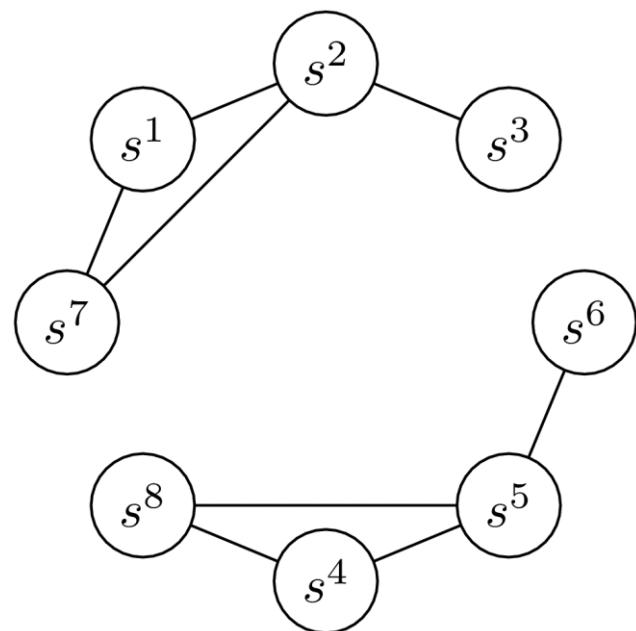

Two reasonable state substitutions:

$$\left\{ \begin{array}{l} \{s^1, s^2, s^7\} \rightarrow s^a \\ \{s^4, s^5, s^8\} \rightarrow s^b \\ \{s^3\} \rightarrow s^c \\ \{s^6\} \rightarrow s^d \end{array} \right.$$

$$\left\{ \begin{array}{l} \{s^1, s^7\} \rightarrow s^\alpha \\ \{s^4, s^8\} \rightarrow s^\beta \\ \{s^2, s^3\} \rightarrow s^\gamma \\ \{s^5, s^6\} \rightarrow s^\omega \end{array} \right.$$


Coding – first try

$$\begin{array}{rcc} s & \rightarrow & q_1 \quad q_2 \\ \hline s^a & \rightarrow & 0 \quad 0 \\ s^b & \rightarrow & 1 \quad 0 \\ s^c & \rightarrow & 0 \quad 1 \\ s^d & \rightarrow & 1 \quad 1 \end{array}$$

	x_C	x_D	00	01	11	10	y_Q
s							
s^a	(s^a)	(s^a)	s^c	(s^a)			0
s^b	(s^b)	(s^b)	(s^b)		s^d		1
s^c	—	s^b	(s^c)	s^a			0
s^d	s^a	—	s^b	(s^d)			1
							s' / y_Q

Coding causing a critical race

	x_C	x_D	00	01	11	10	y_Q
$q_1 q_2 \setminus s$	00	01	11	10			
00 $\leftarrow s^a$	s^a	s^a	s^c	s^a			0
10 $\leftarrow s^b$	s^b	s^b	s^b	s^d			1
01 $\leftarrow s^c$	—	s^b	s^c	s^a			0
11 $\leftarrow s^d$	s^a	—	s^b	s^d			1
						s' / y_Q	

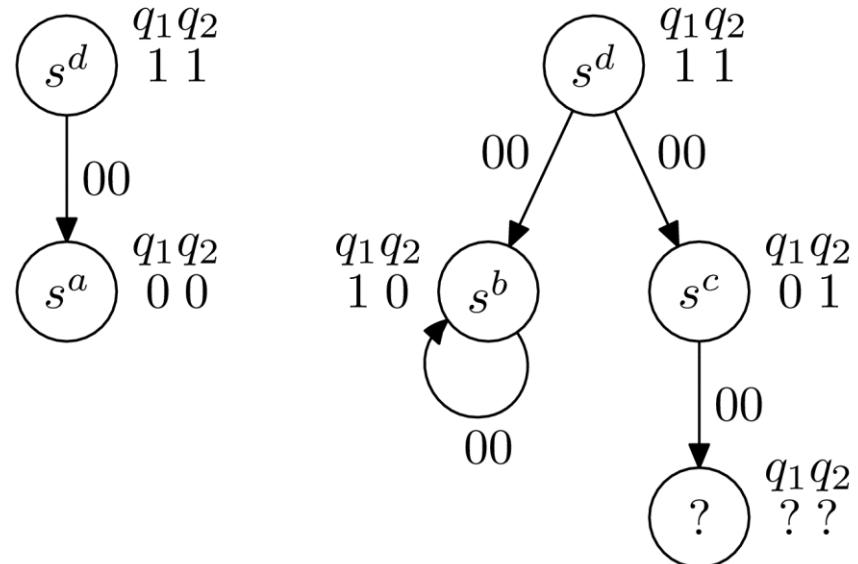

Coding causing a critical race



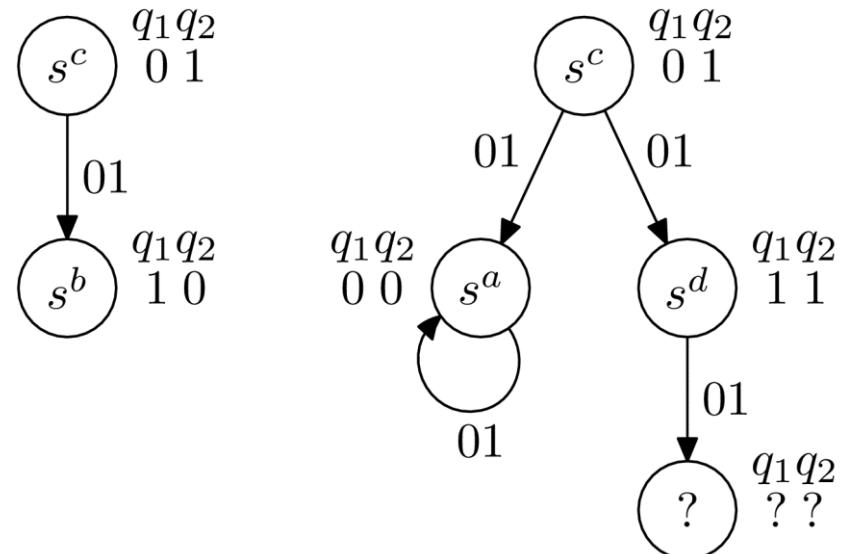
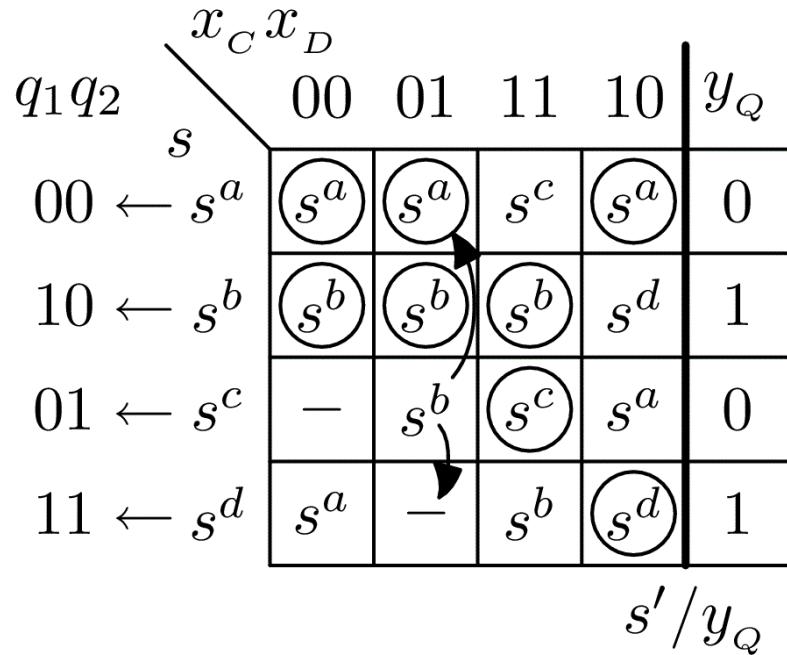
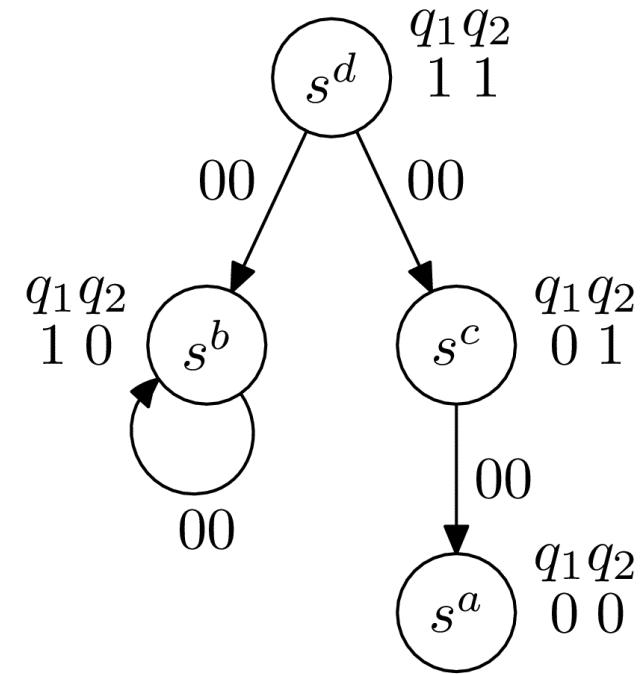





Illustration of a critical and a non-critical race

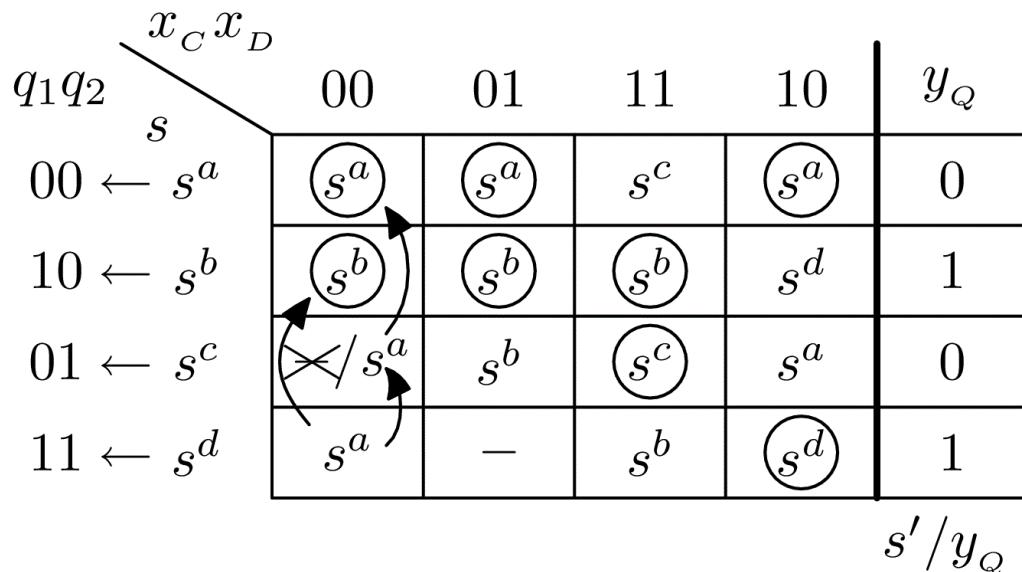


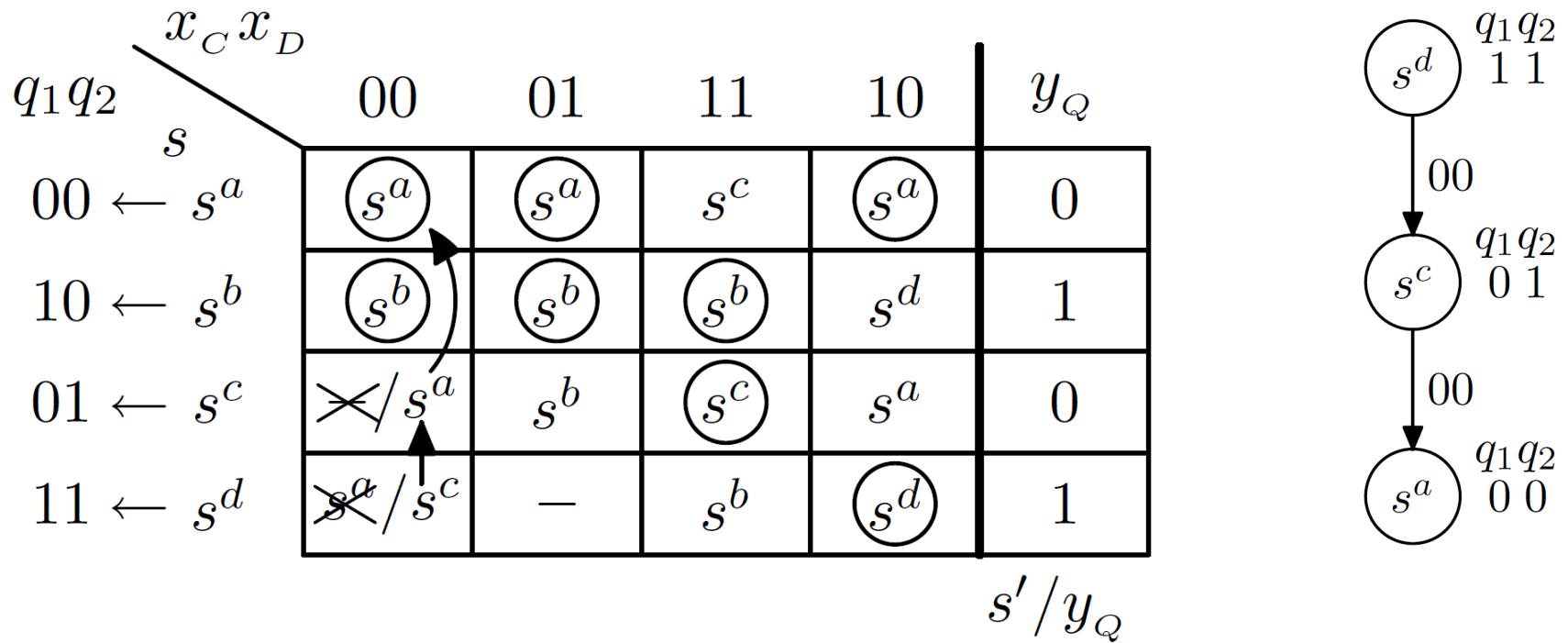Partial solution by introducing a cyclic transition





Hypercube

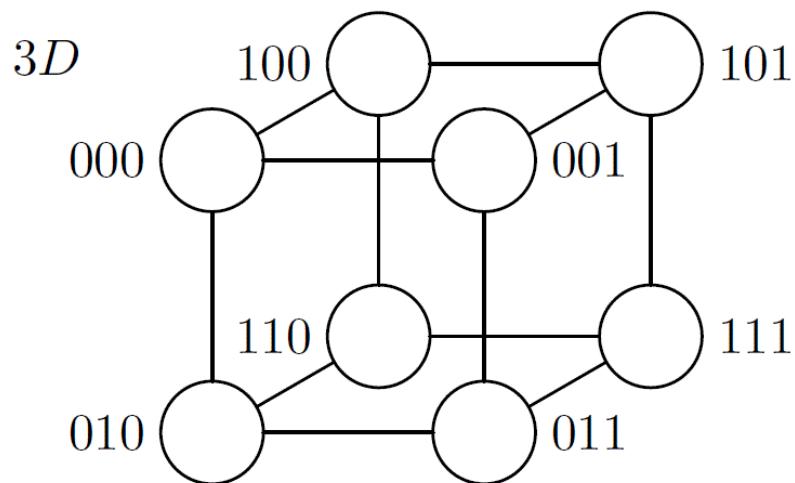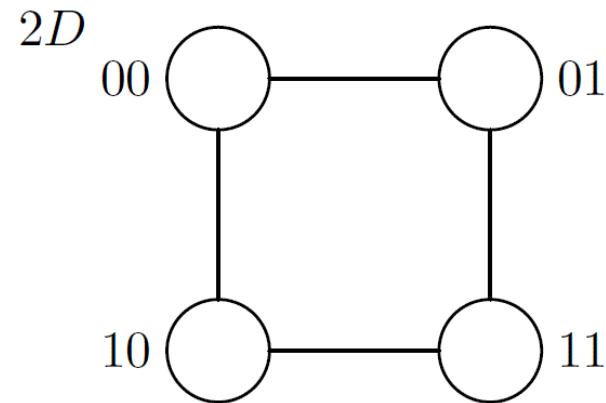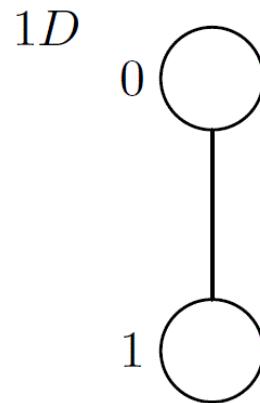

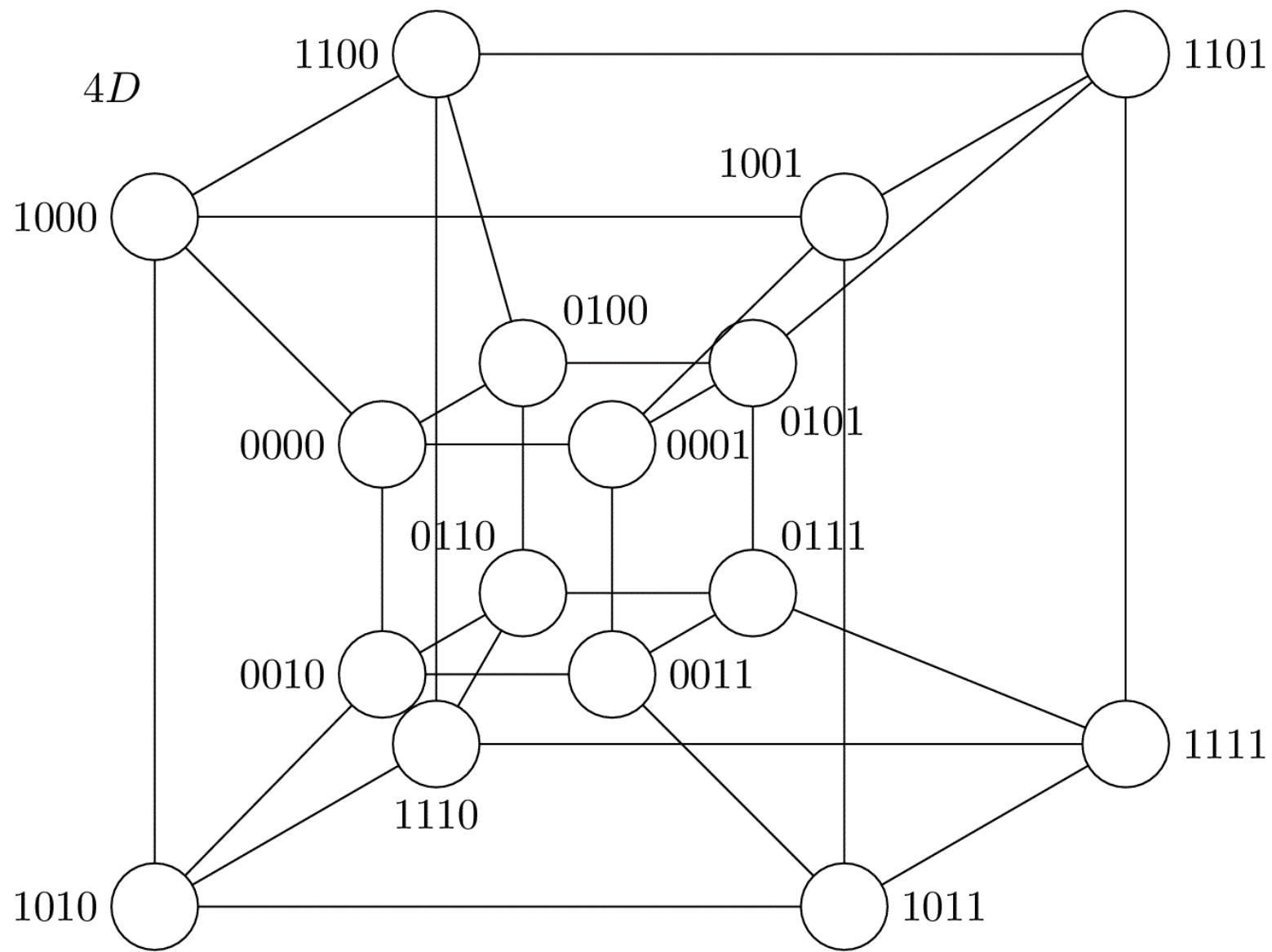

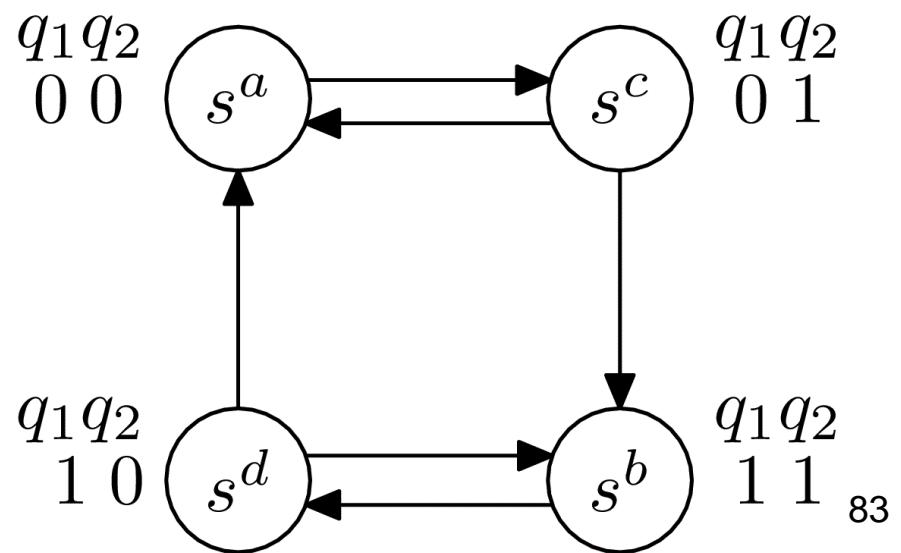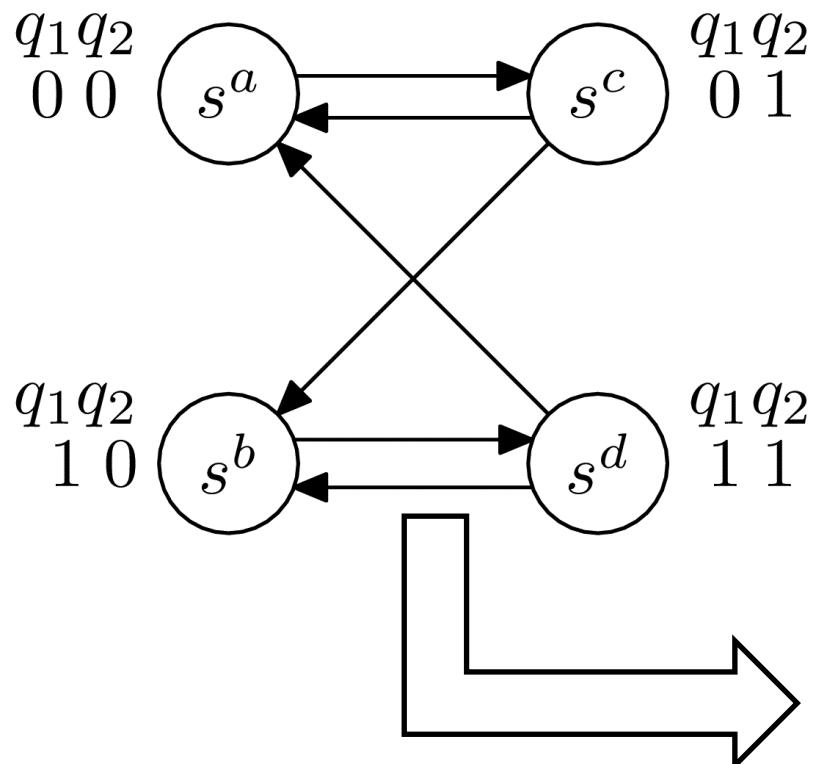State transition graph transformation - coding method



Final coding

$q_1 q_2$	x_C	x_D	00	01	11	10	y_Q
s			s^a	s^a	s^c	s^a	0
$00 \leftarrow s^a$							
$01 \leftarrow s^c$			—	s^b	s^c	s^a	0
$11 \leftarrow s^b$			s^b	s^b	s^b	s^d	1
$10 \leftarrow s^d$			s^a	—	s^b	s^d	1
							s'/y_Q

Coded state transition and output table

x_C	x_D	00	01	11	10	y_Q
$q_1 q_2$	00	00	00	01	00	0
	01	—	11	01	00	0
	11	11	11	11	10	1
	10	00	—	11	10	1
$q'_1 q'_2 / y_Q$						

$$\Rightarrow \quad y_Q = q_1$$


x_C	x_D	00	01	11	10
$q_1 q_2$	00	0	0	0	0
00	0	0	0	0	0
01	—	1	0	0	0
11	1	1	1	1	1
10	0	—	1	1	1

x_C	x_D	00	01	11	10
$q_1 q_2$	00	0	0	1	0
00	0	0	0	1	0
01	—	1	1	1	0
11	1	1	1	1	0
10	0	—	1	1	0

 q'_1
 q'_2

$$\left\{ \begin{array}{l} q'_1 = q_1 x_C + q_1 q_2 + q_2 \bar{x}_C \\ q'_2 = q_2 x_D + x_C x_D + q_2 \bar{x}_C \\ y_Q = q_1 \end{array} \right.$$

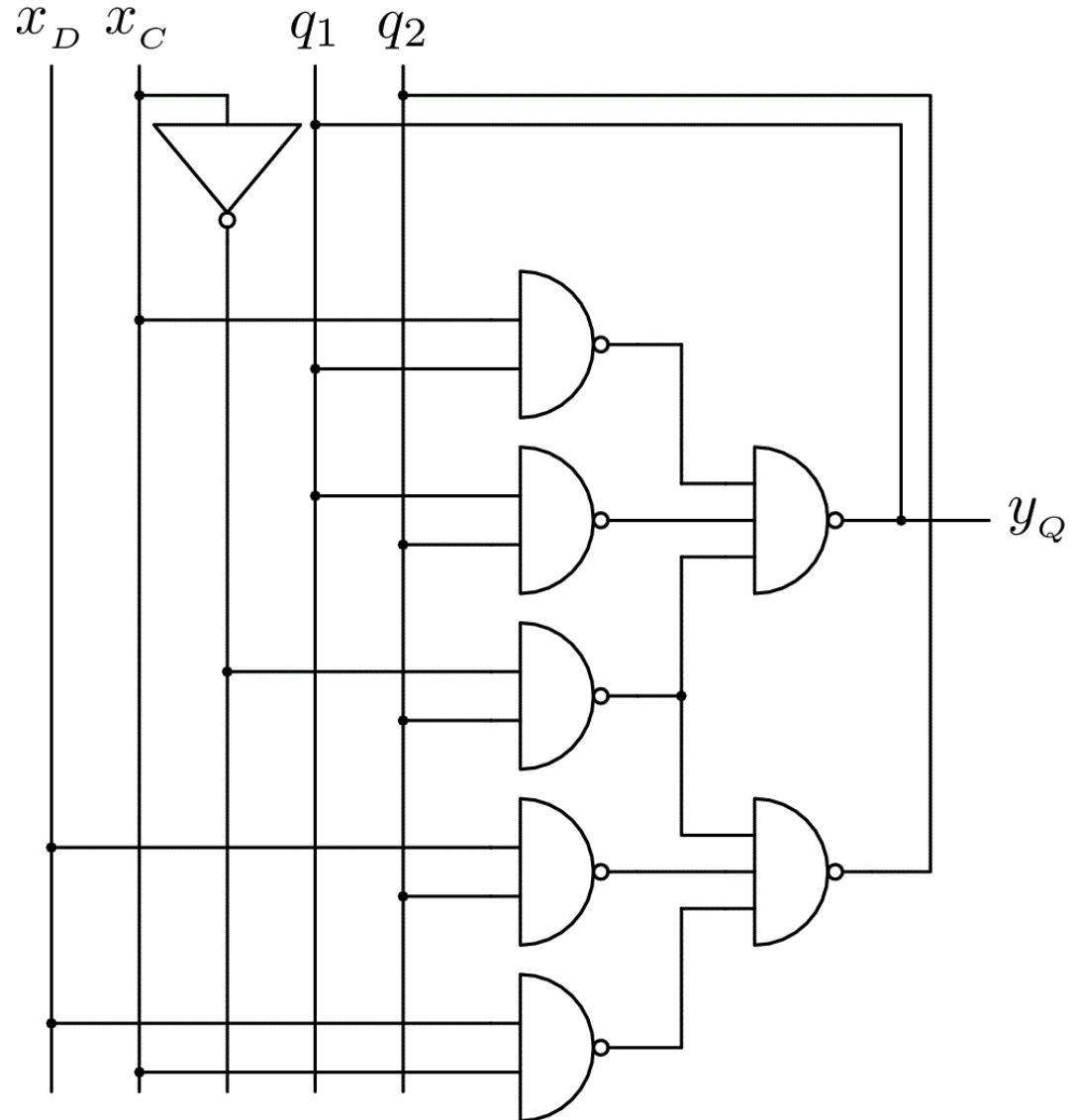Circuit diagram of the negative-edge triggered D-type flip-flop





- D-type flip-flop is an asynchronous automaton
 - Synchronous automatons are constructed out of D-type flip-flops and combinational logic
- ⇒ Every synchronous automaton is a special case of an asynchronous automaton

Alternative method of minimizing asynchronous automata

1. It is a Moore automaton table.
 2. Each row contains a single stable state.
 3. All unstable next states s^k appear only in the column in which the state s^k is stable.
-
- Property (3) \Rightarrow conditions for compatibility can appear only between states that are stable in the same column

The process of minimization can be divided into two phases:

1. Finding pseudoequivalent states
(at this stage conditional compatibility is taken into account)
2. Finding pseudocompatible states
(at this stage the states are pseudocompatible unconditionally)

Pseudoequivalent states

States that are being stable in the same column of the initial table and at the same time are being compatible.

$$(s^i \cong s^j) \iff \exists x : (\delta(s^i, x) = s^i) \wedge (\delta(s^j, x) = s^j) \wedge (s^i \approx s^j)$$

Moore pseudocompatible states

States for which the next states are non-contradictory and
the outputs are also non-contradictory

$$(s^i \approx s^j) \iff \left(\forall x \ (\delta(s^i, x) \simeq \delta(s^j, x)) \right) \wedge \\ (\lambda_1(s^i) \simeq \lambda_1(s^j))$$

Mealy pseudocompatible states

States for which the next states are non-contradictory

$$(s^i \sim s^j) \iff \forall x \ (\delta(s^i, x) \simeq \delta(s^j, x))$$

Minimisation of the number of states of an asynchronous automaton – mathematical formulation of phase 1

$\forall \left(\left({}_{A_1} S^k \subset {}_{A_1} S \right) : \left(\forall \left({}_{A_1} s^{k_i}, {}_{A_1} s^{k_j} \in {}_{A_1} S^k \right) \left({}_{A_1} s^{k_i} \cong {}_{A_1} s^{k_j} \right) \right) \right)$
 and $k, k' = 1, \dots, n$

the following conditions must be fulfilled:

$$({}_{A_1} s^{k_i} \in {}_{A_1} S^k) \wedge ({}_{A_1} s^{k_j} \in {}_{A_1} S^{k'}) \wedge (k \neq k') \Rightarrow (k_i \neq k_j)$$

$$\left(\bigcup_{k=1}^n {}_{A_1} S^k \right) = {}_{A_1} S \longrightarrow \text{cover condition}$$

$$\left(\forall \left({}_{A_1} s^{k_i}, {}_{A_1} s^{k_j}, x \right) : \left({}_{A_1} s^{k_i}, {}_{A_1} s^{k_j} \in {}_{A_1} S^k \right) \right)$$

$$\Rightarrow \left(\exists {}_{A_1} S^{k'} : \left(\delta({}_{A_1} s^{k_i}, x), \delta({}_{A_1} s^{k_j}, x) \in {}_{A_1} S^{k'} \right) \right)$$

→ closure condition

$${}_{A_1}S^k \rightarrow {}_{A_2}s^k, \quad {}_{A_2}s^k \in {}_{A_2}S$$

where:

${}_{A_1}S$ – set of states of initial automaton A_1

${}_{A_1}S^k$ – k th set of pseudoequivalent states of automaton A_1

${}_{A_1}S^{k'}$ – k' th set of pseudoequivalent states of automaton A_1

${}_{A_2}S$ – set of states of minimized automaton A_2

n – number of sets of pseudoequivalent states

Minimisation of the number of states of an asynchronous automaton - mathematical formulation of phase 2

$\forall \left(\left({}_{A_1} S^k \subset {}_{A_1} S \right) : \left(\forall \left({}_{A_1} s^{k_i}, {}_{A_1} s^{k_j} \in {}_{A_1} S^k \right) \left({}_{A_1} s^{k_i} \approx {}_{A_1} s^{k_j} \right) \right) \right)$

and $k, k' = 1, \dots, n$

the following conditions must be fulfilled:

$$({}_{A_1} s^{k_i} \in {}_{A_1} S^k) \wedge ({}_{A_1} s^{k_j} \in {}_{A_1} S^{k'}) \wedge (k \neq k') \Rightarrow (k_i \neq k_j)$$

$$\left(\bigcup_{k=1}^n {}_{A_1} S^k \right) = {}_{A_1} S \quad \longrightarrow \quad \text{cover condition}$$

$${}_{A_1} S^k \rightarrow {}_{A_2} s^k, \quad {}_{A_2} s^k \in {}_{A_2} S$$

where:

- $A_1 S$ – set of states of initial automaton A_1
- $A_1 S^k$ – k th set of pseudocompatible states of automaton A_1
- $A_1 S^{k'}$ – k' th set of pseudocompatible states of automaton A_1
- $A_2 S$ – set of states of minimized automaton A_2
- n – number of sets of pseudocompatible states

- If Moore pseudocompatibility (\approx) is substituted by Mealy pseudocompatibility (\sim) the above minimization procedure will lead to a Mealy automaton instead of a Moore automaton.

Negative-edge triggered D-type flip-flop (cntd)

x_C	x_D	00	01	11	10	y_Q
s						
s^1	(s^1)	s^7	—	s^2		0
s^2	s^1	—	s^3	(s^2)		0
s^3	—	s^4	(s^3)	s^2		0
s^4	s^8	(s^4)	s^5	—		1
s^5	—	s^4	(s^5)	s^6		1
s^6	s^1	—	s^5	(s^6)		1
s^7	(s^1)	(s^7)	s^3	—		0
s^8	(s^8)	s^4	—	s^6		1
					s'/y_Q	

$s^1 \not\cong s^8$ because $\lambda_1(s^1) = 0, \lambda_1(s^8) = 1$

$s^3 \not\cong s^5$ because $\lambda_1(s^3) = 0, \lambda_1(s^5) = 1$

$s^2 \not\cong s^6$ because $\lambda_1(s^2) = 0, \lambda_1(s^6) = 1$

$s^4 \not\cong s^7$ because $\lambda_1(s^4) = 1, \lambda_1(s^7) = 0$

$\Rightarrow \lambda_1(s^1) \neq \lambda_1(s^8)$


$\Rightarrow \lambda_1(s^3) \neq \lambda_1(s^5)$

$\Rightarrow \lambda_1(s^2) \neq \lambda_1(s^6)$

$\Rightarrow \lambda_1(s^4) \neq \lambda_1(s^7)$

\Rightarrow there are no pseudoequivalent states

Graph of Moore pseudocompatible states

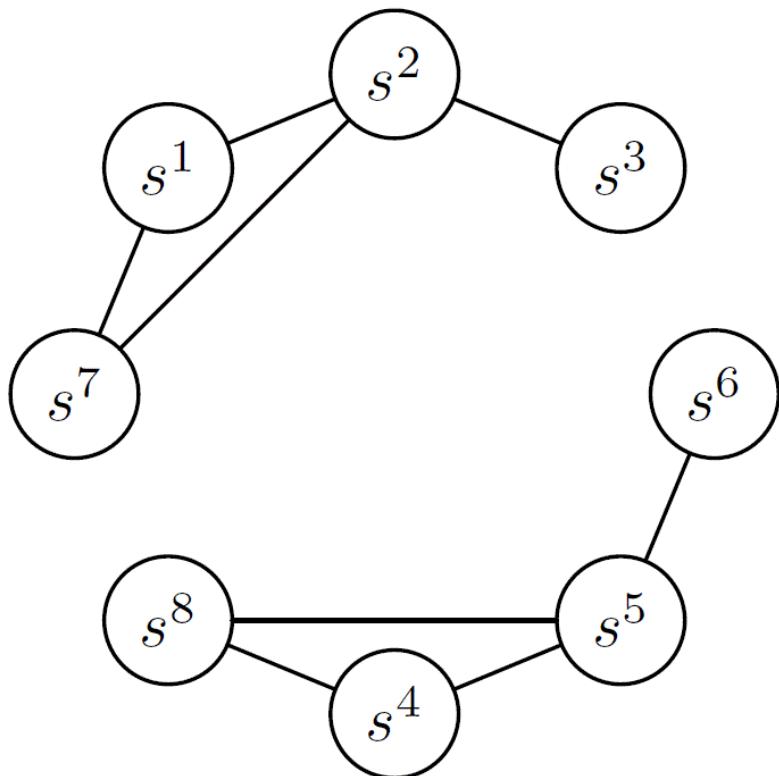


$$\left\{ \begin{array}{l} \{s^1, s^2, s^7\} \rightarrow s^a \\ \{s^4, s^5, s^8\} \rightarrow s^b \\ \{s^3\} \rightarrow s^c \\ \{s^6\} \rightarrow s^d \end{array} \right.$$

$$\left\{ \begin{array}{l} \{s^1, s^7\} \rightarrow s^\alpha \\ \{s^4, s^8\} \rightarrow s^\beta \\ \{s^2, s^3\} \rightarrow s^\gamma \\ \{s^5, s^6\} \rightarrow s^\omega \end{array} \right.$$

Pseudocompatible states are unconditionally pseudocompatible, so in the process of minimization only the cover condition must be fulfilled.

State transition and output table for the second state substitution

$x_C x_D$	00	01	11	10	y_Q
s					
s^α	s^α	s^α	s^γ	s^γ	0
s^β	s^β	s^β	s^ω	s^ω	1
s^γ	s^α	s^β	s^γ	s^γ	0
s^ω	s^α	s^β	s^ω	s^ω	1
					s'/y_Q

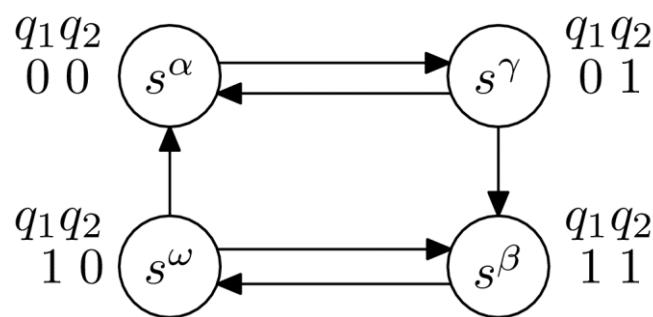

$x_C x_D$	00	01	11	10	y_Q
$q_1 q_2$					
$00 \leftarrow s^\alpha$	s^α	s^α	s^γ	s^γ	0
$01 \leftarrow s^\gamma$	s^α	s^β	s^γ	s^γ	0
$11 \leftarrow s^\beta$	s^β	s^β	s^ω	s^ω	1
$10 \leftarrow s^\omega$	s^α	s^β	s^ω	s^ω	1
Coding					s'/y_Q

x_C	x_D	00	01	11	10
$q_1 q_2$	00	0	0	0	0
	01	0	1	0	0
	11	1	1	1	1
	10	0	1	1	1

q'_1

x_C	x_D	00	01	11	10
$q_1 q_2$	00	0	0	1	1
	01	0	1	1	1
	11	1	1	0	0
	10	0	1	0	0


q'_2

x_C	x_D	00	01	11	10	y_Q
$q_1 q_2$	00	00	00	01	01	0
	01	00	11	01	01	0
	11	11	11	10	10	1
	10	00	11	10	10	1

$q'_1 q'_2 / y_Q$

$$\left\{ \begin{array}{l} q'_1 = q_1 x_C + q_1 x_D + q_1 q_2 + q_1 \bar{x}_C x_D \\ q'_2 = \bar{q}_1 x_C + q_1 q_2 \bar{x}_C + q_2 \bar{x}_C x_D + q_1 \bar{x}_C x_D + \bar{q}_1 q_2 x_D \\ y_Q = q_1 \end{array} \right.$$

Single-pulse extraction circuit



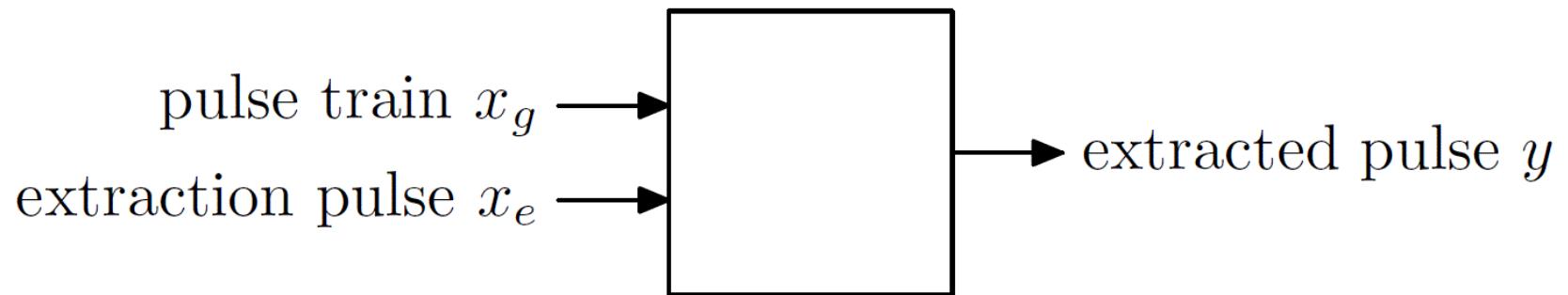


$$T|_{x_e=0} \gg T|_{x_g=0}$$


$$T|_{x_e=1} \gg T|_{x_g=1}$$

- Excel generated solutions will not be accepted
- Please provide hand-made truth tables with islands marked

Cause of the problem

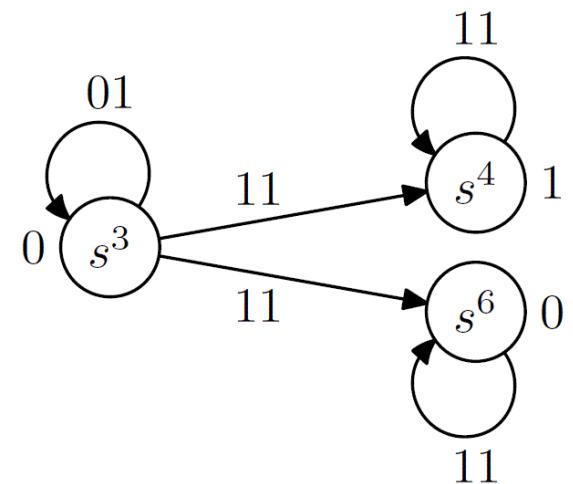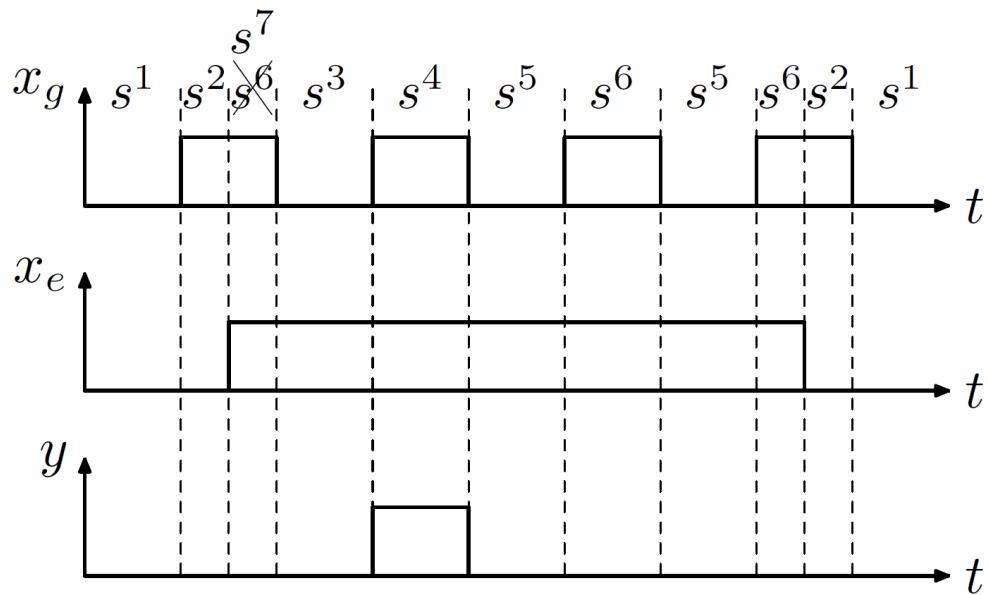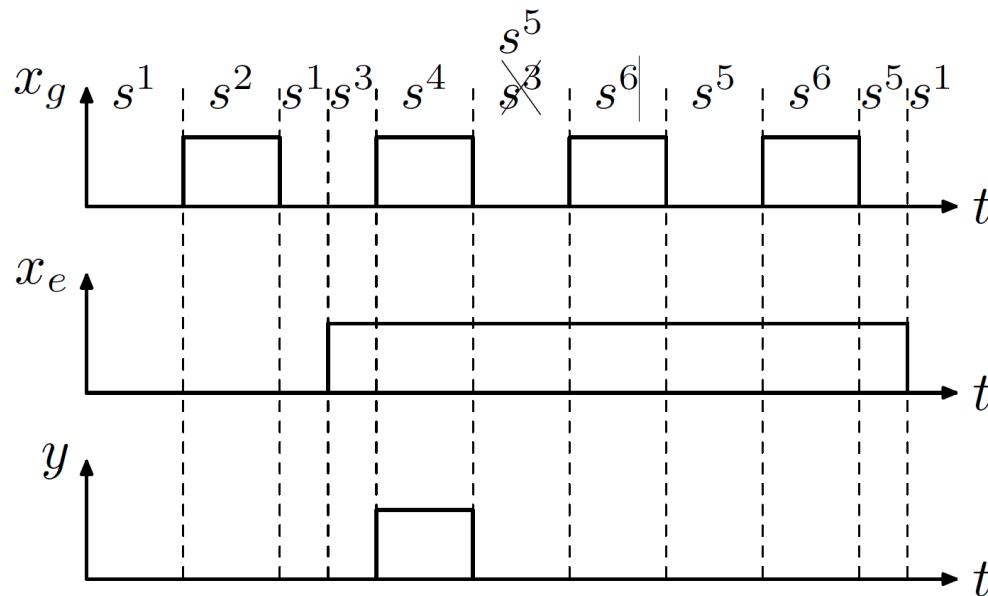


Solution to the problem

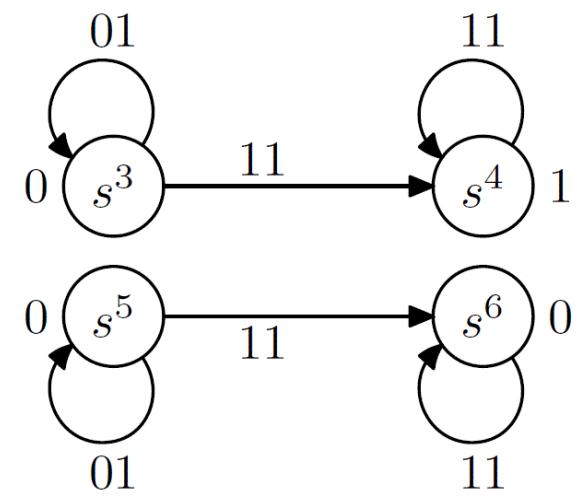

$x_g x_e$	00	01	11	10	y
s	00	01	11	10	
s^1	s^1	s^3	—	s^2	0
s^2	s^1	—	s^7	s^2	0
s^3	—	s^3	s^4	—	0
s^4	—	s^5	s^4	—	1
s^5	s^1	s^5	s^6	—	0
s^6	—	s^5	s^6	s^2	0
s^7	—	s^3	s^7	—	0

s'/y

Graph of Moore pseudocompatible states

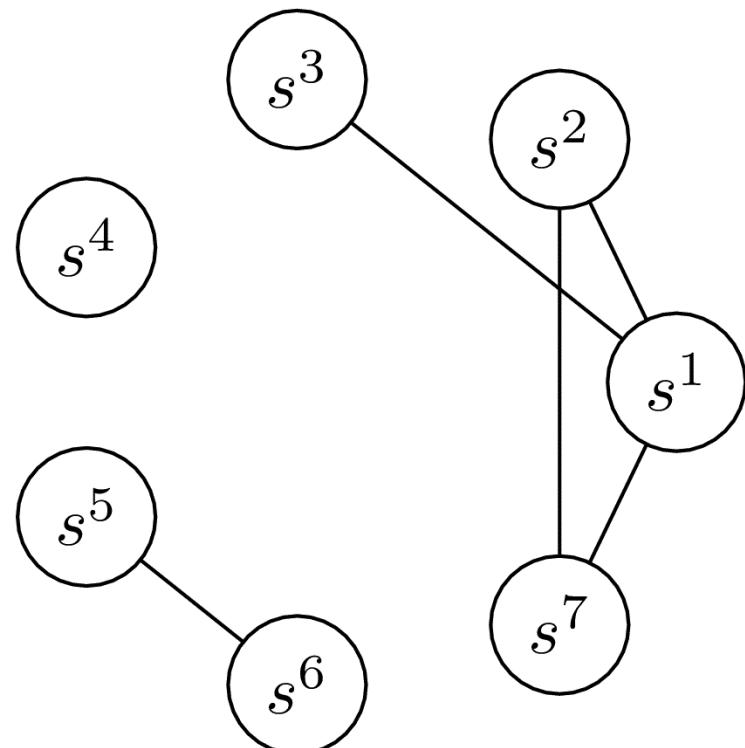

there are no pseudoequivalent states


Two reasonable state substitutions:

$$\left\{ \begin{array}{l} \{s^1, s^2, s^7\} \rightarrow s^a \\ \{s^3\} \rightarrow s^b \\ \{s^4\} \rightarrow s^c \\ \{s^5, s^6\} \rightarrow s^d \end{array} \right.$$

$$\left\{ \begin{array}{l} \{s^1, s^3\} \rightarrow s^\alpha \\ \{s^2, s^7\} \rightarrow s^\beta \\ \{s^4\} \rightarrow s^\gamma \\ \{s^5, s^6\} \rightarrow s^\omega \end{array} \right.$$

State transition and output table for the first state substitution

$x_g x_e$	00	01	11	10	y
s	s^a	s^b	s^a	s^a	0
s^a	s^a	s^b	s^c	—	0
s^b	—	s^b	—	—	0
s^c	—	s^d	s^c	—	1
s^d	s^a	s^d	s^d	s^a	0
s'/y					

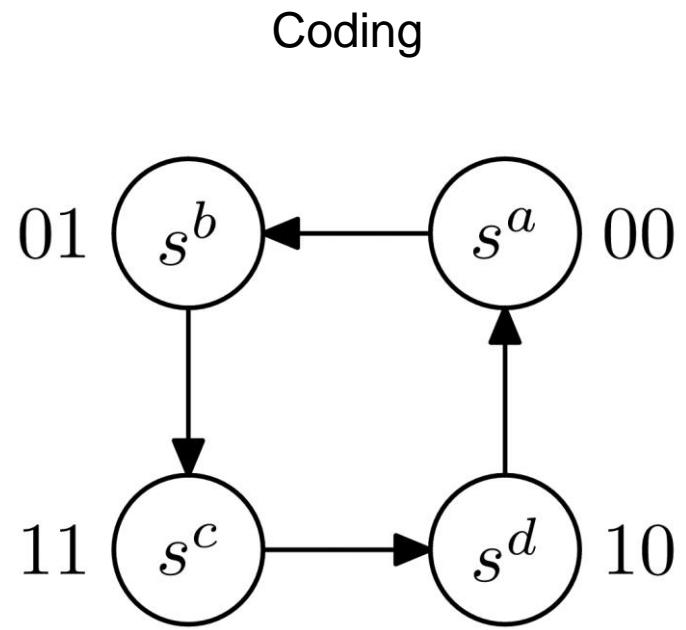

$x_g x_e$	00	01	11	10	y
$q_1 q_2$	00	(00)	01	(00)	00
	01	01	(11)	—	0
	11	—	10	(11)	1
	10	00	(10)	(10)	00
$q'_1 q'_2 / y$	00	01	11	10	

$$\begin{cases} q'_1 = q_2 x_g + q_1 x_e \\ q'_2 = q_2 x_g + \bar{q}_1 q_2 + \bar{q}_1 \bar{x}_g x_e \\ y = q_1 q_2 \end{cases}$$

$x_g x_e$

$q_1 q_2$	00	01	11	10
00	0	0	0	0
01	—	0	1	—
11	—	1	1	—
10	0	1	1	0

a'_1



$x_g x_e$

$q_1 q_2$	00	01	11	10
00	0	1	0	0
01	—	1	1	—
11	—	0	1	—
10	0	0	0	0

q'_2


SR-type static flip-flop

Q	\rightarrow	Q'	S	R
0	\rightarrow	0	0	-
0	\rightarrow	1	1	0
1	\rightarrow	0	0	1
1	\rightarrow	1	-	0

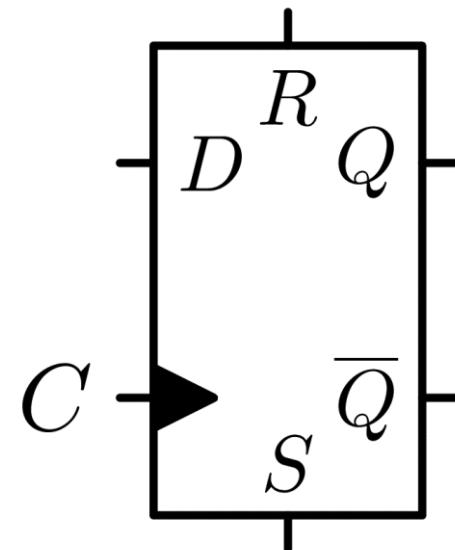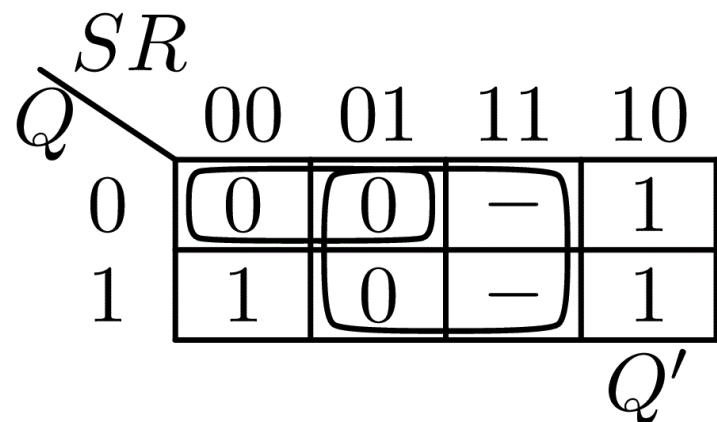The diagram shows a state transition table for the SR flip-flop. The inputs are Q and SR . The outputs are Q' and \bar{Q} . The table has four rows corresponding to the SR states: 00, 01, 11, and 10. The first three rows (00, 01, 11) correspond to the states shown in the truth table above. The fourth row (10) corresponds to the state where both S and R are high. In this state, the Q output is 1 and the \bar{Q} output is 0. The Q' output is also 1. The Q input is shown as a diagonal line, indicating it is the previous state.




Q	SR	Q'	\bar{Q}
0	00	0	1
0	01	0	1
1	11	-	-
1	10	1	0

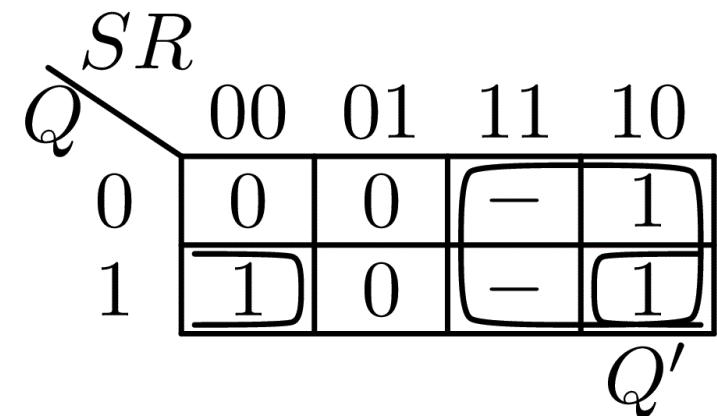




The diagram shows a state transition table for the SR flip-flop with different output assignments. The inputs are Q and SR . The outputs are Q' and \bar{Q} . The table has four rows corresponding to the SR states: 00, 01, 11, and 10. The first three rows (00, 01, 11) correspond to the states shown in the truth table above. The fourth row (10) corresponds to the state where both S and R are high. In this state, the Q output is 1 and the \bar{Q} output is 0. The Q' output is 0. The Q input is shown as a diagonal line, indicating it is the previous state.

Q	SR	Q'	\bar{Q}
0	00	0	1
0	01	0	1
1	11	-	-
1	10	0	1

$$Q' = S + \underbrace{QR}_{*}$$

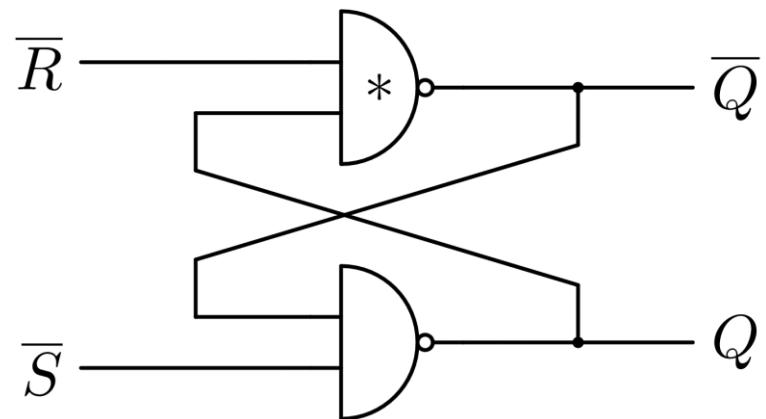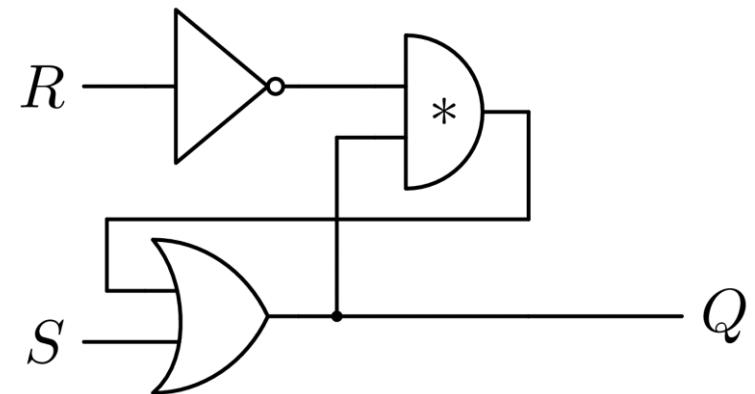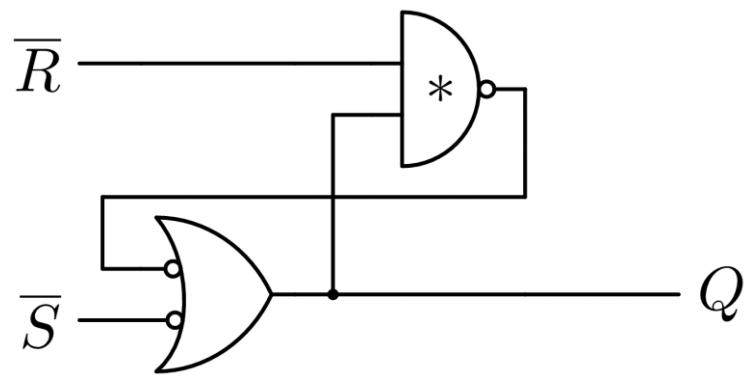
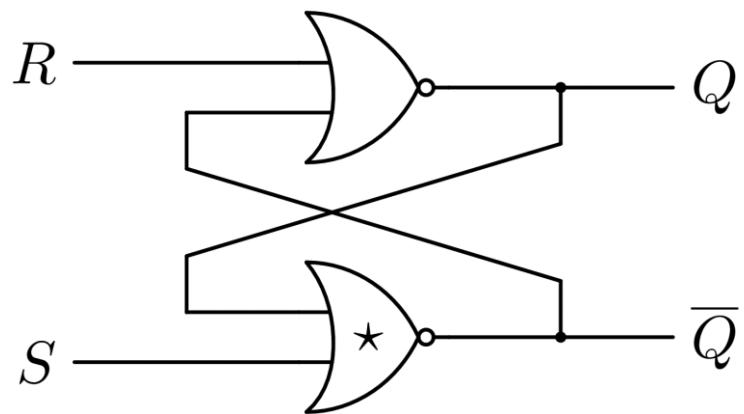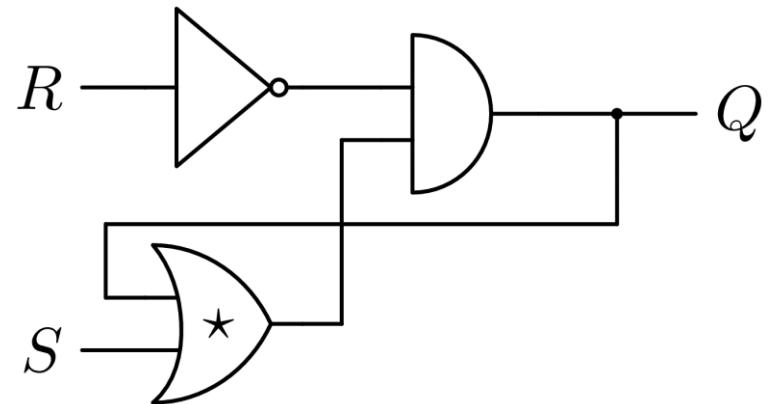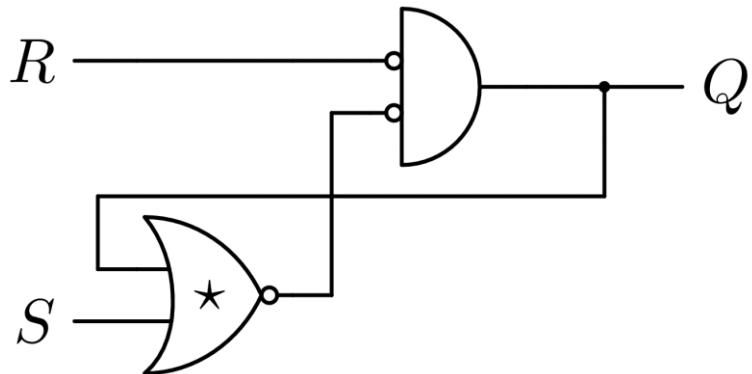
$$Q' = \overline{R} \underbrace{(Q + S)}_{*}$$



		$x_g x_e$	$q_1 q_2$	00	01	11	10
		$q_1 q_2$	00	0	0	0	0
		01	—	0	1	—	—
		11	—	1	1	—	—
		10	0	1	1	0	—
		q'_1	—	—	—	—	—

$$R_1 = \bar{x}_e$$

$$S_1 = q_2 x_g$$

		$x_g x_e$	$q_1 q_2$	00	01	11	10
		$q_1 q_2$	00	—	—	—	—
		01	—	—	0	—	—
		11	—	0	0	—	—
		10	1	0	0	1	—
		q'_1	—	—	—	—	—

		$x_g x_e$	$q_1 q_2$	00	01	11	10
		$q_1 q_2$	00	0	0	0	0
		01	—	0	1	—	—
		11	—	—	—	—	—
		10	0	—	—	0	—
		q'_1	—	—	—	—	—

$x_g x_e$	00	01	11	10	
$q_1 q_2$	00	0	1	0	0
	01	—	1	1	—
	11	—	0	1	—
	10	0	0	0	0

q'_2

$$R_2 = q_1 \bar{x}_g$$

$$S_2 = \bar{q}_1 \bar{x}_g x_e$$


$$y = q_1 q_2$$

$x_g x_e$	00	01	11	10	
$q_1 q_2$	00	—	0	—	—
	01	—	0	0	—
	11	—	1	0	—
	10	—	—	—	—


 R_2

$x_g x_e$	00	01	11	10	
$q_1 q_2$	00	0	1	0	0
	01	—	—	—	—
	11	—	0	—	—
	10	0	0	0	0

 S_2




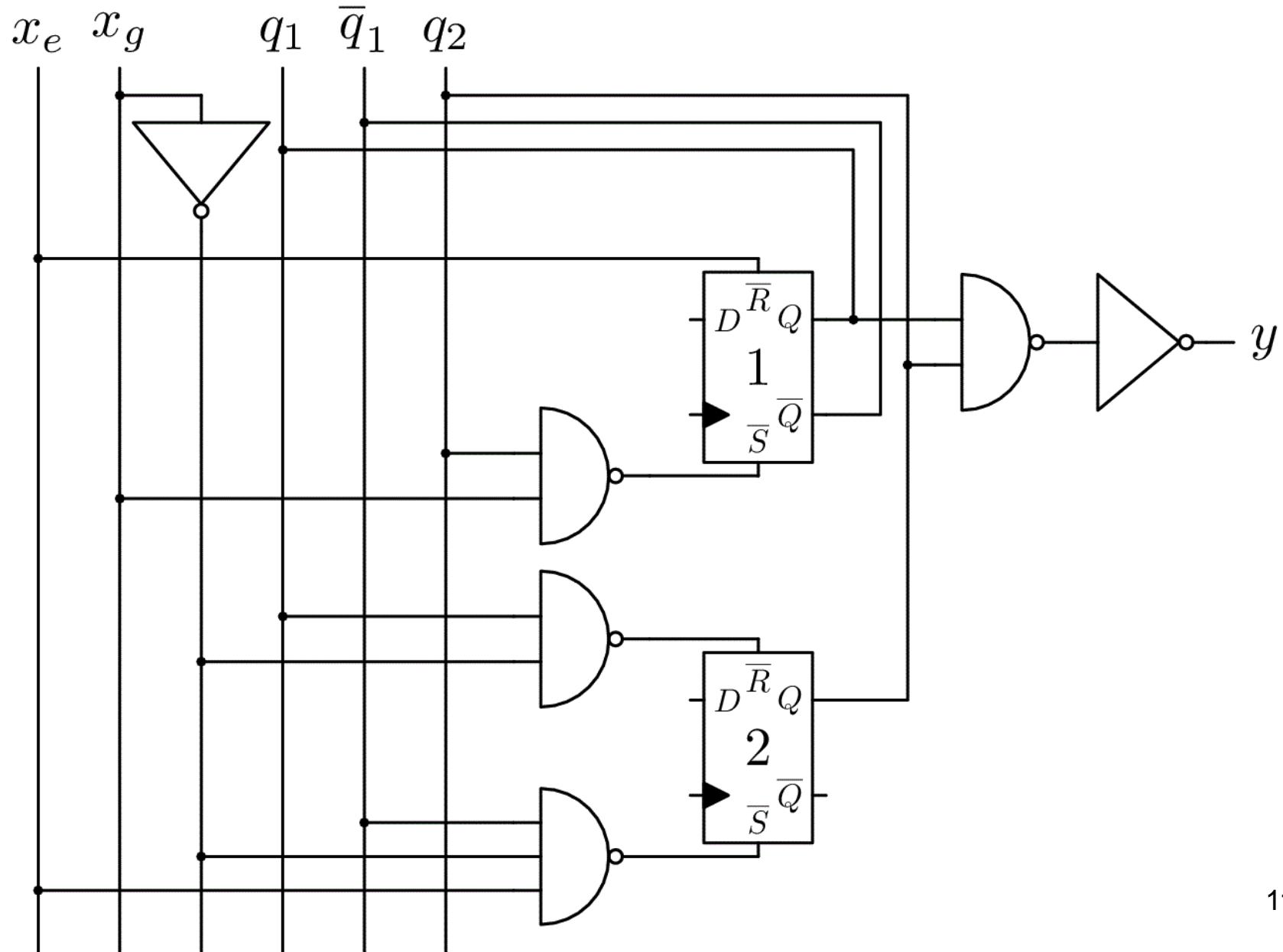


Parcel sorter

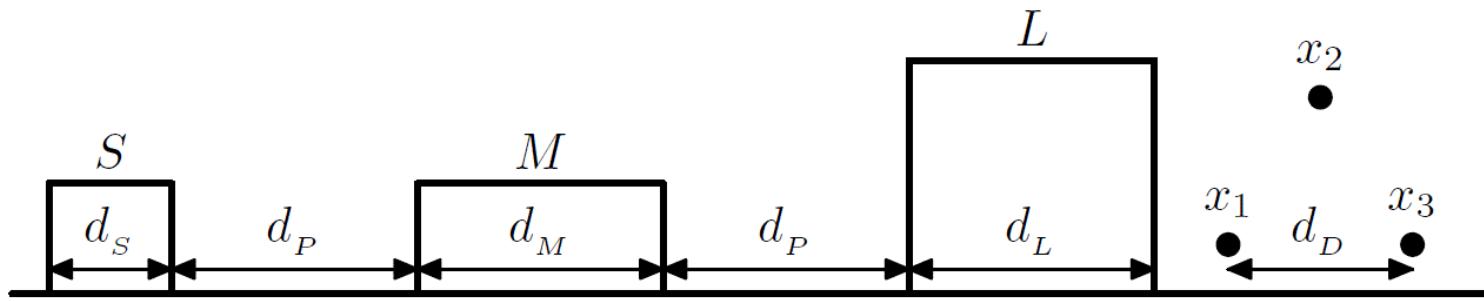


$$\begin{aligned}d_S &< d_D < d_M < d_L \\d_D &< d_P\end{aligned}$$

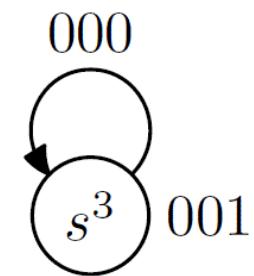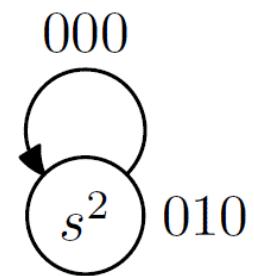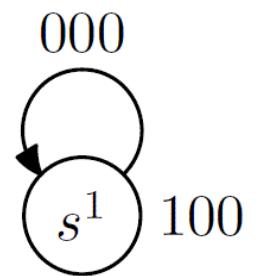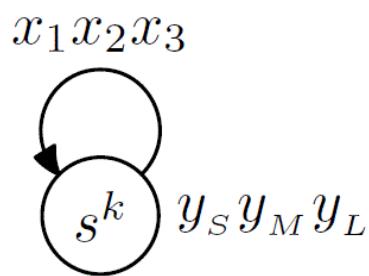
Initial situation - no parcel at the detecting station





A parcel crossing the first detector

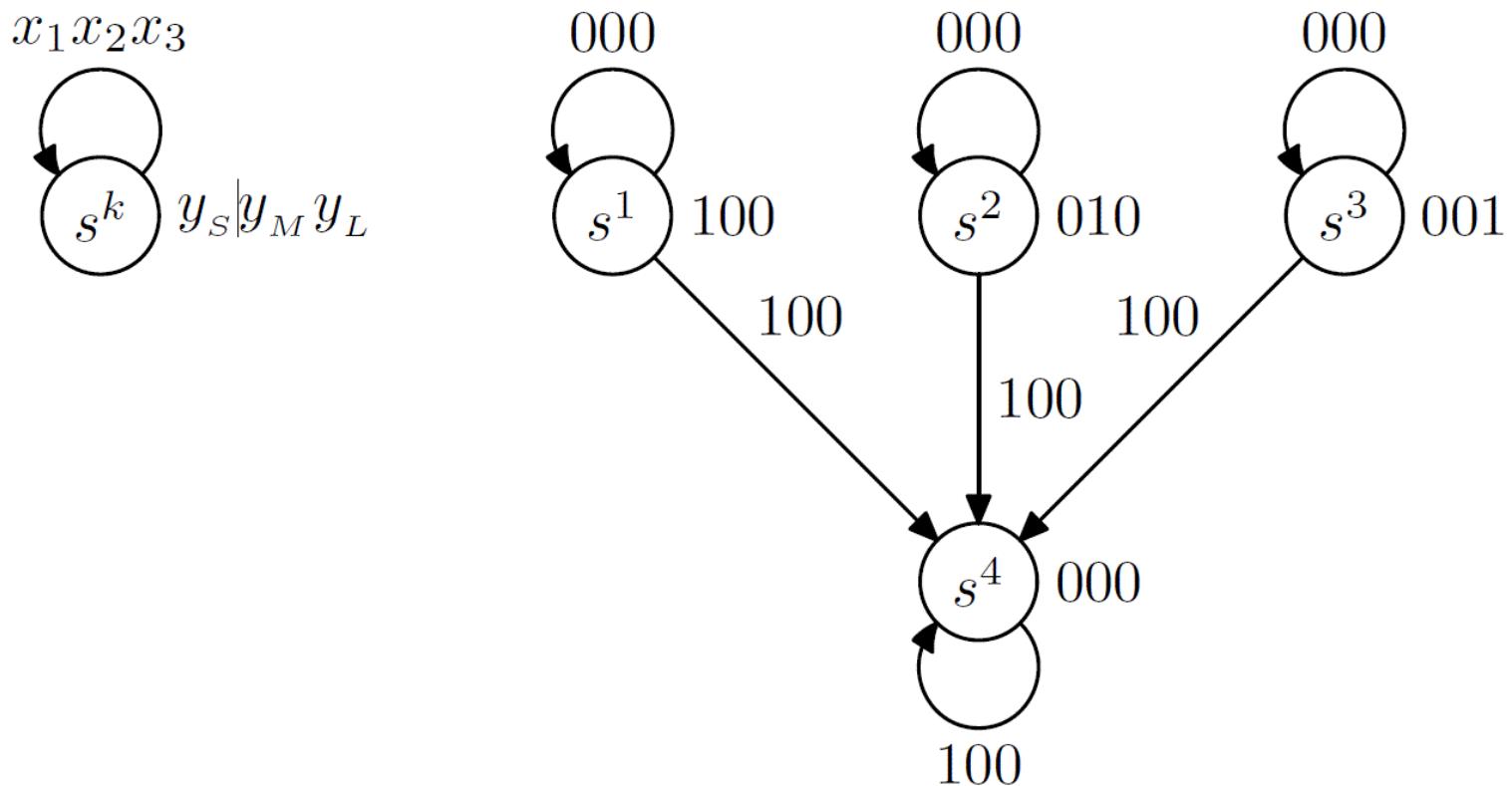


The case of a small parcell S

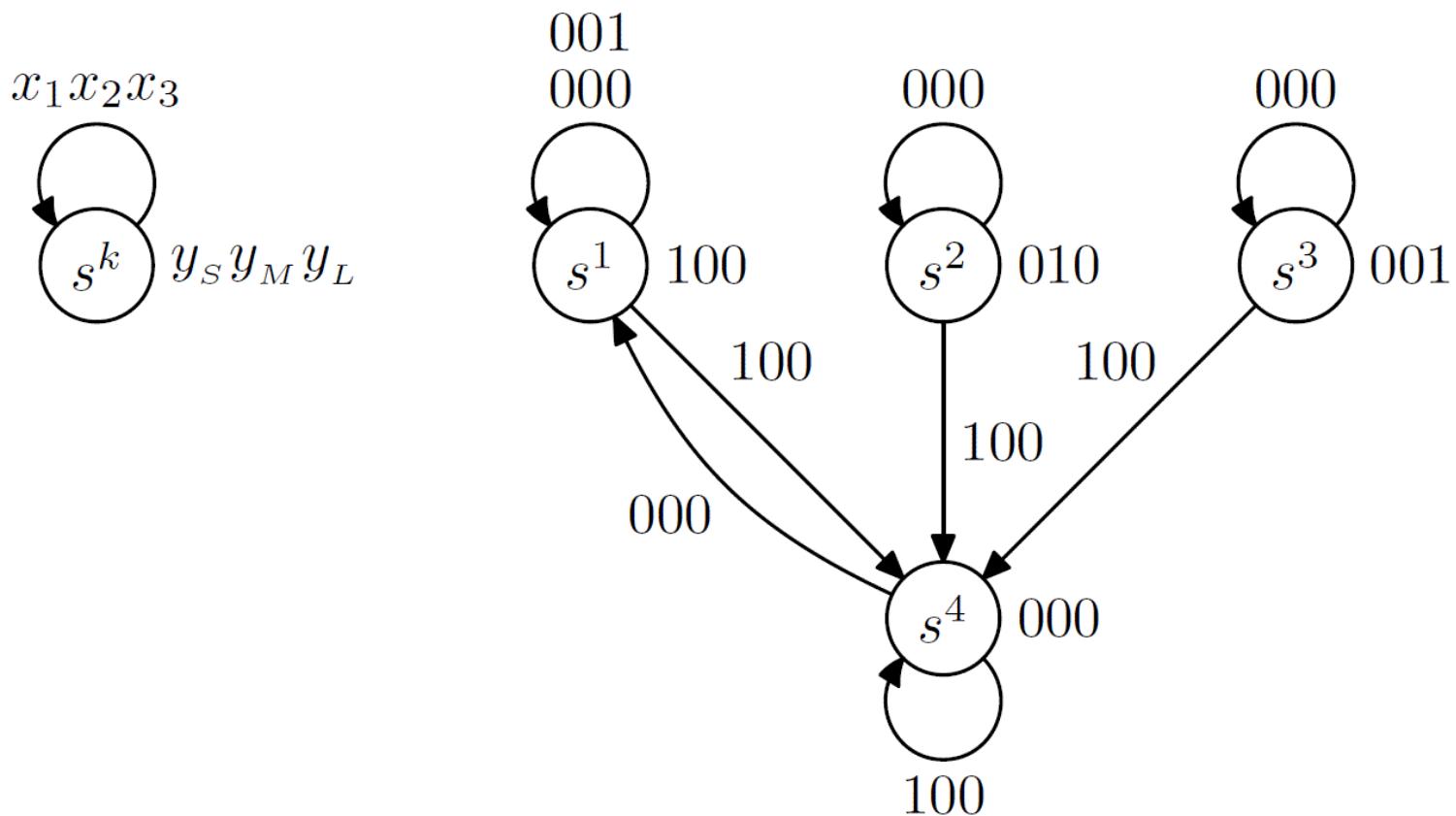

The case of a medium sized parcel M

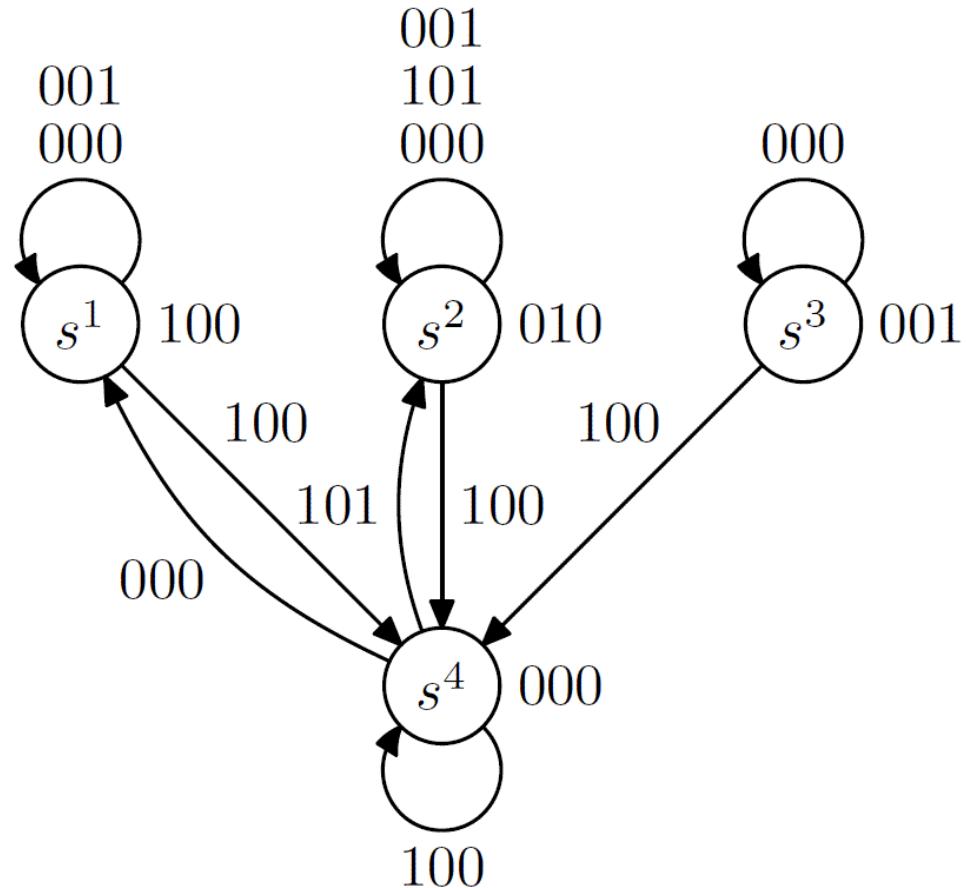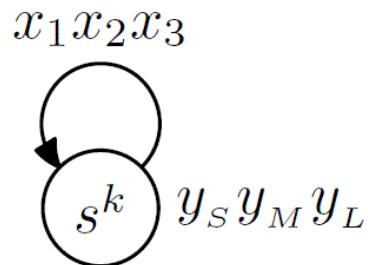

The case of a large parcel L

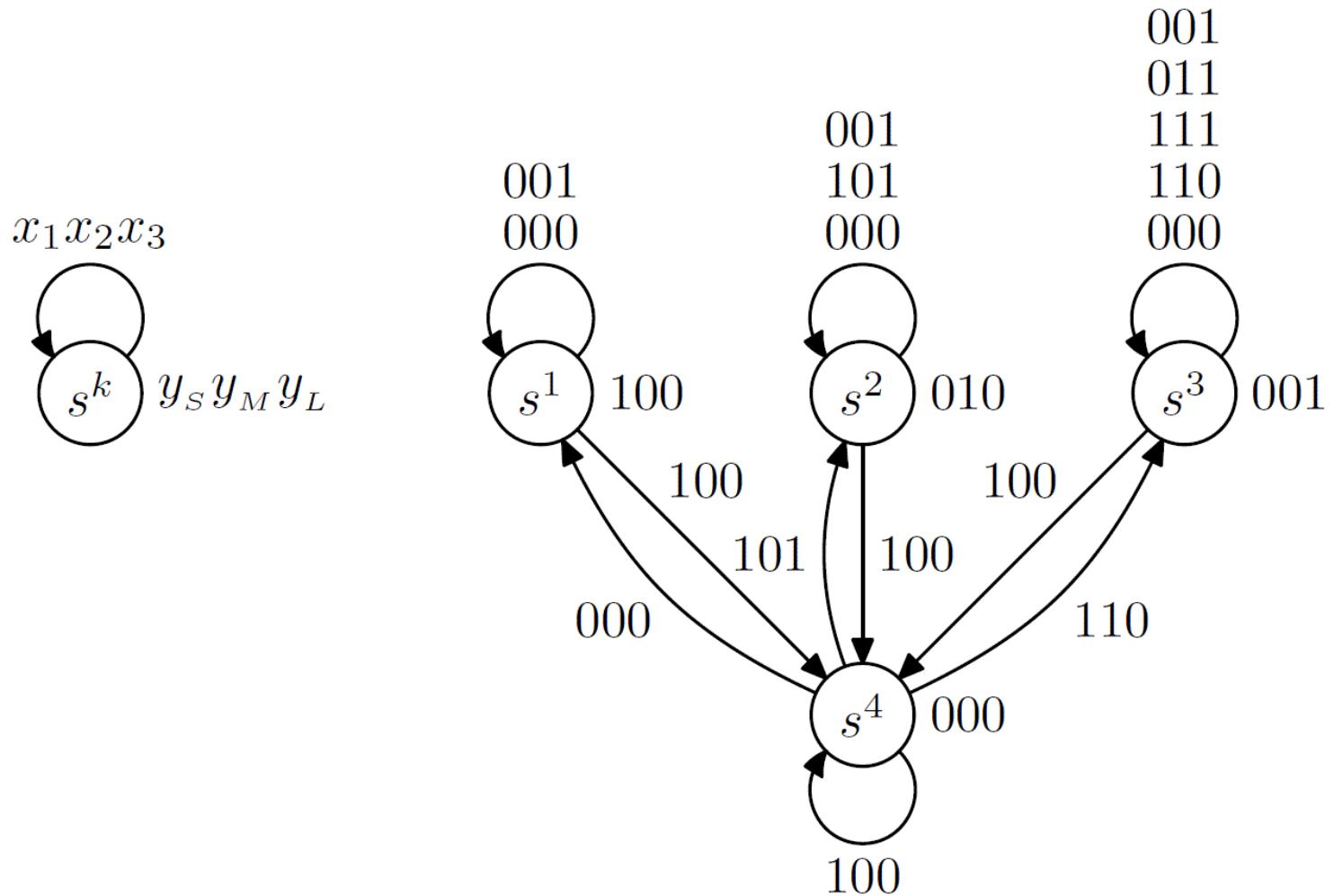


$x_1 x_2 x_3$	000	001	011	010	110	111	101	100	y_S	y_M	y_L
s											
s^1	(s^1)	(s^1)	—	—	—	—	—	s^4	1	0	0
s^2	(s^2)	(s^2)	—	—	—	—	(s^2)	s^4	0	1	0
s^3	(s^3)	(s^3)	(s^3)	—	(s^3)	(s^3)	—	s^4	0	0	1
s^4	s^1	—	—	—	s^3	—	s^2	(s^4)	0	0	0

s'/y

$x_1 x_2 x_3$	000	001	011	010	110	111	101	100	y_S	y_M	y_L
s											
s^1	(s^1)	(s^1)	—	—	—	—	s^2	s^4	1	0	0
s^2	(s^2)	(s^2)	—	—	—	—	(s^2)	s^4	0	1	0
s^3	(s^3)	(s^3)	(s^3)	—	(s^3)	(s^3)	s^2	s^4	0	0	1
s^4	s^1	—	—	—	s^3	—	s^2	(s^4)	0	0	0

s'/y

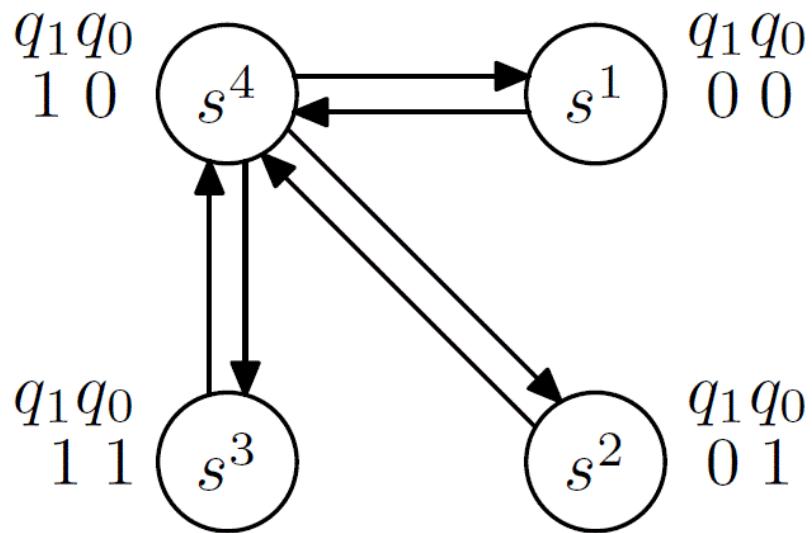

		$x_1 x_2 x_3$	000	001	011	010	110	111	101	100	y_s	y_M	y_L
$q_1 q_0$			00	00	-	-	-	-	01	10	1	0	0
	00	00	00	-	-	-	-	-	01	10	0	1	0
	01	01	01	-	-	-	-	-	01	10	0	1	0
	11	11	11	11	-	-	11	11	01	10	0	0	1
	10	00	-	-	-	-	11	-	01	10	0	0	0

 $q'_1 q'_0 / y$

		$x_1 x_2 x_3$	000	001	011	010	110	111	101	100
		$q_1 q_0$	00	01	11	10	110	111	101	100
q_1	q_0	00	0	0	—	—	—	—	0	1
00	00	0	0	—	—	—	—	—	0	1
01	01	0	0	—	—	—	—	—	0	1
11	11	1	1	1	—	1	1	0	1	
10	10	0	—	—	—	1	—	0	1	

q'_1

		$x_1 x_2 x_3$	000	001	011	010	110	111	101	100
		$q_1 q_0$	00	01	11	10	110	111	101	100
q_1	q_0	00	0	0	—	—	—	—	1	0
00	00	0	0	—	—	—	—	—	1	0
01	01	1	1	—	—	—	—	—	1	0
11	11	1	1	1	—	1	1	1	0	0
10	10	0	—	—	—	1	—	1	0	0

q'_0

	q_0	0	1
q_1	0	1	0
0	0	0	0
1	0	0	0

 y_S


	q_0	0	1
q_1	0	0	0
0	0	0	0
1	0	0	1

 y_L

	q_0	0	1
q_1	0	0	1
0	0	0	0
1	0	0	0

 y_M
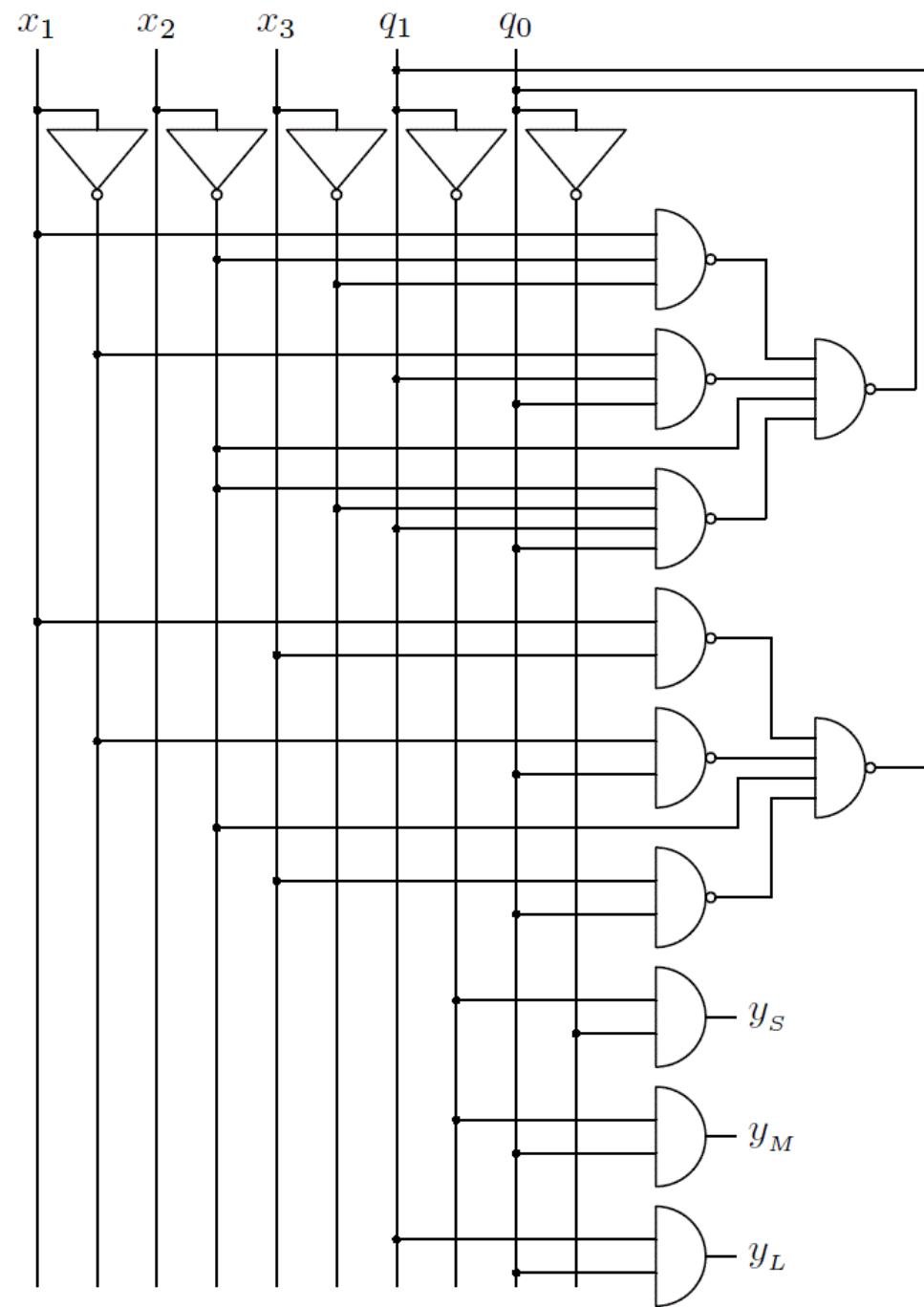
$$\left\{ \begin{array}{lcl} q'_1 & = & x_2 + x_1\bar{x}_2\bar{x}_3 + \bar{x}_1q_1q_0 + \bar{x}_2\bar{x}_3q_1q_0 \\ q'_0 & = & x_2 + x_1x_3 + \bar{x}_1q_0 + x_3q_0 \\ y_S & = & \bar{q}_1\bar{q}_0 \\ y_M & = & \bar{q}_1q_0 \\ y_L & = & q_1q_0 \end{array} \right.$$





WARSAW UNIVERSITY OF TECHNOLOGY
DEVELOPMENT PROGRAMME



HUMAN CAPITAL
HUMAN – BEST INVESTMENT!

EUROPEAN UNION
EUROPEAN
SOCIAL FUND



Project is co-financed by European Union within European Social Fund