

Problem Set 6

Problem 1. Determine the phasors corresponding to the following signals.


- a) $u(t) = 10 \sin(\omega t) \text{V}$
- b) $i(t) = 10 \cos(\omega t + \frac{\pi}{3}) \text{mA}$
- c) $u(t) = 5 \sin(\omega t + 60^\circ) \text{V}$
- d) $u(t) = 2 \text{V} \sin(\omega t - 30^\circ) + 3 \text{V} \cos \omega t$
- e) $i(t) = 12 \cos(\omega t - 12^\circ) \text{A}$

Problem 2. Determine alternating signals corresponding to the following phasors.

- a) $I = \text{jA}$
- b) $I = 6 - \text{j}8 \text{A}$
- c) $I = -6 - \text{j}8 \text{A}$
- d) $I = 12 \text{e}^{\text{j}10^\circ} \text{A}$
- e) $U = \frac{1}{\text{j}+1} \text{V}$
- f) $U = \text{j}^5 \text{V}$
- g) $U = \frac{1+\text{j}}{1-\text{j}} \text{V}$
- h) $U = 4 \text{e}^{\text{j}40^\circ} 2 \text{e}^{\text{j}5^\circ} \text{V}$

Problem 3. The voltage across a one-port, and the current through this one-port (oriented opposite with respect to the voltage) equal, respectively, $u(t) = 200 \sin(\omega t + 80^\circ) \text{V}$ and $i(t) = 10 \sin(\omega t + 20^\circ) \text{A}$. Find the impedance of this one-port.

Problem 4. Find the equivalent impedances of the following one-ports.

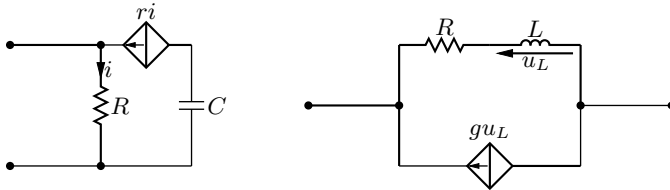

Problem 5. Determine current $i(t)$ in the following circuit.

$e(t) = -6\text{V} \sin \omega t$, $j_1(t) = 12\text{mA} \cos \omega t$, $R_1 = 2\text{k}\Omega$, $R_2 = 1\text{k}\Omega$, $L = 12\text{mH}$, $C = 1\text{nF}$, $\omega = \frac{1}{3}\text{Mrad/s}$.

