

Circuits and Signals

Non-linear circuits

Marek Rupniewski

2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY


Non-linear circuit

Definition

Non-linear circuit is a circuit, in which there is at least one non-linear device.

Non-linear resistor

resistor (linear):

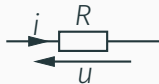

$$u = Ri.$$

non-linear resistor:



$$u = f(i),$$


f is non-linear function, whose graph lies in 1 i 3 quadrants and crosses the origin of coordinates i - u . alternatively:

$$i = g(u),$$

where g is non-linear function, whose graph lies in 1 i 3 quadrants and crosses the origin of coordinates u - i .

Non-linear resistor — cont.



example:

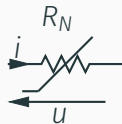


$$u = \underbrace{\alpha(\operatorname{sgn} i)\sqrt{|i|}}_{f(i)},$$

$$\alpha > 0$$
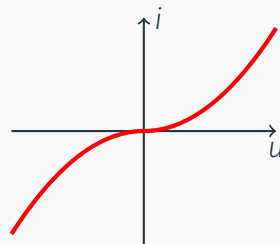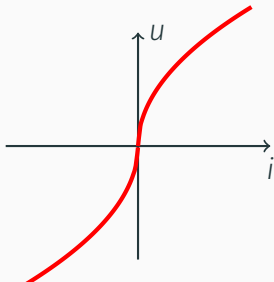
$$i = \underbrace{(\operatorname{sgn} u)(u/\alpha)^2}_{g(i)}.$$



Non-linear capacitor — (revisited)

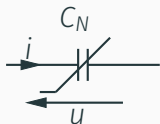


$$\boxed{q = q(u)} \quad \text{lin. case: } q = Cu$$

$$i(t) = q'(t) = \frac{dq}{du} \frac{du}{dt}(t) = \frac{dq(u(t))}{du} u'(t).$$

The graph of q lies in 1 i 3 quadrants and crosses the origin of coordinates u - q .

Non-linear inductor — (revisited)


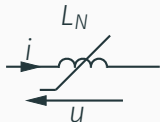


$$\boxed{\psi = \psi(i)} \quad \text{lin. case: } \psi = Li$$


$$u(t) = \psi'(t) = \frac{d\psi}{di} \frac{di}{dt}(t) = \frac{d\psi(i(t))}{di} i'(t).$$

The graph of ψ lies in 1 i 3 quadrants and crosses the origin of coordinates i - ψ .

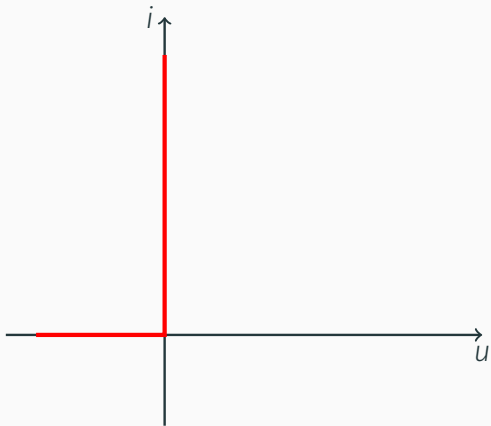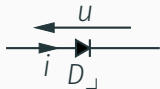
Diode — basic (short-/open- circuit) model





FET transistor as a switch

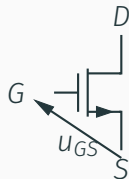


Load line method (DC case)

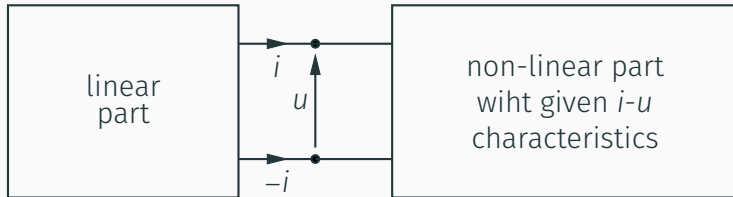


Load line method (DC case)

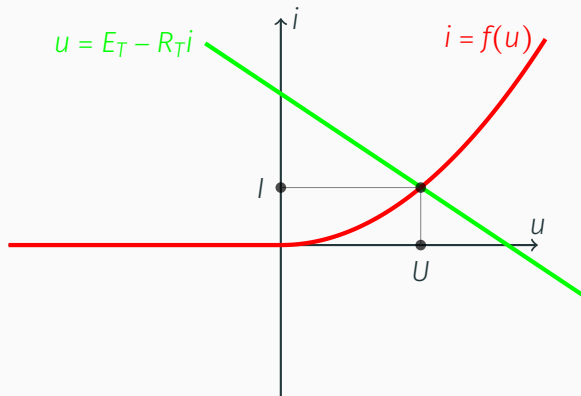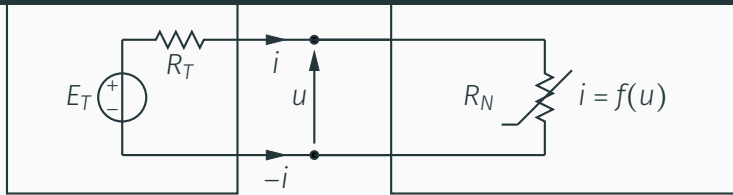


Composing the characteristics

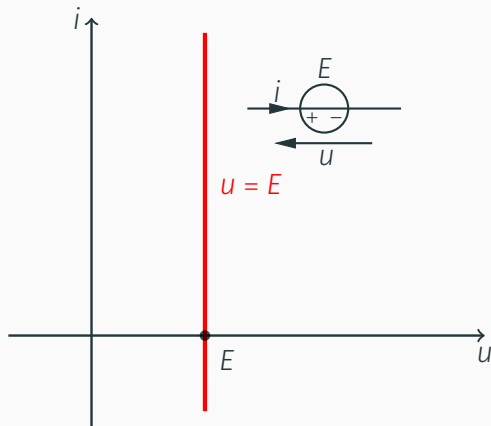


Composing the characteristics

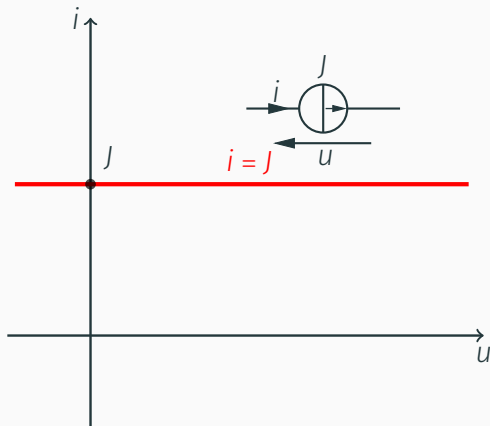


Composing the characteristics

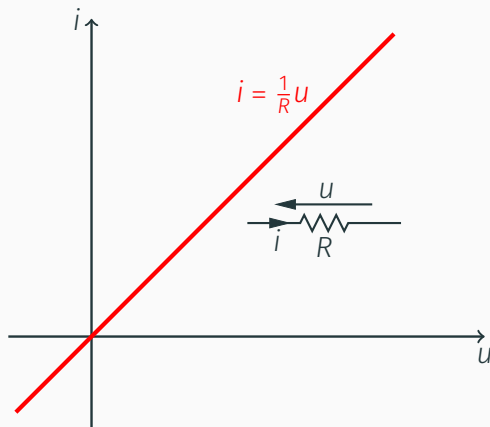

Composing the characteristics

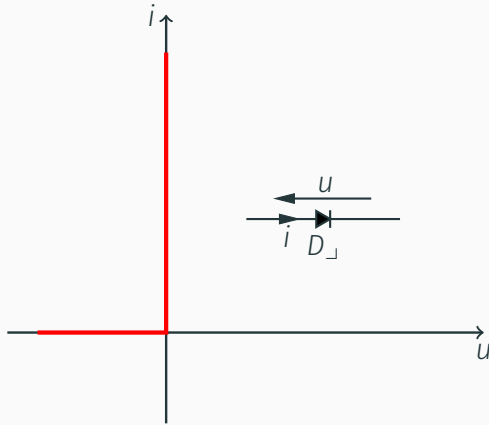



Composing the characteristics

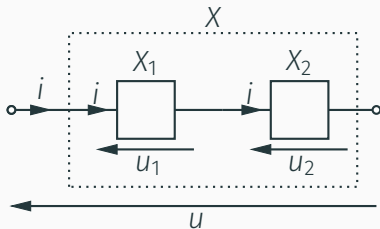



The current through individual one-ports is the current through combined one-port and

$$u = u_1 + u_2$$


Composing the characteristics

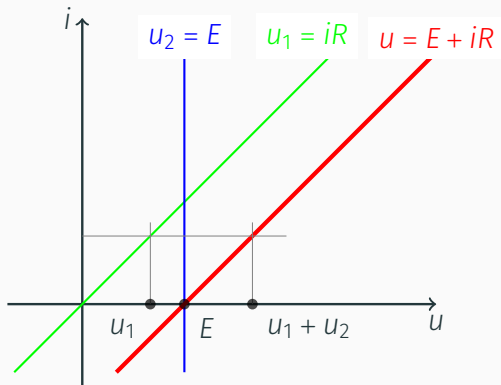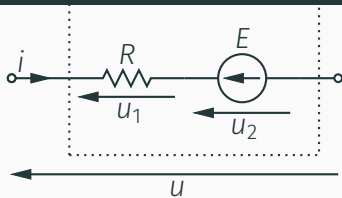

Composing the characteristics

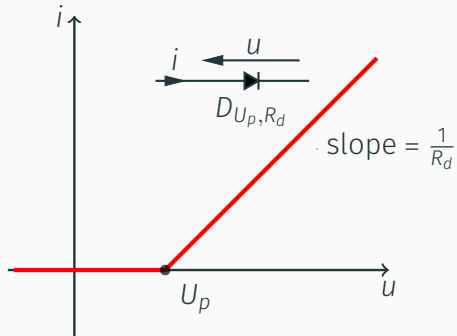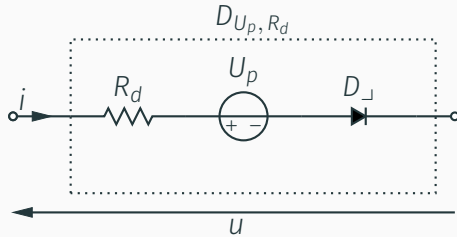



Composing the characteristics

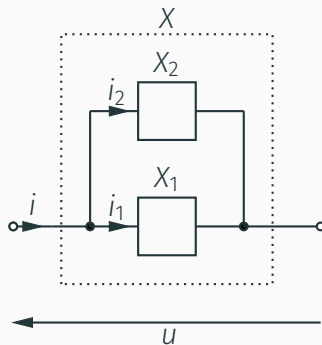


Voltage across the combined one-port equal voltages across individual one-ports and

$$i = i_1 + i_2.$$



Composing the characteristics

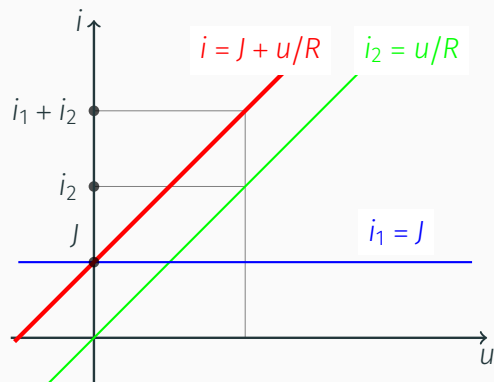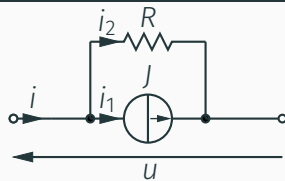



Full-wave rectifier — introduction

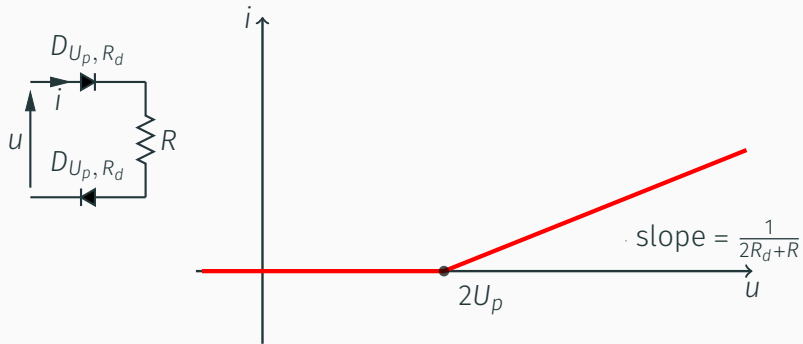



Full-wave rectifier — introduction

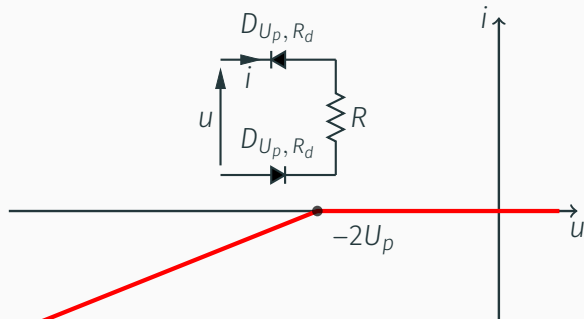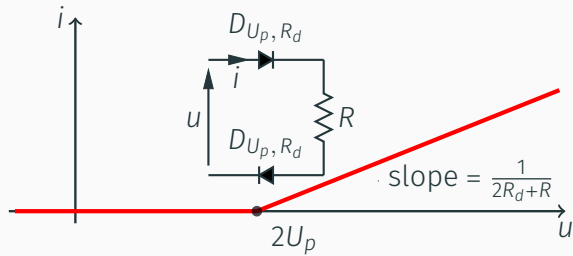


Full-wave rectifier

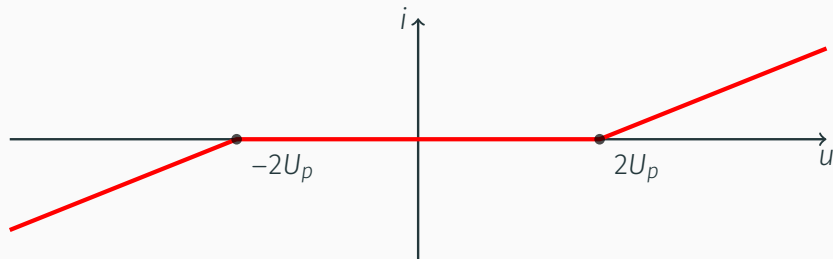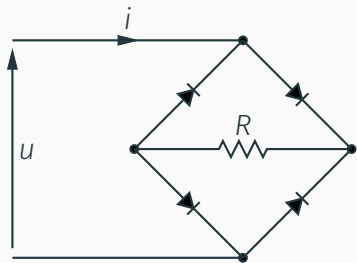


Full-wave rectifier

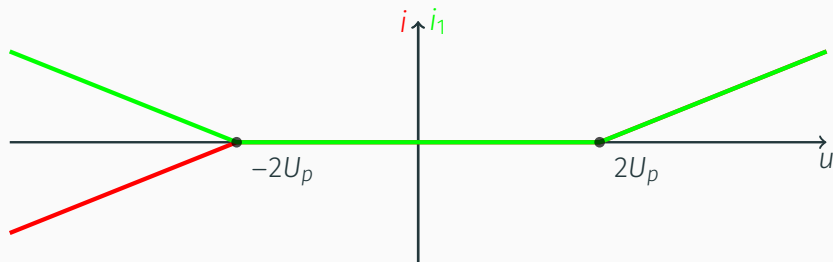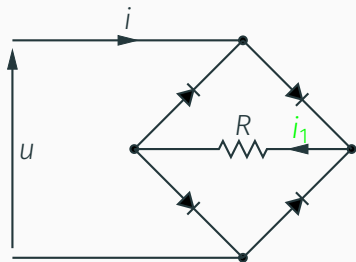



Projection through a characteristics

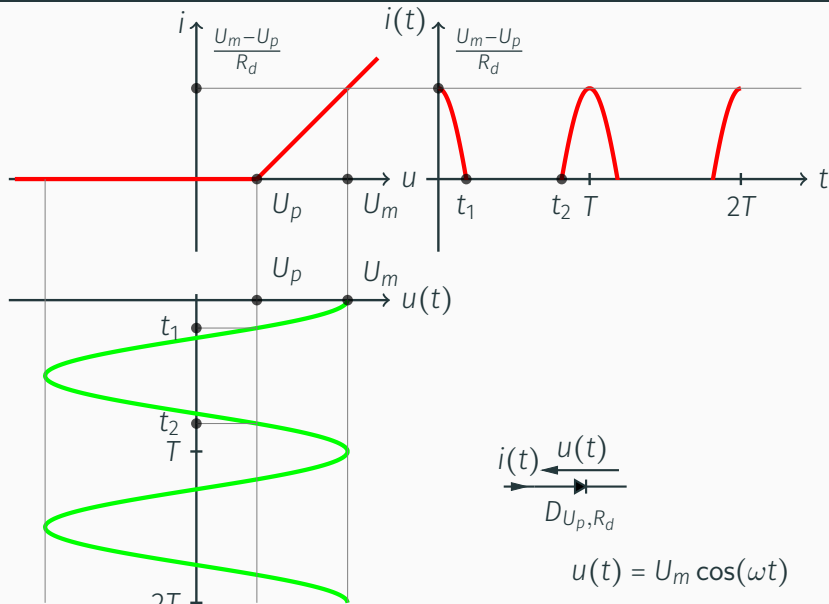

Projection — full-wave rectifier

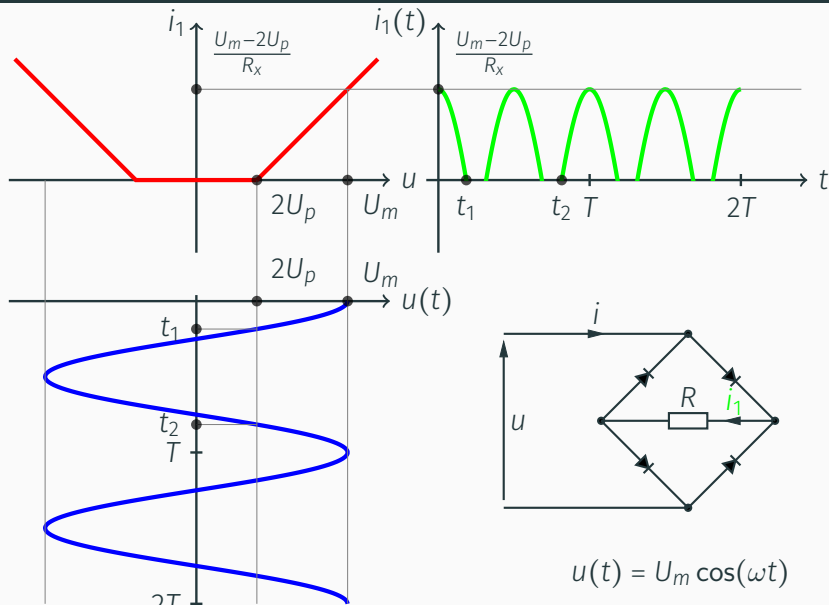

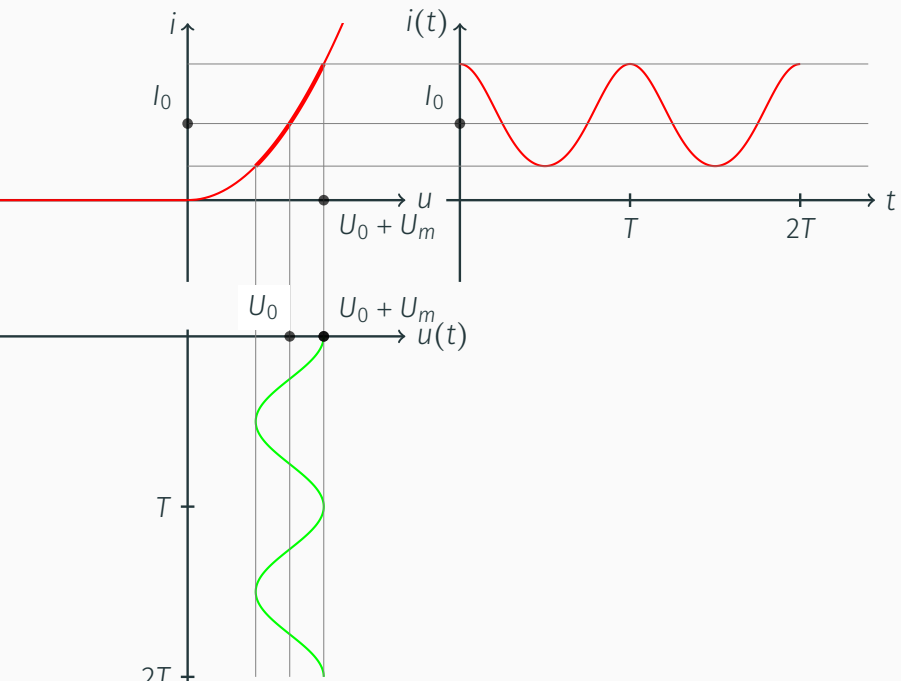

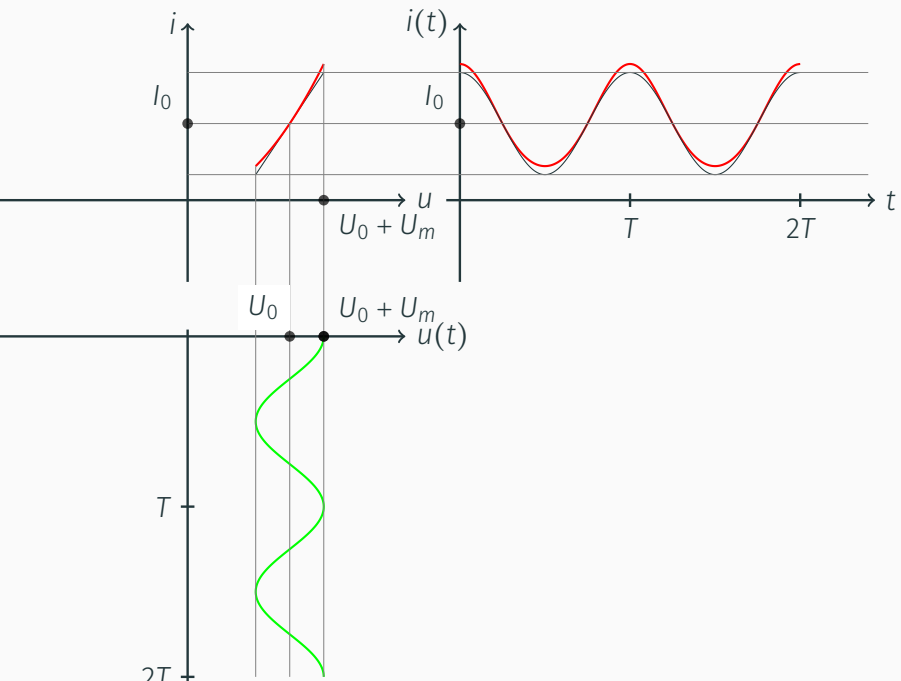



Small-signal method

Small-signal method is a method of approximation of the solution to a non-linear circuit by the sum of:

- DC solution of the original non-linear circuit (with all time-varying signals reduced to zero),
- periodic solution (can be harmonic in particular case) to a **linear** circuit that is obtained through linearization (around the DC solution) of the original circuit and reducing the DC components to zero.

The smaller are non-DC components of the signals, the better is the approximation obtained.

Small-signal analysis

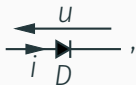
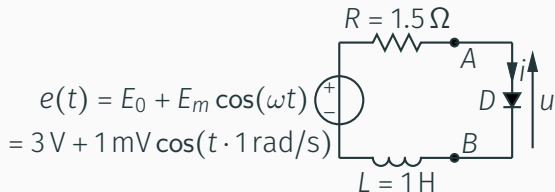


$$i = f(u) = \begin{cases} 0 & \text{if } u < 0, \\ \frac{u^2}{\alpha} & \text{if } u \geq 0, \end{cases} \quad \alpha = \frac{9}{2} \text{ V } \Omega.$$

$$i = ?, \quad u = ?$$


$$i(t) \approx I_0 + I_m \cos(\omega t + \psi), \quad u(t) \approx U_0 + U_m \cos(\omega t + \phi).$$

Small-signal analysis

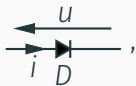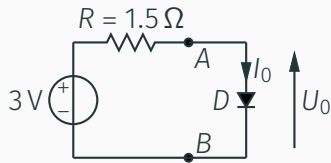



$$i = f(u) = \begin{cases} 0 & \text{if } u < 0, \\ \frac{u^2}{\alpha} & \text{if } u \geq 0, \end{cases} \quad \alpha = \frac{9}{2} \text{V}\Omega.$$

$i = ?$, $u = ?$

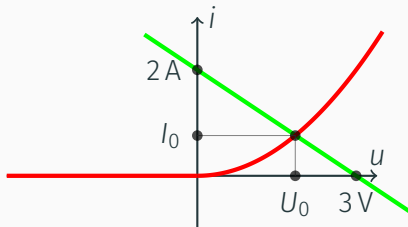

$$U_0 \approx 1.9\text{V}, \quad I_0 \approx 0.8\text{A}.$$


Small-signal analysis

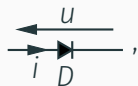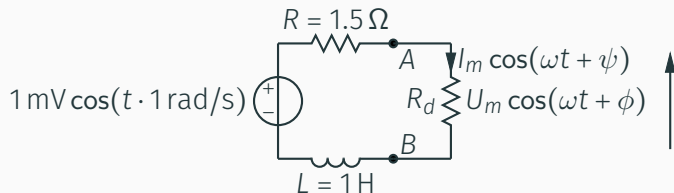

$$i = f(u) = \begin{cases} 0 & \text{if } u < 0, \\ \frac{u^2}{\alpha} & \text{if } u \geq 0, \end{cases} \quad \alpha = \frac{9}{2} \text{ V } \Omega.$$

$$R_d = \frac{1}{f'(U_0)} = \frac{\alpha}{2U_0} \approx 1.2 \Omega.$$

Small-signal analysis

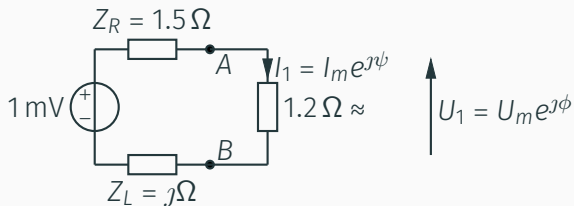

$$I_1 = \frac{E_m}{R + R_d + j\omega L} \approx (0.3 - j0.1) \text{ mA} \approx 0.3 e^{-j0.4} \text{ mA}.$$









From Ohm's law:

$$U_1 = R_d I_1 \approx 0.4 e^{-j0.4} \text{ mV}.$$

$$i(t) \approx 0.8 \text{ A} + 0.3 \cos(\omega t - 0.4) \text{ mA},$$

$$u(t) \approx 1.9 \text{ V} + 0.4 \cos(\omega t - 0.4) \text{ mV}.$$

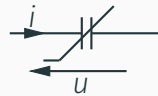One-ports linearization

one-port	linearization	formula
$R_N: i = f(u)$ 		$R_d = \frac{1}{f'(U_0)}$
$R_N: u = g(i)$ 		$R_d = g'(I_0)$
$C_N: q = f(u)$ 		$C_d = f'(U_0)$
$L_N: \psi = f(i)$ 		$L_d = f'(I_0)$

Example

Find $i(t)$. $e(t) = E_0 + E_1 \cos \omega t$, $E_0 = 1\text{ V}$, $E_1 = 22\text{ mV}$, $R = 1\text{ k}\Omega$, $L = 4\text{ mH}$,
 L_N : $\psi(i) = l_0 i + \alpha i^2$, $l_0 = 4\text{ mH}$, $\alpha = -\frac{1}{2}\text{ Wb/A}^2$, $\omega = 1\text{ Mrad/s}$.

