

Circuits and Signals

Equivalent devices

Marek Rupniewski

2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY


Equivalent devices

Devices are called equivalent if they are governed by equivalent equations.


Equivalent devices

In DC case

short-circuit

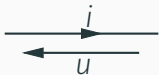


resistor $R = 0$

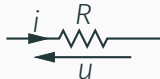

$$u = 0$$

source $e = 0$

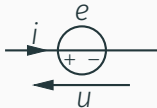


inductor




$$i = 0$$


open-circuit

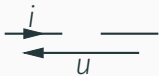


resistor $G = 0$
($R = \infty$)

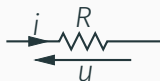

source $j = 0$

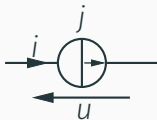


capacitor

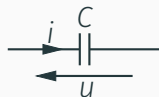

Series connections of one-ports

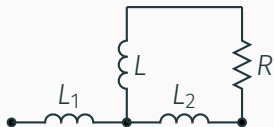Two one-ports are said to be connected in a series if and only if they have exactly one common terminal and no other device is connected to that terminal.



Resistor R and inductor L do form a series connection.


Inductors L_1 and L_2 do not form a series connection.

Series connections of resistors




The diagram illustrates the equivalence between a series connection of resistors and a single equivalent resistor. On the left, a series chain of resistors R_1, R_2, \dots, R_n is shown. This is followed by an equivalence symbol \equiv and a single resistor labeled R_{eq} . The equation $R_{eq} = R_1 + \dots + R_n$ is written above the equivalent resistor.
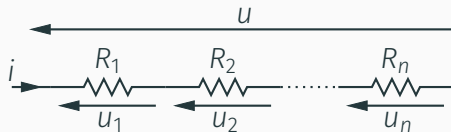
$$R_1 \text{ --- } R_2 \text{ --- } \dots \text{ --- } R_n \equiv \text{ --- } R_{eq} \text{ ---}$$
$$R_{eq} = R_1 + \dots + R_n$$



$$u \stackrel{\text{KVL}}{=} u_1 + \dots + u_n \stackrel{u_k = R_k i}{=} i \underbrace{(R_1 + R_2 + \dots + R_n)}_{R_{eq}}$$


Series connections of voltage sources

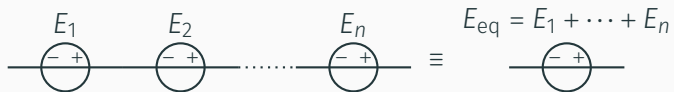


Series connections of inductors

$$\text{---} \overset{L_1}{\text{⏟}} \text{---} \overset{L_2}{\text{⏟}} \text{---} \text{.....} \text{---} \overset{L_n}{\text{⏟}} \text{---} \equiv L_{\text{eq}} = L_1 + \cdots + L_n \text{---} \text{⏟} \text{---}$$

Series connections of capacitors

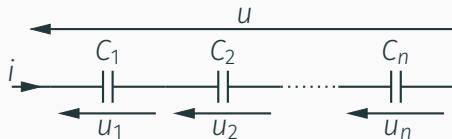
$$C_1 \quad C_2 \quad \dots \quad C_n \equiv \quad \text{---} \parallel \text{---}$$
$$C_{\text{eq}} = \left(\frac{1}{C_1} + \dots + \frac{1}{C_n} \right)^{-1}$$



$$u' \stackrel{\text{KVL}}{=} u'_1 + \dots + u'_n \stackrel{i=C_k u'_k}{=} i \left(\frac{1}{C_1} + \dots + \frac{1}{C_n} \right)$$


$$i = \underbrace{\left(\frac{1}{C_1} + \dots + \frac{1}{C_n} \right)^{-1}}_{C_{\text{eq}}} u'.$$

Series connections of current sources



Parallel connections of one-ports


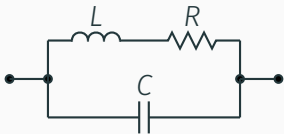
Two or more one-ports form a parallel connection if and only if there exist two distinct nodes that are terminals of each of the one-ports.



One-ports L and C **do not** form a parallel connection.

The capacitor is parallel connected with one-port that is a series connection of L and R .


Parallel connections of resistors

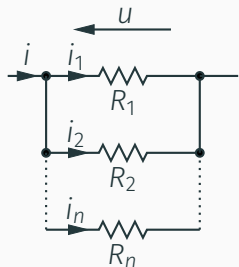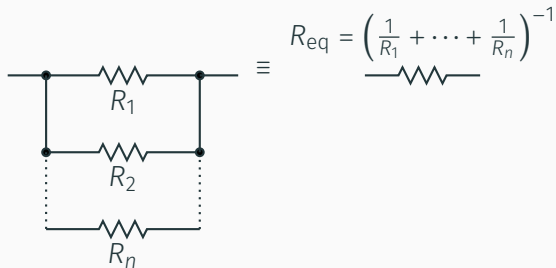


$$i \stackrel{\text{KCL}}{=} i_1 + \dots + i_n \stackrel{u=R_k i_k}{=} u \left(\frac{1}{R_1} + \dots + \frac{1}{R_n} \right)$$

$$u = \underbrace{\left(\frac{1}{R_1} + \dots + \frac{1}{R_n} \right)^{-1}}_{R_{eq}} i.$$


Parallel connections of 2 resistors

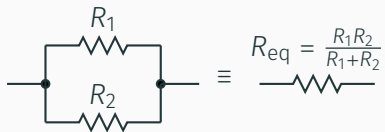



Parallel connections of inductors

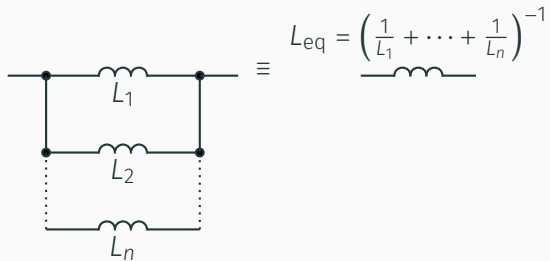

Parallel connections of current sources

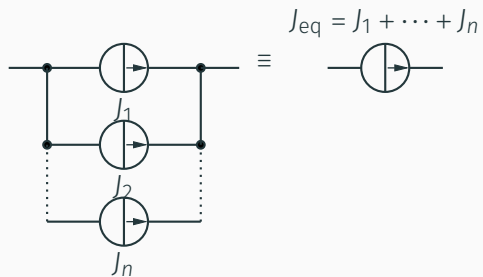


Parallel connections of capacitors

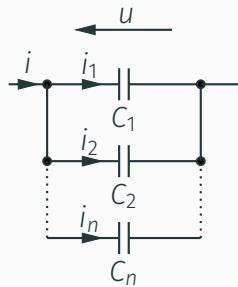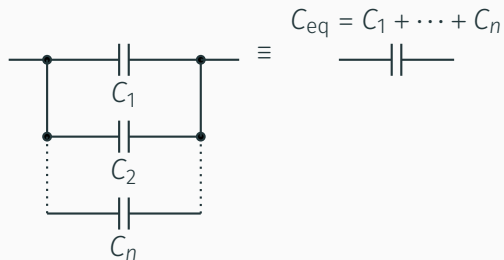

$$i \stackrel{\text{KCL}}{=} i_1 + \dots + i_n$$

$$i_k = C_k u' \stackrel{=}{=} \underbrace{(C_1 + \dots + C_n)}_{C_{\text{eq}}} u'$$

Parallel connections of voltage sources

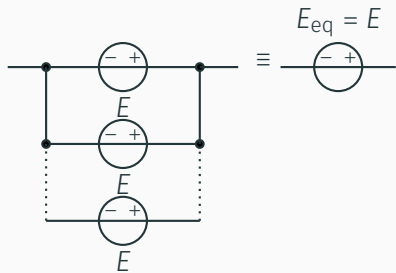

One-port connections — reordering

