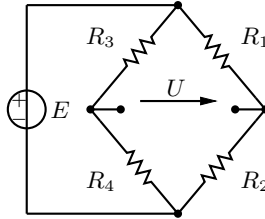



## Problem Set 3

**Problem 1.** Find voltage  $U$ .




*Answer.*  $U = E \left( \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$ .

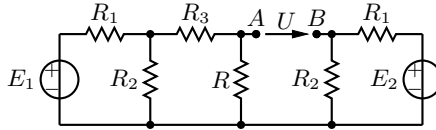**Problem 2.** Find the value of  $R$  for which  $U = 0$ . Use the voltage divider formula. The following data is given:  $E_1 = 15\text{ V}$ ,  $E_2 = 4\text{ V}$ ,  $R_1 = 2\text{ k}\Omega$ ,  $R_2 = 6\text{ k}\Omega$ ,  $R_3 = 4\text{ k}\Omega$ .




*Answer.*  $R = 2\text{ k}\Omega$ .

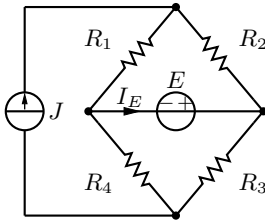**Problem 3.** Using superposition rule, find current  $I_E$ . Give the conditions under which  $I_E = 0$ .





*Answer.*  $I_E = E \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} \right) + J \left( \frac{R_2}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$ .  $I_E = 0$  if  $E = J \frac{R_1 R_3 - R_2 R_4}{R_1 + R_2 + R_3 + R_4}$ .

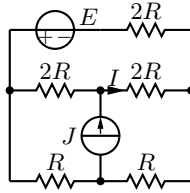**Problem 4.** Using superposition rule find current  $I$ . The following data is given:  $E = 24\text{ V}$ ,  $J = 1.2\text{ A}$ ,  $R = 1\ \Omega$ .



*Answer.*  $I = \frac{J}{2} + \frac{E}{10R}$ .

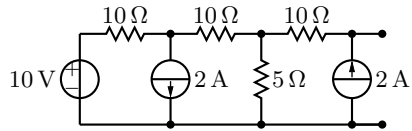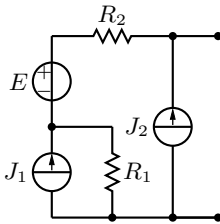**Problem 5.** Using superposition rule find voltages across the following 1-ports.



*Answer.*  $E + J_2(R_1 + R_2) + J_1R_1$ ,  $26\text{ V}$ .