

Circuits and Signals

Power and Energy

Marek Rupniewski


2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

Instantaneous power

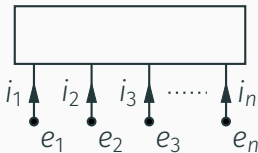



Instantaneous power delivered to an n -terminal device:

$$p(t) = e_1(t)i_1(t) + \cdots + e_n(t)i_n(t).$$

Instantaneous power generated by a device:


$$p_{\text{gen}}(t) = -p(t).$$

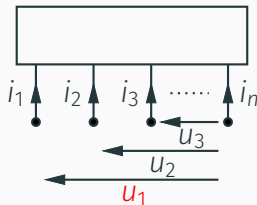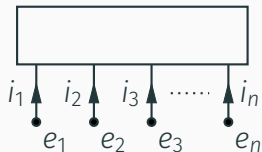Instantaneous power — current-voltage definition




$$\begin{aligned}
 p(t) &= e_1(t)i_1(t) + \cdots + e_{n-1}(t)i_{n-1}(t) + e_n(t)\mathbf{i}_n(t) \\
 &= e_1(t)i_1(t) + \cdots + e_{n-1}(t)i_{n-1}(t) + e_n(t)(-\mathbf{i}_1 - \mathbf{i}_2 - \cdots - \mathbf{i}_{n-1})(t) \\
 &= i_1(t) \underbrace{(e_1 - e_n)}_{\mathbf{u}_1}(t) + i_2(t) \underbrace{(e_2 - e_n)}_{u_2}(t) + \cdots + i_{n-1}(t) \underbrace{(e_{n-1} - e_n)}_{u_{n-1}}(t) \\
 &= i_1(t)u_1(t) + i_2(t)u_2(t) + \cdots + i_{n-1}(t)u_{n-1}(t).
 \end{aligned}$$

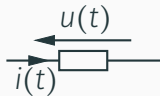Instantaneous power delivered to one-ports



$$p(t) = u(t)i(t).$$

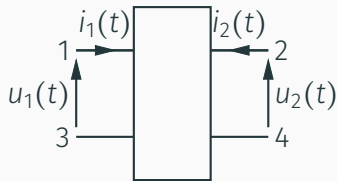Instantaneous power delivered to two-ports



$$p(t) = (e_1 i_1 + e_3 (-i_1) + e_2 i_2 + e_4 (-i_2))(t)$$

$$= u_1(t) i_1(t) + u_2(t) i_2(t).$$


Tellegen's Theorem

Tellegen's Theorem

The total sum of instantaneous powers delivered to all the device comprising a circuit equals zero.

Proof of Tellegen's Theorem


a complicated circuit:

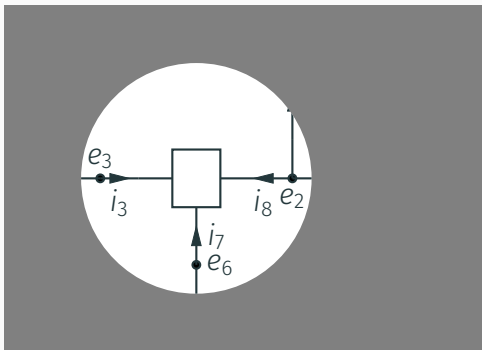

The sum of instantaneous powers is the sum of all the products $e_k i_l$, where e_k is a node's potential and i_l is a current diverging from that node (and flowing into a terminal of some device). Every potential of a node is multiplied by the sum of all the currents diverging from that node

Proof of Tellegen's Theorem


a complicated circuit:

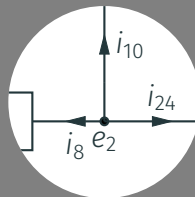


Every potential of a node is multiplied by the sum of all the currents diverging from that node which (the sum) is zero by KCL.

$$p = \cdots + e_2(i_8 + i_{10} + i_{24}) + \cdots$$

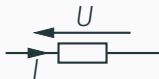
Power delivered to one-port in DC circuits — examples



$$P = UI.$$

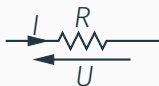
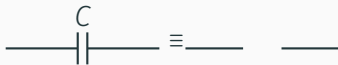
$$P = UI \stackrel{U=RI}{=} I^2 R = \frac{U^2}{R}.$$




$$P = 0.$$



$$P = 0.$$

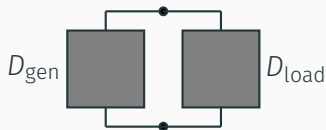
Maximum Power Transfer (MPT) Theorem — introduction




assumption: D_{gen} is fixed (we cannot change it).

For what one-port D_{load} the power delivered to D_{load} is maximal?


MPT Theorem — restrictions

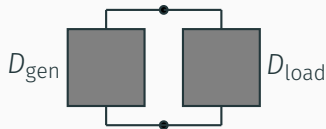


We may restrict the problem to:

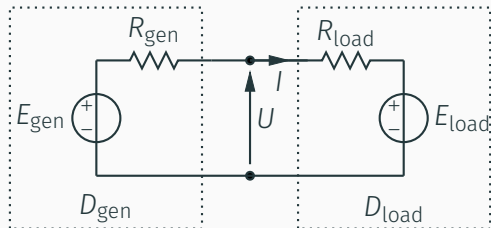

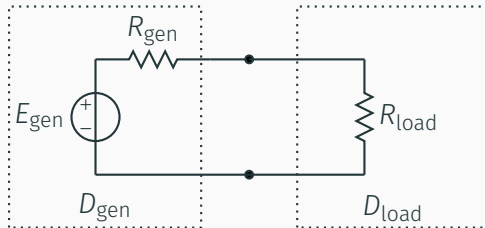From an engineer's viewpoint,
the most important case is:



Maximum Power Transfer Theorem (DC case)

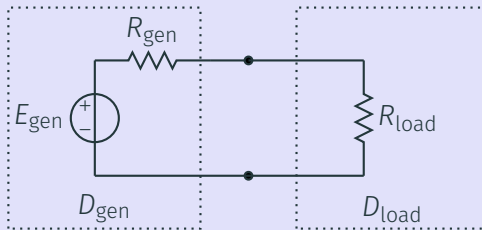


If $E_{\text{gen}} \neq 0$ and $R_{\text{gen}} > 0$ are fixed parameters, then the maximal power that can be delivered (transferred) to $R_{text{load}}$ equals

$$P_{\text{max}} = \frac{E_{\text{gen}}^2}{4R_{\text{gen}}}.$$

Such power is delivered to R_{load} if and only if

$$R_{\text{load}} = R_{\text{gen}}.$$

Proof of MPT Theorem

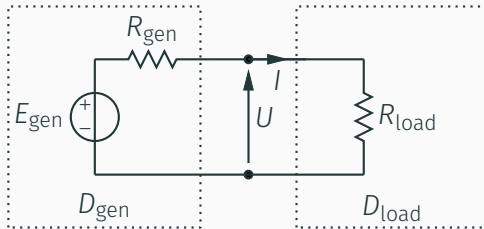

$$P = \left(\frac{E_{\text{gen}}}{R_{\text{gen}} + R_{\text{load}}} \right)^2 R_{\text{load}} = \frac{E_{\text{gen}}^2}{4R_{\text{gen}}} \frac{R_{\text{load}}}{R_{\text{gen}} + R_{\text{load}}} \frac{4R_{\text{gen}}}{R_{\text{gen}} + R_{\text{load}}}$$

$$4 \frac{R_{\text{load}}}{R_{\text{gen}} + R_{\text{load}}} \frac{R_{\text{gen}}}{R_{\text{gen}} + R_{\text{load}}} \stackrel{4ab \leq (a+b)^2}{\leq} \left(\frac{R_{\text{load}}}{R_{\text{gen}} + R_{\text{load}}} + \frac{R_{\text{gen}}}{R_{\text{gen}} + R_{\text{load}}} \right)^2 = 1.$$

Thus $P \leq \frac{E_{\text{gen}}^2}{4R_{\text{gen}}}$ and „ = “ $\stackrel{a=b}{\iff} R_{\text{load}} = R_{\text{gen}}$.

Electric Energy

Energy delivered to a device in the period (t_0, t_1) is the quantity

$$w(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt,$$


where $p(t)$ is the instantaneous power delivered to the device in time instant $t \in (t_0, t_1)$.

Energy delivered to a resistor



$$w(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} i^2(t) R dt \geq 0.$$

Energy delivered to an inductor

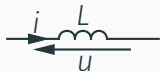


$$\begin{aligned} w(t_0, t_1) &= \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} \underbrace{Li'(t)}_{u(t)} i(t) dt = \int_{t_0}^{t_1} \left(\frac{1}{2} Li^2(t) \right)' dt \\ &= \frac{1}{2} Li^2(t_1) - \frac{1}{2} Li^2(t_0). \end{aligned}$$

$w(t_0, t_1)$ may be negative, positive or zero.

Energy stored in the inductor: $w_L(i) = \frac{1}{2} Li^2$.

$$w(t_0, t_1) = w_L(i(t_1)) - w_L(i(t_0)).$$

Energy delivered to a capacitor

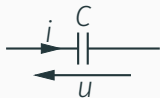


$$\begin{aligned} w(t_0, t_1) &= \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} u(t) \underbrace{Cu'(t)}_{i(t)} dt = \int_{t_0}^{t_1} \left(\frac{1}{2} Cu^2(t) \right)' dt \\ &= \frac{1}{2} Cu^2(t_1) - \frac{1}{2} Cu^2(t_0). \end{aligned}$$

$w(t_0, t_1)$ may be negative, positive or zero.

Energy stored in the capacitor: $w_C(u) = \frac{1}{2} Cu^2$.

$$w(t_0, t_1) = w_C(u(t_1)) - w_C(u(t_0)).$$

Energy delivered to a transformer

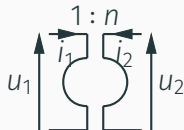


$$p(t) = (u_1 i_1 + u_2 i_2)(t) = \left(u_1 i_1 + \underbrace{(n u_1) \left(-\frac{1}{n} i_1 \right)}_{-u_1 i_1} \right) (t) = 0.$$

$$w(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt = 0.$$

Coupled Inductors

Coupled inductors is a 2-port:

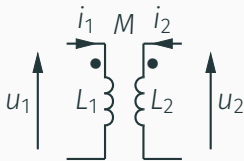

$$u_1 = L_1 i_1' + M i_2',$$

$$u_2 = L_2 i_2' + M i_1',$$

where $0 \leq M \leq \sqrt{L_1 L_2}$ is called mutual inductance [H]

($k = M/\sqrt{L_1 L_2}$ is called the coupling coefficient).

Energy delivered to coupled inductors

$$u_1 = L_1 i_1' + M i_2',$$


$$u_2 = L_2 i_2' + M i_1',$$

$$\begin{aligned} w(t_0, t_1) &= \int_{t_0}^{t_1} \underbrace{(u_1 i_1 + u_2 i_2)}_p(t) dt = \\ &= \frac{1}{2} L_1 (i_1^2(t_1) - i_1^2(t_0)) + \frac{1}{2} L_2 (i_2^2(t_1) - i_2^2(t_0)) + \\ &\quad + M (i_1(t_1) i_2(t_1) - i_1(t_0) i_2(t_0)). \end{aligned}$$

Energy stored in coupled inductors:

$$w_M(i_1, i_2) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2.$$

Nonlinear capacitor

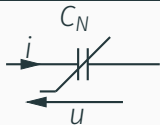


$$q = q(u) \quad \text{linear case: } q = Cu$$

$$i(t) = q'(t) = \frac{dq}{du} \frac{du}{dt}(t) = \frac{dq(u(t))}{du} u'(t).$$

$$\begin{aligned} w(t_0, t_1) &= \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} u(t) \frac{dq(u(t))}{du} u'(t) dt = \\ &\quad \dots \left| \begin{array}{l} u = u(t) \\ du = u'(t) dt \end{array} \right| \dots = \int_{u(t_0)}^{u(t_1)} u \frac{dq(u)}{du} du. \end{aligned}$$

$$\text{Energy stored: } w_{C_N}(u) = \int_0^u u \frac{dq(u)}{du} du.$$

Nonlinear inductor

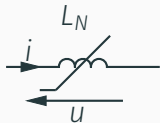


$$\boxed{\psi = \psi(i)} \quad \text{linear case: } \psi = Li$$

$$u(t) = \psi'(t) = \frac{d\psi}{di} \frac{di}{dt}(t) = \frac{d\psi(i(t))}{di} i'(t).$$

$$w(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} i(t) \frac{d\psi(i(t))}{di} i'(t) dt =$$
$$\cdots \left| \begin{array}{l} i = i(t) \\ di = i'(t) dt \end{array} \right| \cdots = \int_{i(t_0)}^{i(t_1)} i \frac{d\psi(i)}{di} di.$$

$$\text{Energy stored: } w_{L_N}(i) = \int_0^i i \frac{d\psi(i)}{di} di.$$

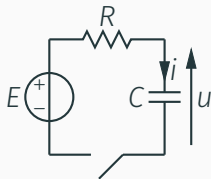
How is the energy delivered to elements in DC circuits



$$t < t_0,$$

$$i(t) = 0,$$

$$u(t) = 0.$$

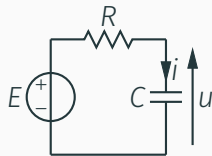

$$t \geq t_0$$

