

Circuits and Signals

Transient states in RLC circuits

Marek Rupniewski


2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

RLC circuit

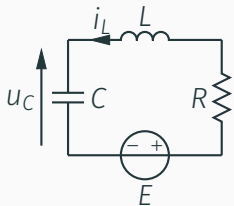

$$u_C(t_0) = U_0, \quad i_L(t_0) = I_0.$$

$$u_C + Li'_L + Ri_L = E.$$


$$i_L = Cu'_C, \quad i'_L = Cu''_C.$$

$$LCu''_C + RCu'_C + u_C = E,$$

$$\underbrace{\frac{L}{CR^2}}_{Q^2} \underbrace{(RC)^2}_{\tau^2} u''_C + \underbrace{RC}_{\tau} u'_C + u_C = E,$$

$$(Q\tau)^2 u''_C + \tau u'_C + u_C = E.$$

RLC circuit

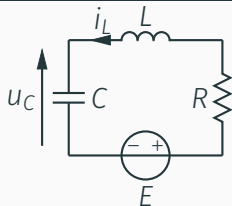


$$(Q\tau)^2 u_C'' + \tau u_C' + u_C = E, \quad \tau = RC, \quad Q = \frac{\sqrt{L/C}}{R}.$$

$$\Delta = \tau^2 - 4(Q\tau)^2 = \tau^2(1 - 2Q)(1 + 2Q).$$

There are 3 qualitatively different cases:

- $Q < \frac{1}{2}$ — the overdamped case,
- $Q > \frac{1}{2}$ — the underdamped case.
- $Q = \frac{1}{2}$ — the critically damped case,

RLC circuit — overdamped case

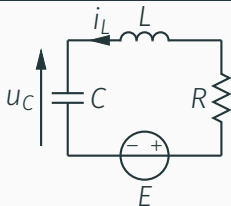

$$(Q\tau)^2 u_C'' + \tau u_C' + u_C = E, \quad \tau = RC, \quad Q = \frac{\sqrt{L/C}}{R} < \frac{1}{2}.$$



$$u_C(t) = E + Ae^{\omega_1(t-t_0)} + Be^{\omega_2(t-t_0)},$$

where ω_1 and ω_2 are real roots of the characteristic equation:


$$(Q\tau)^2 s^2 + \tau s + 1 = 0,$$

and A , B are constants to be determined (using IC).

RLC circuit — overdamped case

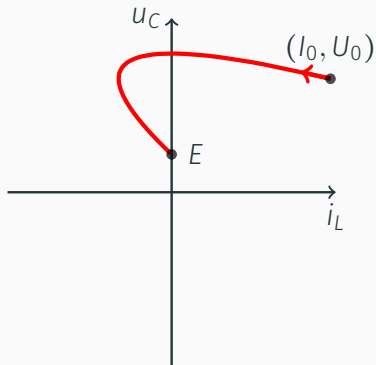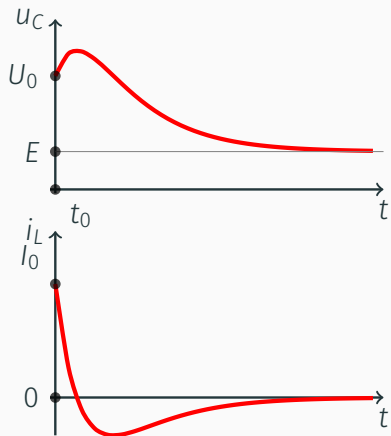

RLC circuit — underdamped case

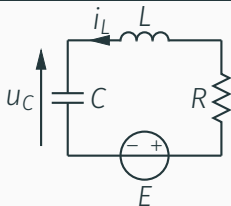

$$(Q\tau)^2 u_C'' + \tau u_C' + u_C = E, \quad \tau = RC, \quad Q = \frac{\sqrt{L/C}}{R} > \frac{1}{2}.$$



$$u_C(t) = E + Ae^{-\omega_r(t-t_0)} \cos(\omega_s(t-t_0) + \varphi),$$

where $\omega_r \pm j\omega_s$ are (conjugated) complex roots of the characteristic equation:


$$(Q\tau)^2 s^2 + \tau s + 1 = 0,$$

and A , φ are constants to be determined (using IC).

RLC circuit — underdamped case

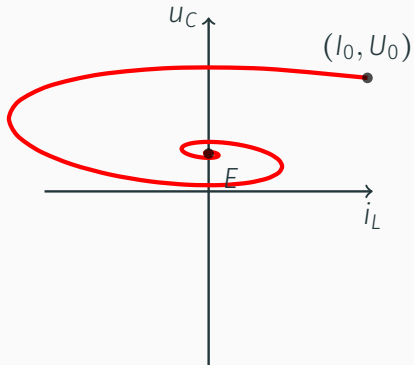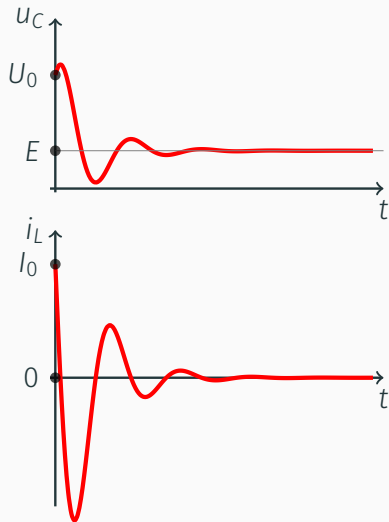

RLC circuit — critically damped case

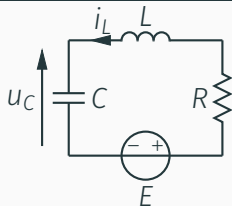

$$(Q\tau)^2 u_C'' + \tau u_C' + u_C = E, \quad \tau = RC, \quad Q = \frac{\sqrt{L/C}}{R} = \frac{1}{2}.$$

$$u_C(t) = E + Ae^{-\frac{t-t_0}{\tau/2}} + B(t-t_0)e^{-\frac{t-t_0}{\tau/2}},$$

where $-\tau/2$ is the double (real) root of the characteristic equation:

$$(Q\tau)^2 s^2 + \tau s + 1 = 0,$$

and A, B are constants to be determined (using IC).

RLC circuit — critically damped case

