

Circuits and Signals

Signals, Devices, Circuits, Kirchhoff's Laws — continuation

Marek Rupniewski

2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

Recap




Lumped Device



We assume that $i_1 + i_2 + \dots + i_n = 0$ (the total charge stored in the device is preserved).

The device is described by a set of relations (equations) that relates terminal currents and inter-terminal voltages.

Basic devices

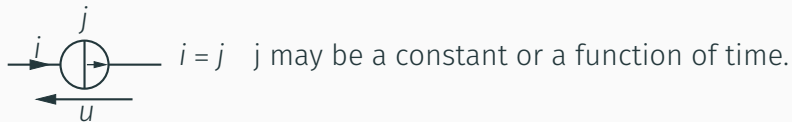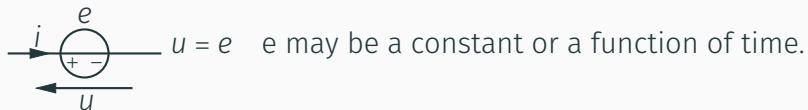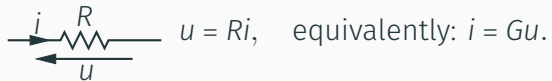

Symmetry of device's terminals




$$u = Ri$$



$$u = Ri$$




$$u = e$$

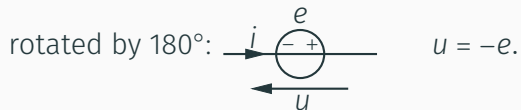

$$u = -e.$$

Kirchhoff's Current Law (KCL)

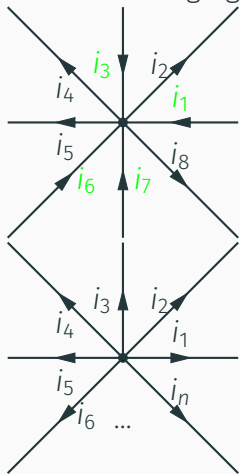The total sum of the currents converging to a node equals the sum of all the currents diverging from the node.




$$i_1 + i_3 + i_6 + i_7 = i_2 + i_4 + i_5 + i_8.$$

$$i_1 + i_2 + \cdots + i_n = 0.$$

Kirchhoff's Voltage Law (KVL)

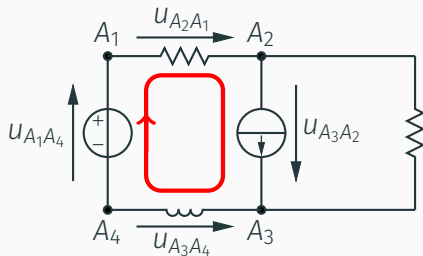The algebraic sum of the voltage drops along any directed loop equals zero.



$$u_{A_1A_4} + u_{A_2A_1} + u_{A_3A_2} - u_{A_3A_4} = 0.$$

Equivalent formulation: The voltage between any two nodes does not depend on the (oriented) path along which it is computed.

$$u_{A_1A_4} = u_{A_3A_4} - u_{A_3A_2} - u_{A_2A_1}.$$


Some more basic devices

Capacitor

real-life...
... and its symbol



$$q = Cu, \quad i = Cu'.$$

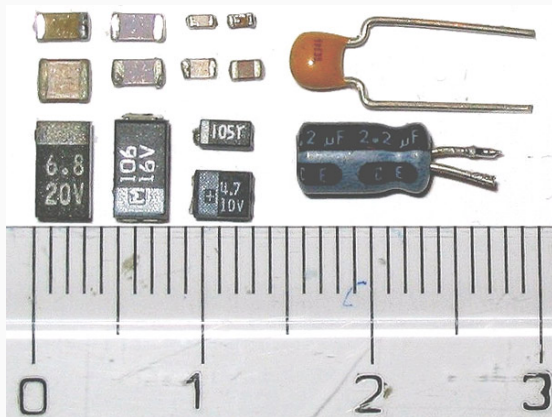

C [F] is called **capacitance**.


Alternative symbols: , , ,

Inductor

real-life...
... and its symbol




$$\psi = Li, \quad \boxed{u = Li'}.$$

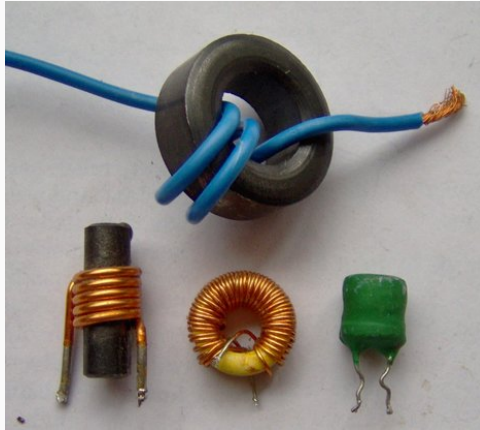

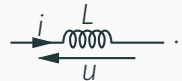
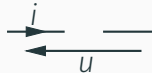
L [H] is called **inductance**.



Alternative symbols:





Special one-ports

• short-circuit _____ , equation:  $u = 0$,

• open-circuit _____ , equation:  $i = 0$,

• fixator  , equation:  $u = e, i = j$,

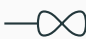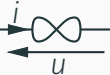• norator  , equation:  \emptyset .

A device port

A **port** of a device is a pair of device terminals such that any current flowing in through one terminal of a port must flow out through the other terminal of the port.



Every 2-terminal device is automatically a one-port!

Two-ports



Some basic linear 2-ports



Transformer and DC-DC converters

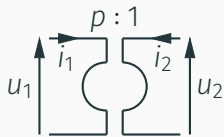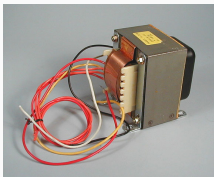

$$\begin{aligned} u_1 &= p u_2, \\ i_1 &= -\frac{1}{p} i_2. \end{aligned}$$

$p[]$ is called **winding ratio**.


Alternative symbols:

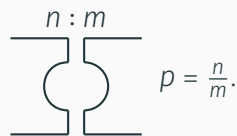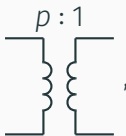

Controlled Voltage Sources




Voltage Controlled V. S.

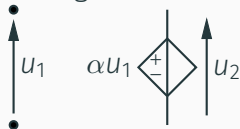

$$u_2 = \alpha u_1,$$

α is a **voltage gain**.

Current Controlled V. S.

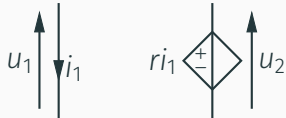


$$u_2 = r i_1,$$

$r [\Omega]$ is a **transresistance**.

Controlled Current Sources



Voltage Controlled C. S.

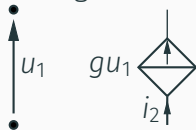

$$i_2 = gu_1,$$

$g [S]=[U]$ is transconductance.

Current Controlled C. S.




$$i_2 = \beta i_1,$$

β is a current gain.

Circuit diagrams

Circuit Schematic — an example

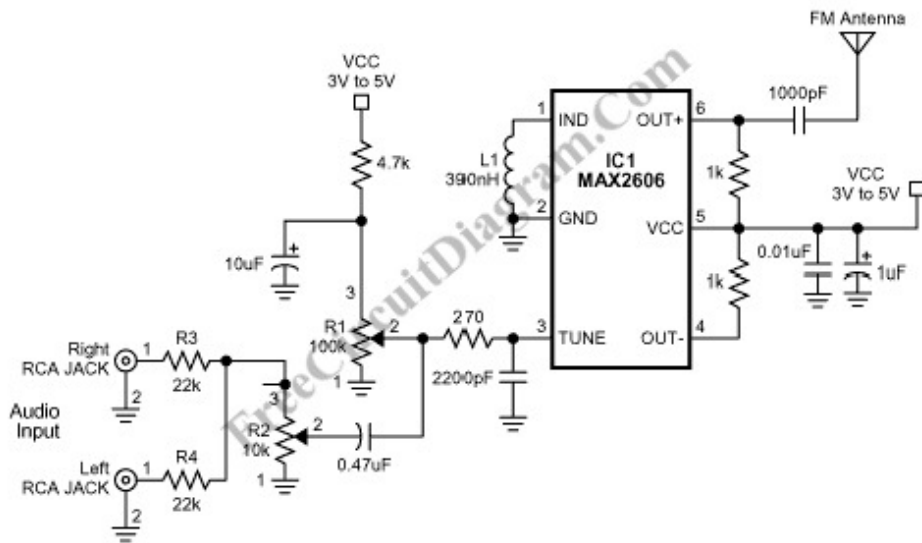

Circuit Schematic — another example

