

Circuits and Signals

Powers in AC circuits

Marek Rupniewski


2022 spring semester



**Faculty of Electronics
and Information
Technology**


WARSAW UNIVERSITY OF TECHNOLOGY

Instantaneous power — recap

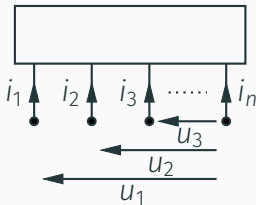


$$p(t) = i_1(t)u_1(t) + i_2(t)u_2(t) + \dots + i_{n-1}(t)u_{n-1}(t).$$

For a one-port:

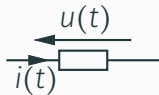

$$p(t) = u(t)i(t).$$

Instantaneous power in an AC circuit

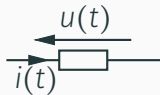

$$p(t) = u(t)i(t).$$

$$i(t) = I_m \cos(\omega t + \phi), \quad u(t) = U_m \cos(\omega t + \psi).$$

$$\begin{aligned} p(t) &= I_m U_m \cos(\omega t + \phi) \cos(\omega t + \psi) \quad \cos \alpha \cos \beta = \frac{1}{2} (\cos(\alpha + \beta) + \cos(\alpha - \beta)) \\ &= \frac{1}{2} U_m I_m \cos(\phi - \psi) + \frac{1}{2} U_m I_m \cos(2\omega t + \phi + \psi). \end{aligned}$$

Mean power and real power

Mean power:

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt, \quad T = \frac{2\pi}{\omega}.$$

In the AC circuit context, the mean power is called also the **real power**.


If

$$p(t) = \frac{1}{2} U_m I_m \cos(\phi - \psi) + \frac{1}{2} U_m I_m \cos(2\omega t + \phi + \psi),$$

then

$$P = \frac{1}{2} U_m I_m \cos(\phi - \psi).$$

Real power and the phasors

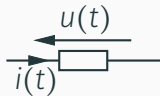

$$p(t) = u(t)i(t).$$

$$i(t) = I_m \cos(\omega t + \phi), \quad u(t) = U_m \cos(\omega t + \psi).$$

$$P = \frac{1}{2} U_m I_m \cos(\phi - \psi).$$


It occurs that

$$P = \frac{1}{2} \operatorname{Re}(U \bar{I}), \quad U = U_m e^{j\psi}, I = I_m e^{j\phi}.$$

Indeed

$$U \bar{I} = U_m e^{j\psi} I_m e^{-j\phi} = U_m I_m e^{j(\psi - \phi)} = U_m I_m (\cos(\psi - \phi) + j \sin(\psi - \phi)).$$

Real power and the impedance

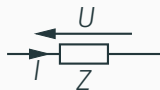


$$P = \frac{1}{2} \operatorname{Re}(U\bar{I})$$

$$P \stackrel{U=ZI}{=} \frac{1}{2} \operatorname{Re}(Z \underbrace{\bar{I}I}_{|I|^2}) = \frac{1}{2} |I|^2 \operatorname{Re} Z.$$

And also

$$P \stackrel{I=U/Z}{=} \frac{1}{2} \operatorname{Re}(\underbrace{U\bar{U}}_{|U|^2} / \bar{Z}) = \frac{1}{2} |U|^2 \operatorname{Re} \frac{1}{\bar{Z}} \stackrel{\operatorname{Re} Z = \operatorname{Re} \bar{Z}}{=} \frac{1}{2} |U|^2 \operatorname{Re} \frac{1}{Z}.$$

Real power — examples

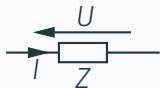

$$P = \frac{1}{2}|I|^2 \operatorname{Re} Z = \frac{1}{2}|U|^2 \operatorname{Re} \frac{1}{Z}.$$

Inductor ($Z = j\omega L$):

$$P = 0.$$

Capacitor ($Z = \frac{1}{j\omega C} = -j\frac{1}{\omega C}$):

$$P = 0.$$

Resistor ($Z = R$):

$$P = \frac{1}{2}|I|^2 R = \frac{1}{2} \frac{|U|^2}{R}.$$

RMS value of a signal


RMS (root mean square) value X_{RMS} of a T -periodic signal x :

$$X_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}, \quad T = \frac{2\pi}{\omega}.$$

For a harmonic signal $x(t) = X_m \cos(\omega t + \phi)$:

$$\begin{aligned} X_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} X_m^2 \cos^2(\omega t + \phi) dt} \quad \cos^2 \alpha = \frac{1}{2}(\cos 2\alpha + 1) \\ &= \sqrt{\underbrace{\frac{1}{T} \int_{t_0}^{t_0+T} \frac{1}{2} X_m^2 dt}_{T \frac{1}{2} X_m^2} + \underbrace{\frac{1}{T} \int_{t_0}^{t_0+T} \frac{1}{2} X_m^2 \cos(2\omega t + 2\phi) dt}_0} \\ &= \sqrt{\frac{1}{2} X_m^2} = \frac{X_m}{\sqrt{2}}. \end{aligned}$$

Real power and RMS values

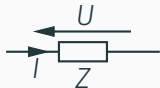

$$P = \frac{1}{2}|I|^2 \operatorname{Re} Z = \frac{1}{2}|U|^2 \operatorname{Re} \frac{1}{Z}.$$


Therefore

$$P = I_{\text{RMS}}^2 \operatorname{Re} Z = U_{\text{RMS}}^2 \operatorname{Re} \frac{1}{Z}.$$

For a resistor $Z = R$ we thus obtain „the same” formulas as those for DC case

$$P = I_{\text{RMS}}^2 R = \frac{U_{\text{RMS}}^2}{R}.$$

Powers in AC circuits

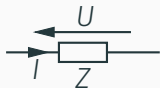

Real power:

$$P = \frac{1}{2} \operatorname{Re}(U\bar{I}) \quad [\text{W}].$$

Reactive power:

$$Q = \frac{1}{2} \operatorname{Im}(U\bar{I}) \quad [\text{VAr}].$$

Complex power:


$$S = \frac{1}{2} U\bar{I} \quad [\text{VA}].$$

Apparent power:

$$|S| = \frac{1}{2} U_m I_m \quad [\text{VA}].$$

$$S = P + jQ$$

Power factor

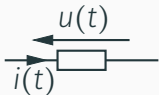

$$p(t) = u(t)i(t).$$

$$i(t) = I_m \cos(\omega t + \phi), \quad u(t) = U_m \cos(\omega t + \psi).$$


$$p(t) = \underbrace{\frac{1}{2} U_m I_m \cos(\phi - \psi)}_P + \underbrace{\frac{1}{2} U_m I_m \cos(2\omega t + \phi + \psi)}_{|S|}.$$

Power factor P.F.

$$\text{P.F.} = \frac{P}{|S|} \quad -1 \leq \text{P.F.} \leq 1.$$

$$P = |S| \times \text{P.F.}, \quad \text{P.F.} = \cos \angle (U, I) = \cos \arg \frac{U}{I} = \cos \arg Z.$$

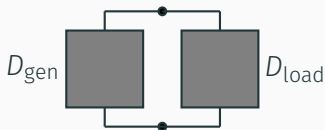
Maximum power transfer theorem — introduction



Assumption: D_{gen} is fixed (we cannot change it).

For what one-port D_{load} the **real** power delivered to $D_{text{load}}$ is maximal?

Maximum Power Transfer Theorem (AC case)

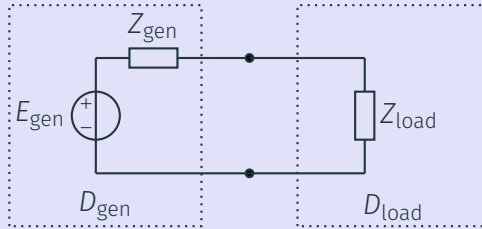

If $E_{\text{gen}} \neq 0$ and Z_{gen} are fixed parameters and if $\text{Re}Z_{\text{gen}} > 0$, then the maximal **real** power that can be delivered (transferred) to Z_{load} equals

$$P_{\text{max}} = \frac{|E_{\text{gen}}|^2}{8 \text{Re}Z_{\text{gen}}}.$$


Such power is delivered to Z_{load} if and only if

$$Z_{\text{load}} = \overline{Z_{\text{gen}}}.$$

MPT theorems in DC and AC cases — comparison

	„DC case”	„AC case”
assumptions	$E_{\text{gen}} \neq 0,$ $R_{\text{gen}} > 0$	$E_{\text{gen}} \neq 0,$ $\text{Re } Z_{\text{gen}} > 0$
MPT condition	$R_{\text{load}} = R_{\text{gen}}$	$Z_{\text{load}} = \overline{Z_{\text{gen}}}$
maximal power	$\frac{E_{\text{gen}}^2}{4R_{\text{gen}}}$	$\frac{ E_{\text{gen}} ^2}{8 \text{Re } Z_{\text{gen}}}$
max. power („Norton counterpart”)	$\frac{I_{\text{gen}}^2}{4} R_{\text{gen}}$	$\frac{ I_{\text{gen}} ^2}{8 \text{Re } \frac{1}{Z_{\text{gen}}}}$

MPT theorem — proof

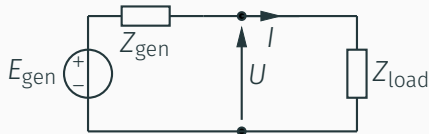

$$P = \frac{1}{2} \left| \frac{E_{\text{gen}}}{Z_{\text{gen}} + Z_{\text{load}}} \right|^2 \text{Re} Z_{\text{load}} = \frac{|E_{\text{gen}}|^2}{8 \text{Re} Z_{\text{gen}}} \frac{2 \text{Re} Z_{\text{load}}}{|Z_{\text{gen}} + Z_{\text{load}}|} \frac{2 \text{Re} Z_{\text{gen}}}{|Z_{\text{gen}} + Z_{\text{load}}|}$$

$$\frac{2 \text{Re} Z_{\text{load}}}{|Z_{\text{gen}} + Z_{\text{load}}|} \frac{2 \text{Re} Z_{\text{gen}}}{|Z_{\text{gen}} + Z_{\text{load}}|} \stackrel{4ab \leq (a+b)^2}{\leq} \left(\frac{\text{Re} Z_{\text{load}} + \text{Re} Z_{\text{gen}}}{|Z_{\text{gen}} + Z_{\text{load}}|} \right)^2 = \frac{\text{Re}^2(Z_{\text{load}} + Z_{\text{gen}})}{\text{Re}^2(Z_{\text{load}} + Z_{\text{gen}}) + \text{Im}^2(Z_{\text{load}} + Z_{\text{gen}})} \stackrel{|x|/(|x|+|y|) \leq 1}{\leq} 1.$$

Thus $P \leq \frac{|E_{\text{gen}}|^2}{8 \text{Re} Z_{\text{gen}}}$ and „ $\stackrel{a=b, |y|=0}{\iff}$ “ $\text{Re} Z_{\text{load}} = \text{Re} Z_{\text{gen}}$ and $\text{Im} Z_{\text{load}} = -\text{Im} Z_{\text{gen}}$.