

Circuits and Signals

Equivalent devices (continuation)

Marek Rupniewski

2022 spring semester



**Faculty of Electronics
and Information
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

Equivalent devices

Devices are called equivalent if they are governed by equivalent equations.


Device equations determines the behaviour of the device in any circuit!

Device equation — an example

Device equation:




$$u = Ri$$

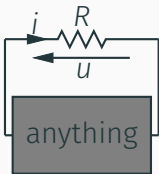


$$u = Ri$$

Device as a part of a bigger circuit vs device as independent circuit


Device equation:

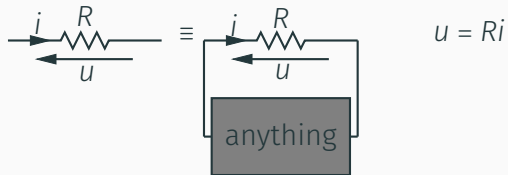

Device as independent circuit:

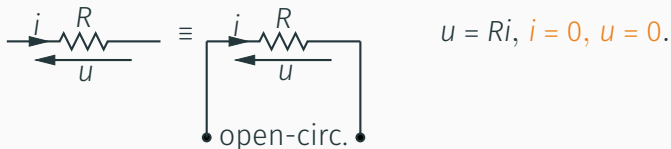


Thévenin's equivalent

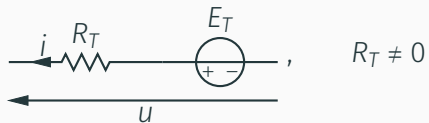



$$u = E_T - R_T i.$$

Norton's equivalent

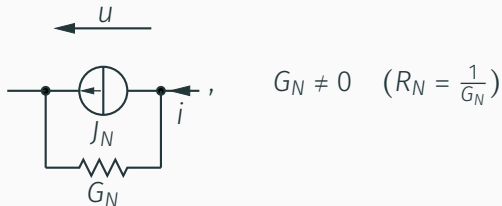

$$i = J_N - uG_N = J_N - \frac{u}{R_N}.$$

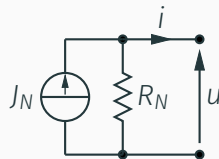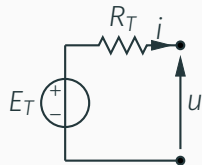Thévenin's and Norton's equivalents equivalence




Thévenin's and Norton's equivalents are equivalent if and only if


$$R_T = R_N \quad \text{and} \quad E_T = J_N R_N.$$

$$u = E_T - R_T i \qquad i = J_N - \frac{u}{R_N} \quad \equiv \quad u = J_N R_N - R_N i.$$


Attention:

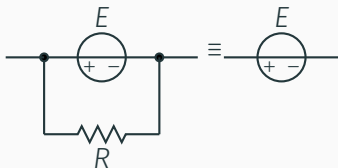


One-port equivalences — an example

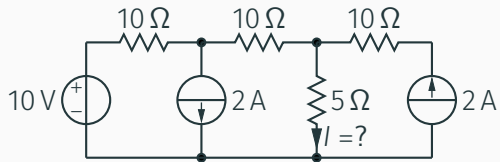


One-port equivalences — an example

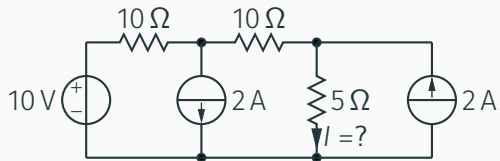


One-port equivalences — an example

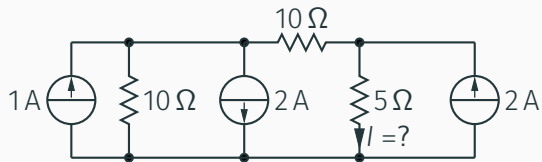

One-port equivalences — an example

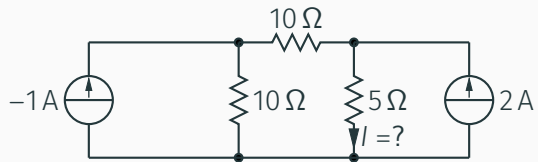


One-port equivalences — an example

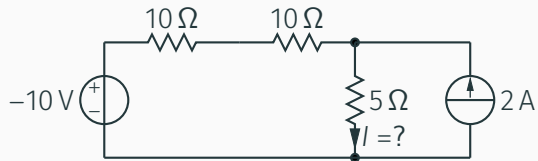

One-port equivalences — an example



One-port equivalences — an example


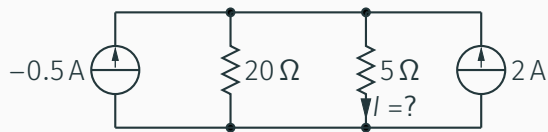


One-port equivalences — an example



$$I \stackrel{\text{CDF}}{=} \frac{3}{2} \times \frac{20}{20 + 5} \text{ A} \\ = \frac{6}{5} \text{ A}$$

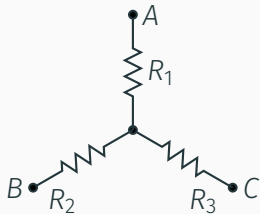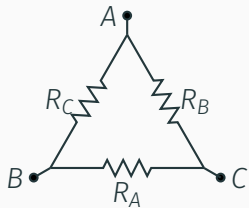$\Delta - \star$ and $\star - \Delta$ transformations



Equivalent if:

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1},$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2},$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$


In other words:

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C},$$


$$R_2 = \frac{R_C R_A}{R_A + R_B + R_C},$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}.$$

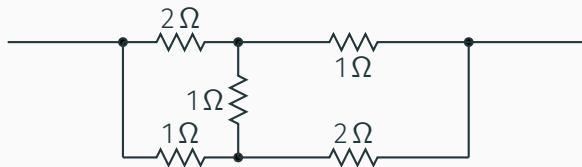Every one-port comprising of resistors only is equivalent to a resistor




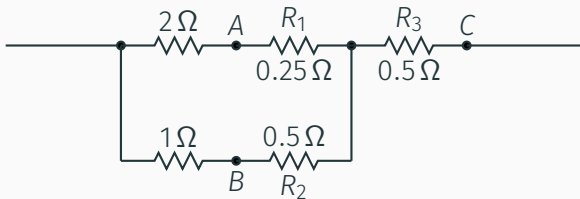Every one-port comprising of resistors only is equivalent to a resistor



$$R_{\text{eq}} = \left(\frac{9}{4} \parallel \frac{3}{2} + \frac{1}{2} \right) \Omega = \left(\frac{\frac{9}{4} \times \frac{3}{2}}{\frac{9}{4} + \frac{3}{2}} + \frac{1}{2} \right) \Omega = \left(\frac{27}{30} + \frac{1}{2} \right) \Omega = \frac{7}{5} \Omega.$$

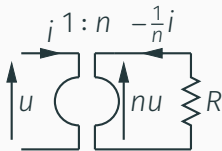
A one-port comprising of different devices can still be equivalent with a resistor



$$u \stackrel{?}{=} R_{\text{eq}} i$$


$$nu = -R\left(-\frac{1}{n}i\right), \quad u = \underbrace{\frac{1}{n^2}R}_{R_{\text{eq}}} i.$$

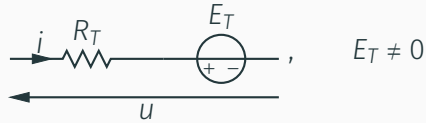A one-port comprising of different devices **does not have to** be equivalent to a resistor



$$u = E_T + R_T i.$$

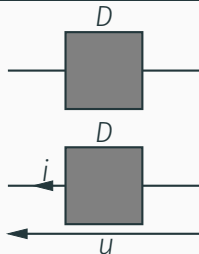What is a **linear DC** one-port equivalent to?





The following cases are possible:

$i = J_N$,	u arbitrary,	current source,
i arbitrary,	$u = E_T$,	voltage source,
i arbitrary,	$u = E_T - iR_T$, $R_T \neq 0$,	Thévenin's equivalent ,
$i = J_N$,	$u = E_T$,	fixator,
i arbitrary,	u arbitrary,	norator.


What is a **linear DC** one-port equivalent to?

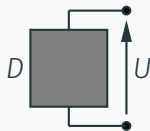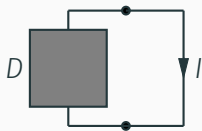Consider two connections (not necessarily circuits!):





I	U	one-port's type
*	*	norator
\emptyset	\emptyset	fixator
\emptyset	E	voltage source or fixator generating zero current
J	\emptyset	current source or fixator generating zero voltage
J	E	Thévenin's equivalent: $E_T = E$, $R_T = E/J$ (equivalently, Norton's equivalent: $J_N = J$, $R_N = E/J$)
0	0	nullator or resistor.

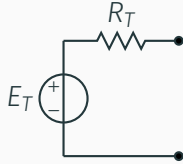
Thévenin's and Norton's equivalents parameters



$$E_T = J_N R_N, R_T = R_N$$

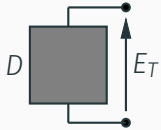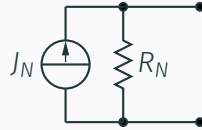

E_T is the open-circuit voltage,

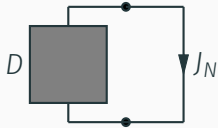

J_N is the short-circuit current,

$$R_T = R_N = \frac{E_T}{J_N}.$$

An alternative way of determining internal (output) resistance



If short-circuit current is non-zero:

$$R_T = R_N = \frac{\text{open-circuit voltage}}{\text{short-circuit current}}.$$


In general:

The internal (output) resistance $R_T = R_N$ of a one-port equals the equivalent resistance of the reduced one-port that results from the original one-port by reduction of all the independent sources to zeros.

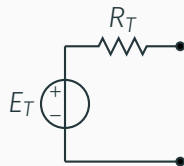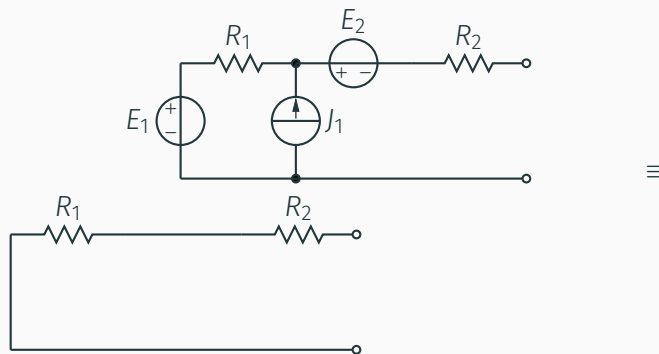Thévenin's equivalent parameters — an example




$$R_T = R_1 + R_2.$$

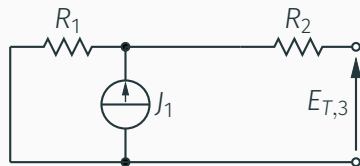


$$E_T = \underbrace{E_1} + \underbrace{(-E_2)} + \underbrace{J_1 R_1}.$$

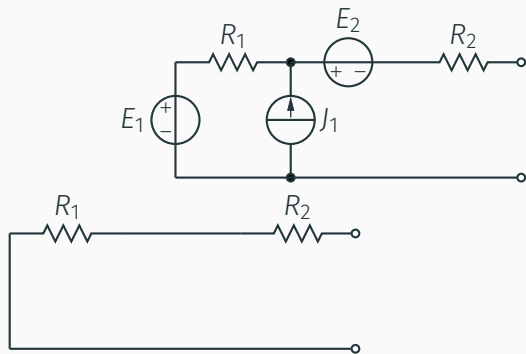
Norton's equivalent parameters — an example



\equiv

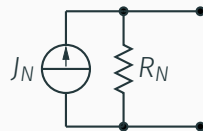


$$R_T = R_1 + R_2.$$

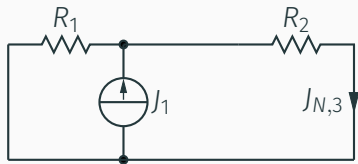

$$J_N = \underbrace{\frac{E_1}{R_1 + R_2}}_{J_{N,1}} + \underbrace{\frac{-E_2}{R_1 + R_2}}_{J_{N,2}} + \underbrace{J_1 \frac{R_1}{R_1 + R_2}}_{J_{N,3}}.$$


Thévenin equivalent – another example – 1st option (find E_T and R_T)
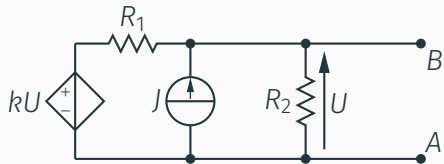
$$J = 6 \text{ mA}, k = \frac{1}{4}, R_1 = 1.5 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega.$$



Thévenin equivalent – another example – 2nd option (find E_T and J_N ; then $R_T = \frac{E_T}{J_N}$)
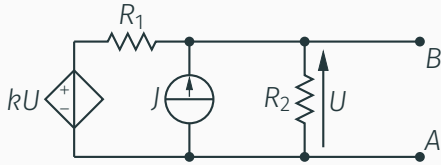
$$J = 6 \text{ mA}, k = \frac{1}{4}, R_1 = 1.5 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega.$$



Thévenin equivalent – another example – 3rd option (find J_N and R_T ; then $E_T = J_N R_T$)

$$J = 6 \text{ mA}, k = \frac{1}{4}, R_1 = 1.5 \text{ k}\Omega, R_2 = 6 \text{ k}\Omega.$$

