

# Circuits and Signals

DC analysis

---

Marek Rupniewski

2022 spring semester



**Faculty of Electronics  
and Information  
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

# DC analysis

A DC (**direct current**) solution to a circuit is a solution consisting entirely of constant signals (all voltages and currents).

# DC analysis

For DC analysis all ODEs reduce to algebraic equations:

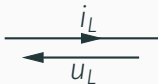

$$u_L = Li'_L,$$

for direct signals  $u_L, i_L$ :

$$u_L = Li'_L = 0$$

thus  $u_L = 0$ ,

short-circuit




$$i_C = Cu'_C,$$

for direct signals  $u_C, i_C$ :

$$i_C = Cu'_C = 0$$

thus  $i_C = 0$ ,

open-circuit




# What do we have at our disposal?

- Kirchhoff's laws (KCL, KVL),
- device equations.

## Nodal method

1. Label all the nodes with variables  $e_1, e_2, \dots, e_N$  denoting electric potentials,

# Nodal method

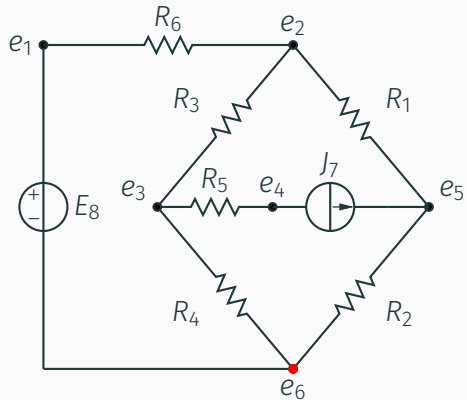


## Nodal method

1. Label all the nodes with variables  $e_1, e_2, \dots, e_N$  denoting electric potentials,
2. Label the currents  $(i_1, i_2, \dots, i_M)$  flowing into all the elements. For each  $n$ -terminal element we introduce  $n - 1$  new variables in this way,

The current **flowing out** of the last terminal of an  $n$ -terminal element equals the sum of the currents **flowing into** all the other terminals.

# Nodal method

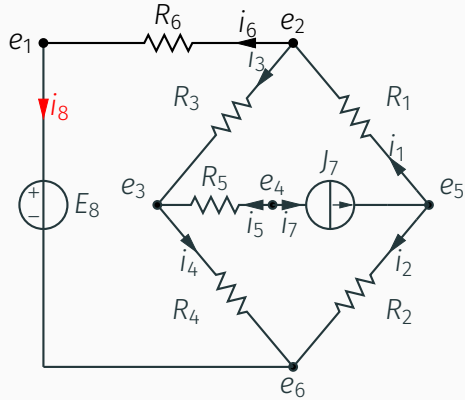




## Nodal method

1. Label all the nodes with variables  $e_1, e_2, \dots, e_N$  denoting electric potentials,
2. Label the currents  $(i_1, i_2, \dots, i_M)$  flowing into all the elements. For each  $n$ -terminal element we introduce  $n - 1$  new variables in this way,
3. Write down the KCL equations (for each node),

# Nodal method

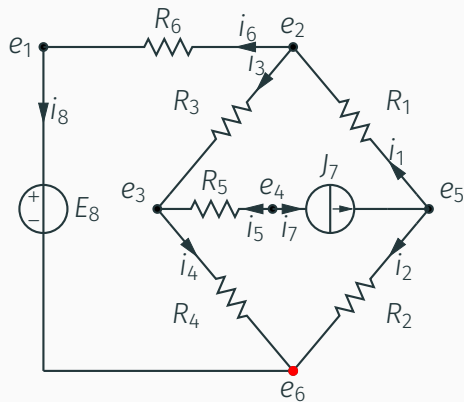

$$i_6 = i_8, \quad (e_1)$$

$$i_1 = i_3 + i_6, \quad (e_2)$$

$$i_3 + i_5 = i_4, \quad (e_3)$$

$$0 = i_5 + i_7, \quad (e_4)$$


$$i_7 = i_1 + i_2, \quad (e_5)$$

$$i_2 + i_4 + i_8 = 0. \quad (e_6)$$

## Nodal method

1. Label all the nodes with variables  $e_1, e_2, \dots, e_N$  denoting electric potentials,
2. Label the currents  $(i_1, i_2, \dots, i_M)$  flowing into all the elements. For each  $n$ -terminal element we introduce  $n - 1$  new variables in this way,
3. Write down the KCL equations (for each node),
4. Write down element equations expressed in terms of electric potentials  $e_1, \dots, e_N$  and currents  $i_1, \dots, i_M$ .

# Nodal method

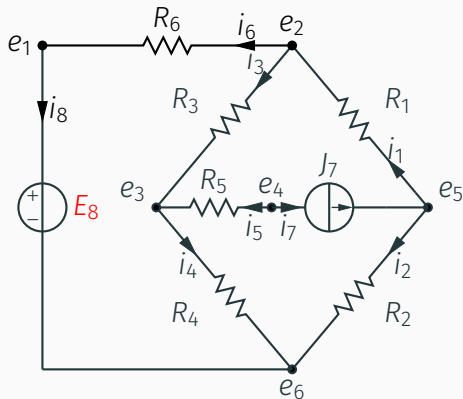

$$e_5 - e_2 = i_1 R_1, \quad (1)$$

$$e_5 - e_6 = i_2 R_2, \quad (2)$$

$$e_2 - e_3 = i_3 R_3, \quad (3)$$

$$e_3 - e_6 = i_4 R_4, \quad (4)$$

$$e_4 - e_3 = i_5 R_5, \quad (5)$$

$$e_2 - e_1 = i_6 R_6, \quad (6)$$

$$i_7 = J_7, \quad (7)$$

$$e_1 - e_6 = E_8. \quad (8)$$

## Nodal method

1. Label all the nodes with variables  $e_1, e_2, \dots, e_N$  denoting electric potentials,
2. Label the currents  $(i_1, i_2, \dots, i_M)$  flowing into all the elements. For each  $n$ -terminal element we introduce  $n - 1$  new variables in this way,
3. Write down the KCL equations (for each node),
4. Write down the element equations expressed in terms of electric potentials  $e_1, \dots, e_N$  and currents  $i_1, \dots, i_M$ .
5. Solve the obtained set of equations.

Every voltage can be recovered as the difference of appropriate electric potentials.

# Nodal method

$$i_6 = i_8, \quad (e_1) \quad e_5 - e_2 = i_1 R_1, \quad (1)$$

$$i_1 = i_3 + i_6, \quad (e_2) \quad e_5 - e_6 = i_2 R_2, \quad (2)$$

$$i_3 + i_5 = i_4, \quad (e_3) \quad e_2 - e_3 = i_3 R_3, \quad (3)$$

$$0 = i_5 + i_7, \quad (e_4) \quad e_3 - e_6 = i_4 R_4, \quad (4)$$

$$i_7 = i_1 + i_2, \quad (e_5) \quad e_4 - e_3 = i_5 R_5, \quad (5)$$

$$i_2 + i_4 + i_8 = 0. \quad (e_6) \quad e_2 - e_1 = i_6 R_6, \quad (6)$$

$$i_7 = J_7, \quad (7)$$

$$e_1 - e_6 = E_8. \quad (8)$$

# Nodal method

$$i_6 = i_8, \quad (e_1)$$

$$i_1 = i_3 + i_6, \quad (e_2)$$

$$i_3 + i_5 = i_4, \quad (e_3)$$

$$0 = i_5 + i_7, \quad (e_4)$$

$$i_7 = i_1 + i_2, \quad (e_5)$$

$$\underline{i_2 + i_4 + i_8 = 0.} \quad (e_6)$$

$$e_5 - e_2 = i_1 R_1, \quad (1)$$

$$e_5 - 0 = i_2 R_2, \quad (2)$$

$$e_2 - e_3 = i_3 R_3, \quad (3)$$

$$e_3 - 0 = i_4 R_4, \quad (4)$$

$$e_4 - e_3 = i_5 R_5, \quad (5)$$


$$e_2 - e_1 = i_6 R_6, \quad (6)$$

$$i_7 = J_7, \quad (7)$$

$$e_1 - 0 = E_8. \quad (8)$$


$$e_6 = 0 \quad (9)$$

# Nodal method

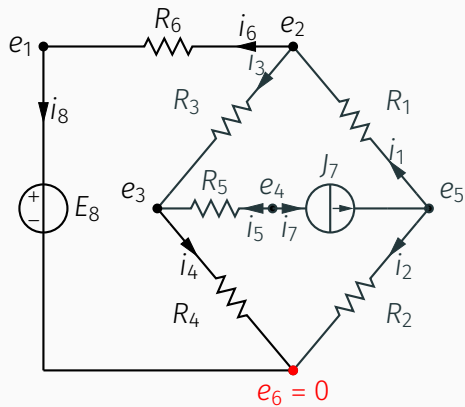



# Nodal method

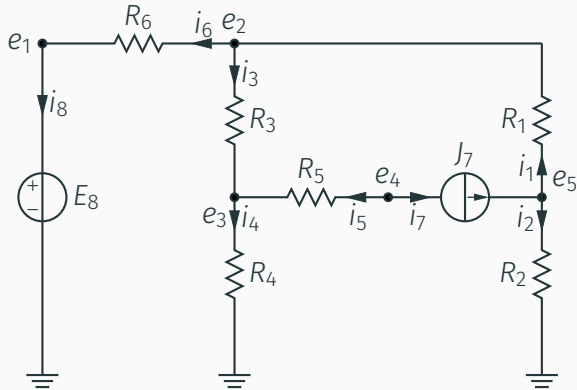

Electric potentials are measured with respect to ground node and KCL for that node is dropped.