

# Circuits and Signals

## Resonance

---

Marek Rupniewski


2022 spring semester



**Faculty of Electronics  
and Information  
Technology**

WARSAW UNIVERSITY OF TECHNOLOGY

## Resonance pulsation/frequency

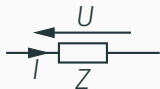

### Definition

A **resonant pulsation** of a one port is any pulsation  $\omega_0$  such that  $|Z(\omega)|$  attains at  $\omega_0$  a proper local minimum or a proper local maximum.

$|Z|$  can be substituted with  $|Z|^2$ ,  $\frac{1}{|Z|} = |Y|$  or  $|Y|^2$ .

Another definition (**not equivalent to the previous one**):

Resonant pulsation is a pulsation for which impedance becomes real.

Frequency and pulsation:

$$\omega_0 = 2\pi f_0.$$



## Definition

A **Q factor** related to resonant pulsation  $\omega_0$  is the number

$$Q_{\omega_0} = 2\pi \frac{w_{\max}}{w(0, T)}, \quad T = \frac{2\pi}{\omega_0},$$

where  $w(0, T)$  is the energy transferred to the one-port during the period ( $T_0 = 2\pi/\omega_0$ ), and  $w_{\max}$  is the maximal (over interval of length  $T_0$ ) value of the energy stored in the one-port.

## Series resonant circuit (SRC)

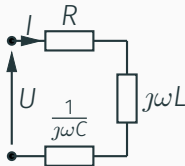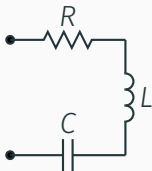

$$Z(\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right).$$

$$|Z(\omega)|^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2.$$

## SRC — resonant pulsation $\omega_0$

$$|Z(\omega)|^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 = R^2 - \frac{2L}{C} + \omega^2 L^2 + \frac{1}{C^2 \omega^2}.$$

$$0 = \frac{d|Z|^2}{d\omega}(\omega_0),$$

therefore

$$0 = 2L^2\omega_0 - \frac{2}{C^2\omega_0^3} \quad \Leftrightarrow \quad 1 = \omega_0^4 L^2 C^2 \quad \Rightarrow \quad \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}.$$

We have

$$\frac{d^2|Z|^2}{d\omega^2}(\omega) = 2L^2 + \frac{6}{C^2\omega^4} > 0.$$

Thus  $\omega_0$  is the unique resonant pulsation of the SRC, and  $|Z|$  attains a global minimum (in the domain  $\omega > 0$ ) at  $\omega_0$ .

## SRC — resonant pulsation $\omega_0$ cont.

$$Z(\omega) = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + \frac{1}{\omega C}j(\omega^2 LC - 1).$$


$$\omega_0 = \frac{1}{\sqrt{LC}}.$$

Thus  $Z$  becomes real at  $\omega_0$ :

$$Z(\omega_0) = R.$$

$\omega_0$  is resonant according to both (non-equivalent in general) definitions of a resonant pulsation.

## SRC — $Q$ factor

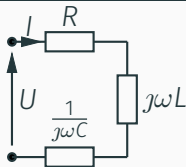

$$Q = 2\pi \frac{W_{\max}}{w(0, T)}, \quad T = \frac{2\pi}{\omega_0},$$

Real power transferred to the one-port

$$P_\omega = \frac{1}{2} |I|^2 \operatorname{Re} Z(\omega).$$

Thus

$$w(0, T) = \frac{2\pi}{\omega_0} P_{\omega_0} = \frac{\pi}{\omega_0} |I|^2 R.$$

$$W_{\max} = \max_{t \in (t_0, t_0 + T]} (w_L(t) + w_C(t)) = \frac{1}{2} \max_{t \in (t_0, t_0 + T]} (Li^2(t) + Cu_C^2(t)).$$

## SRC — Q factor cont.

$$Q = 2\pi \frac{W_{\max}}{w(0, T)}, \quad T = \frac{2\pi}{\omega_0}, \quad w(0, T) = \frac{\pi}{\omega_0} |I|^2 R.$$

$$i(t) = |I| \cos(\omega_0 t + \arg I), \quad U_C = \frac{I}{j\omega_0 C}$$

$$u_C(t) = \frac{|I|}{\omega_0 C} \cos(\omega_0 t + \arg I - \frac{\pi}{2}) = \frac{|I|}{\omega_0 C} \sin(\omega_0 t + \arg I).$$

$$\begin{aligned} W_{\max} &= \frac{1}{2} \max_{t \in (t_0, t_0+T]} (Li^2(t) + Cu_C^2(t)) \\ &= \frac{|I|^2}{2\omega_0^2 C} \max_{t \in (t_0, t_0+T]} \left( \underbrace{\omega_0^2 LC}_{1} \cos^2(\omega_0 t + \arg I) + \sin^2(\omega_0 t + \arg I) \right) = \frac{|I|^2}{2\omega_0^2 C}. \\ Q &= 2\pi \frac{|I|^2}{2\omega_0^2 C} \frac{\omega_0}{\pi |I|^2 R} = \frac{1}{\omega_0 RC}. \end{aligned}$$



## SRC — $Q$ factor cont.

$$Q = 2\pi \frac{W_{\max}}{w(0, T)}, \quad T = \frac{2\pi}{\omega_0}, \quad Q = \frac{1}{\omega_0 RC}.$$

Since  $\omega_0^2 LC = 1$ , we have also

$$Q \stackrel{\omega_0 C = 1/\omega_0 L}{=} \frac{\omega_0 L}{R}$$

and



$$Q \stackrel{\omega_0 = 1/\sqrt{LC}}{=} \boxed{\frac{\sqrt{\frac{L}{C}}}{R}}.$$

The quantity

$$\boxed{\rho = \sqrt{\frac{L}{C}}}$$

is called **characteristic resistance** of SRC.

# Absolute detuning

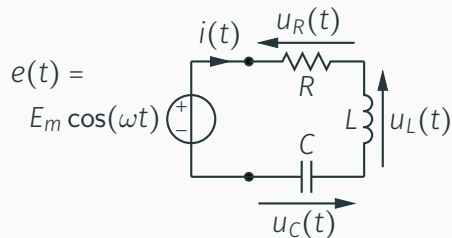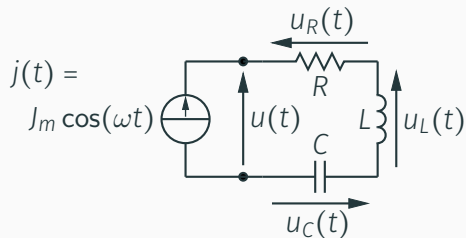


## Definition

For SRC, the **absolute detuning** related to pulsation  $\omega$  is defined as



$$\xi_\omega = (\omega L - \frac{1}{\omega C})/R.$$

## Absolute detuning cont.

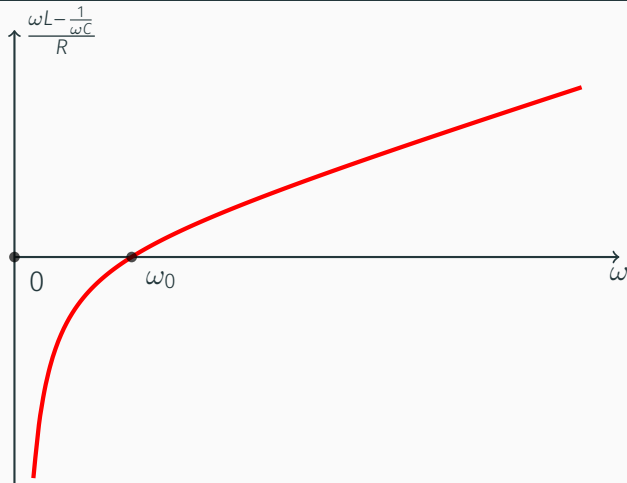

$$Z(\omega) = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + jR\xi_\omega = R(1 + j\xi_\omega).$$

## SRC — filtration

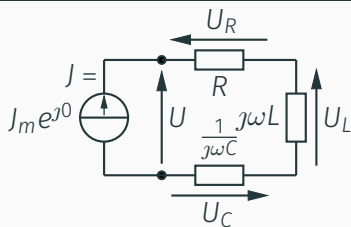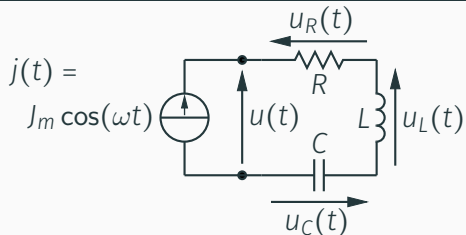

$$U = JZ(\omega), \quad U_R = JR, \quad U_L = Jj\omega L, \quad U_C = \frac{J}{j\omega C}, \quad Z(\omega) = R(1 + j\xi_\omega)$$


Thus

$$u_R(t) = J_m R \cos(\omega t), \quad u(t) = J_m R \sqrt{1 + \xi_\omega^2} \cos(\omega t + \arctan \xi_\omega),$$



$$u_L(t) = J_m \omega L \cos(\omega t + \frac{\pi}{2}) = J_m R \frac{\omega L}{R} \cos(\omega t + \frac{\pi}{2}),$$

$$u_C(t) = \frac{J_m}{\omega C} \cos(\omega t - \frac{\pi}{2}) = \frac{J_m R}{\omega R C} \cos(\omega t - \frac{\pi}{2}).$$



## SRC — filtration cont.

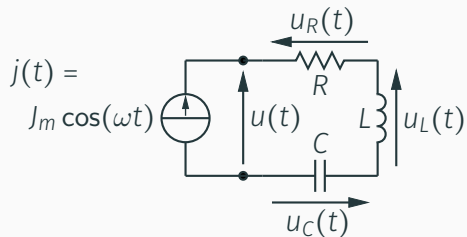
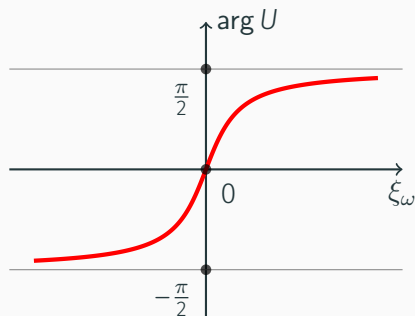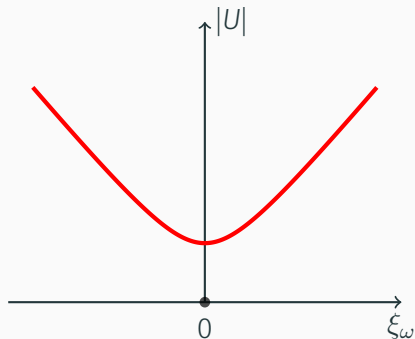
$$u(t) = J_m R \sqrt{1 + \xi_\omega^2} \cos(\omega t + \arctan \xi_\omega).$$



## SRC — filtration cont.

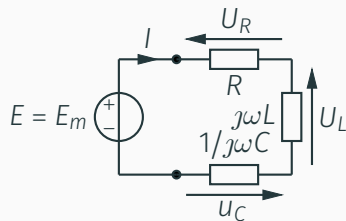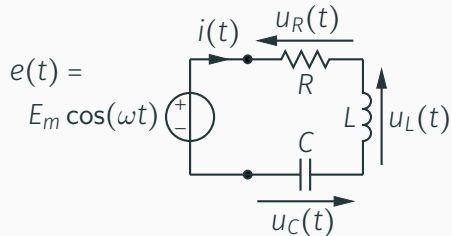


$$I = \frac{E}{Z(\omega)} = \frac{E}{R(1 + j\xi_\omega)} \quad \text{thus} \quad i(t) = \underbrace{E_m / (R\sqrt{1 + \xi_\omega^2})}_{I_m(\omega)} \cos(\omega t - \arctan \xi_\omega)$$

$$u_R(t) = I_m(\omega) R \cos(\omega t - \arctan \xi_\omega),$$

$$u_L(t) = I_m(\omega) \omega L \cos(\omega t + \pi/2 - \arctan \xi_\omega),$$

$$u_C(t) = I_m(\omega) / (\omega C) \cos(\omega t - \pi/2 - \arctan \xi_\omega).$$

## SRC — filtration cont.

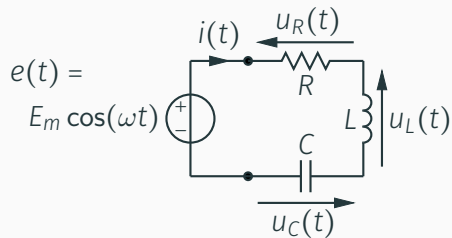


For resonant pulsation  $\omega = \omega_0$  (i.e.  $\xi = 0$ ):  $i(t) = \frac{E_m}{R} \cos(\omega_0 t)$  and

$$u_R(t) = E_m \cos(\omega_0 t),$$



$$u_L(t) = QE_m \cos\left(\omega_0 t + \frac{\pi}{2}\right),$$

$$u_C(t) = QE_m \cos\left(\omega_0 t - \frac{\pi}{2}\right).$$

## SRC — filtration cont.

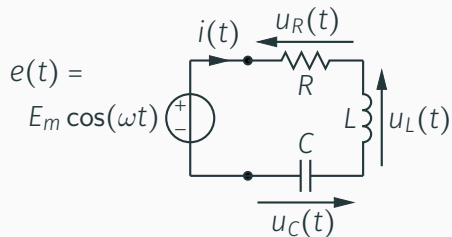
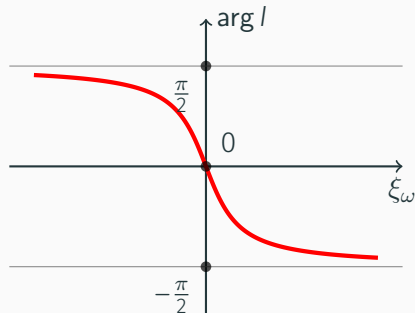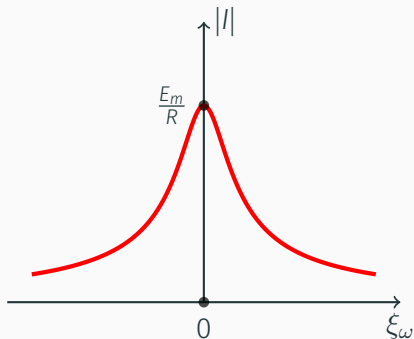
$$i(t) = E_m / (R \sqrt{1 + \xi_\omega^2}) \cos(\omega t - \arctan \xi_\omega)$$





# Relative detuning

## Definition

The **relative detuning** related to pulsation  $\omega$  is defined as

$$\nu_{\omega} = \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}.$$



It occurs that

$$\xi_{\omega} = Q\nu_{\omega}.$$

Indeed



$$Q\nu_{\omega} = Q\frac{\omega}{\omega_0} - Q\frac{\omega_0}{\omega} = \frac{\omega_0 L}{R} \frac{\omega}{\omega_0} - \frac{1}{\omega_0 RC} \frac{\omega_0}{\omega} = (\omega L - \frac{1}{\omega C})/R = \xi_{\omega}.$$

## SRC — filtration cont.

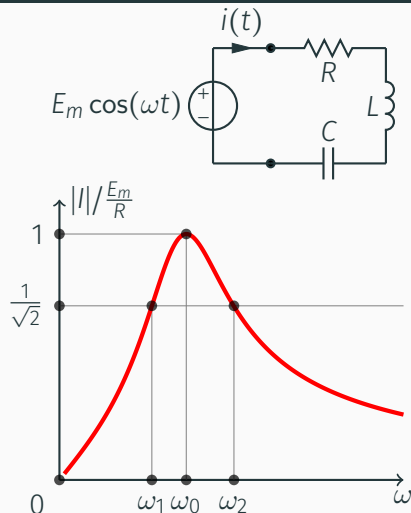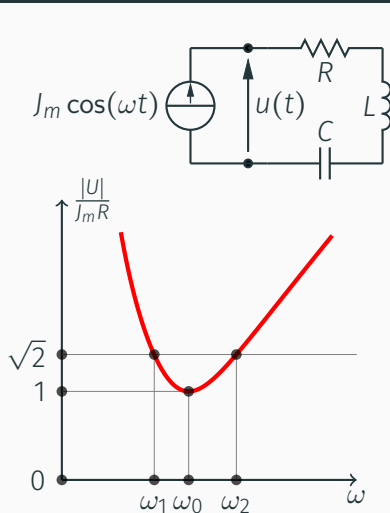

$$|U| = J_m R \sqrt{1 + \xi_\omega^2} \quad |I| = E_m / (R \sqrt{1 + \xi_\omega^2}), \quad \xi_{\omega_1} = -1, \quad \xi_{\omega_2} = 1.$$

## SRC — filtration cont.

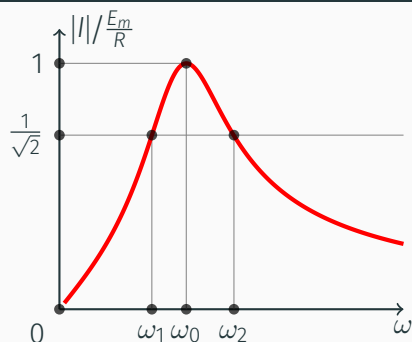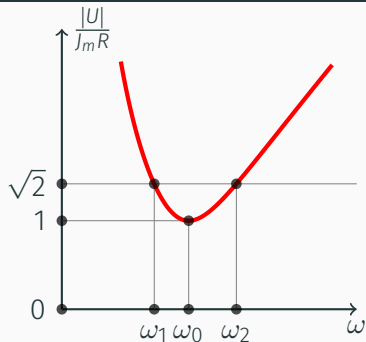

$$\xi_{\omega_1} = -1, \quad \xi_{\omega_2} = 1, \quad \xi = Q\nu.$$

$$\frac{-1}{Q} = \frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_1}$$

$\boxed{+}$



$$\frac{1}{Q} = \frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2}$$

$\boxed{-}$

$$\frac{1}{\omega_0} - \frac{\omega_0}{\omega_1 \omega_2} = 0 \Rightarrow \omega_1 \omega_2 = \omega_0^2$$

$$\frac{2(\omega_2 - \omega_1)}{\omega_0} = \frac{2}{Q} \Rightarrow \omega_2 - \omega_1 = \frac{\omega_0}{Q}.$$

## SRC — filtration cont.

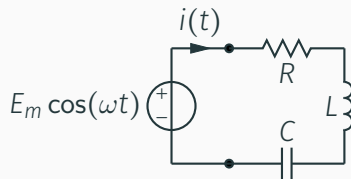
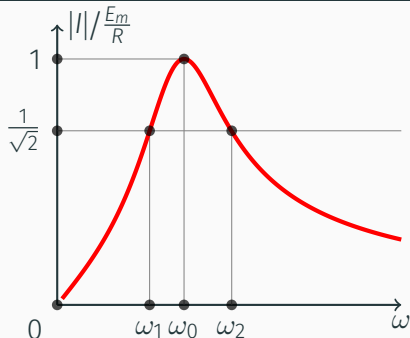


$$\xi_{\omega_1} = -1, \quad \xi_{\omega_2} = 1, \quad \omega_0 = \sqrt{\omega_1 \omega_2}, \quad \omega_2 - \omega_1 = \omega_0 / Q.$$

$$P = \frac{1}{2} |I|^2 R$$

$\omega_1, \omega_2$  are pulsations, for which (real) power transferred to the one port falls to one half of the value attained for  $\omega_0$ .

## SRC — filtration cont.

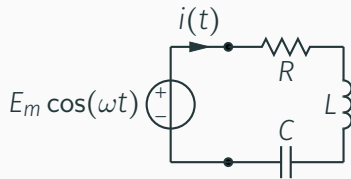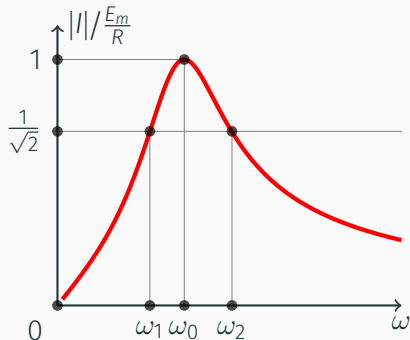

$$\xi_{\omega_1} = -1, \quad \xi_{\omega_2} = 1,$$


$$\omega_2 - \omega_1 = \omega_0/Q.$$

$\omega_1, \omega_2$  are pulsations, for which (real) power transferred to the one port falls to one half of the value attained for  $\omega_0$  i.e. the power changes by 3 dB.

$$\text{power ratio [dB]} = 10 \log_{10} \frac{P}{P_0},$$

$B = B|_{3\text{dB}} = \omega_2 - \omega_1 = \omega_0/Q$  is called the **Bandwidth** of SRC.

## Parallel resonant circuit (PRC)

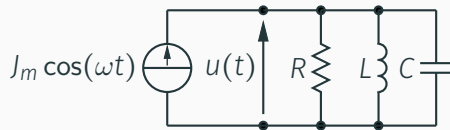

$$Y(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C = \frac{1}{R} \left( 1 + \underbrace{jR\left(\omega C - \frac{1}{\omega L}\right)}_{\xi_\omega} \right).$$

$$Z(\omega) = \frac{R}{1 + j\xi_\omega}.$$

$$\omega_0 = \frac{1}{\sqrt{LC}}.$$

## PRC — $Q$ factor

$$Q = 2\pi \frac{W_{\max}}{w(0, T)}, \quad T = \frac{2\pi}{\omega_0},$$

Analogously to SRC case one can get:

$$Q = \frac{R}{\omega_0 L} = Q = \omega_0 RC = \boxed{\frac{R}{\sqrt{\frac{L}{C}}}}.$$

The quantity

$$\boxed{\rho = \sqrt{\frac{L}{C}}}$$

is called **characteristic resistance** of PRC.

# Detunings

Absolute detuning

$$\xi_{\omega} = R\left(\omega C - \frac{1}{\omega L}\right).$$


Relative detuning

$$\nu_{\omega} = \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}.$$

$$\xi = Q\nu.$$



## PRC — current resonance

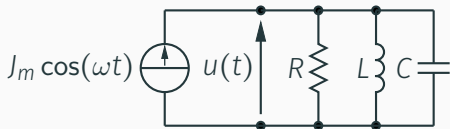

For resonant pulsation  $\omega = \omega_0$  (i.e.  $\xi = 0$ ):

$$u(t) = J_m R \cos(\omega_0 t)$$



and

$$i_R(t) = J_m \cos(\omega_0 t),$$

$$i_L(t) = Q J_m \cos(\omega_0 t - \frac{\pi}{2}),$$

$$i_C(t) = Q J_m \cos(\omega_0 t + \frac{\pi}{2}).$$

## PRC — filtration

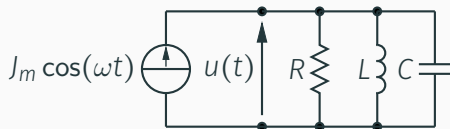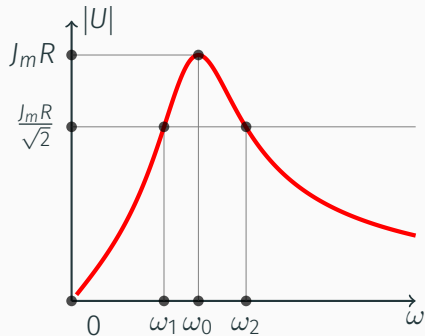

$$\xi_{\omega_1} = -1, \quad \xi_{\omega_2} = 1, \quad \omega_0 = \sqrt{\omega_1 \omega_2}, \quad \omega_2 - \omega_1 = \omega_0 / Q.$$

$\omega_1, \omega_2$  are half-power points ( $P = \frac{1}{2}|I|^2 R$ ), i.e. they form the limits of 3 dB-pass-band

$$B = B|_{3\text{ dB}} = \omega_2 - \omega_1 = \omega_0 / Q.$$

## SRC and PRC — comparison

	SRC	PRC
$\omega_0$	$1/\sqrt{LC}$	$1/\sqrt{LC}$
$\rho$	$\sqrt{L/C}$	$\sqrt{L/C}$
$Q$	$2\pi \frac{W_{\max}}{w(0,T)} = \frac{1}{\omega_0 RC} = \frac{\omega_0 L}{R} = \frac{\rho}{R}$	$2\pi \frac{W_{\max}}{w(0,T)} = \omega_0 RC = \frac{R}{\omega_0 L} = \frac{R}{\rho}$
$\nu_\omega$	$\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}$	$\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}$
$\xi_\omega$	$Q\nu_\omega = (\omega L - \frac{1}{\omega C})/R$	$Q\nu_\omega = R(\omega C - \frac{1}{\omega L})$
$Z(\omega)$	$R(1 + j\xi_\omega)$	$R/(1 + j\xi_\omega)$
$Z(\omega_0)$	$R$	$R$
$B$	$\omega_2 - \omega_1 = \omega_0/Q$	$\omega_2 - \omega_1 = \omega_0/Q$
$\omega_0$	$\sqrt{\omega_1 \omega_2}$	$\sqrt{\omega_1 \omega_2}$