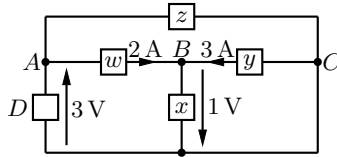



Problem Set 5

Problem 1. The one-port D absorbs the power of 6 W. Solve the circuit for the currents, the voltages and the powers.




Answer. $U_{AB} = 4 \text{ V}$, $U_{CB} = 1 \text{ V}$, $U_{AC} = 3 \text{ V}$; currents through one-ports: 5 A through x downward, 2 A through D downward, 4 A through z to the left; powers delivered: 6 W to D , 8 W to w , -5 W to x , 3 W to y , -12 W to z .

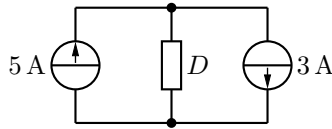Problem 2. The source of 5 A current generates the power of 10 W. Find the values of the power absorbed by the other source and by the one-port D .




Answer. 4 W by D , 6 W by the current source.

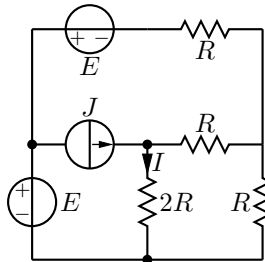Problem 3. Using superposition rule, find the value of the current I . Determine the power for the resistor $2R$.



Answer. $I = \frac{3}{7}J - \frac{E}{7R} + \frac{E}{7R} = \frac{3}{7}J$, $P = \frac{18}{49}J^2R$.

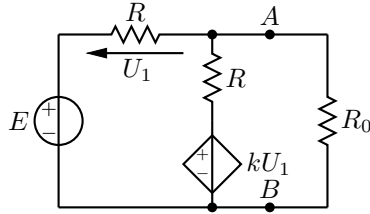
Problem 4. Find the Thévenin equivalent source of the subcircuit to the left of the terminals A, B . Compute the power for R_0 . For what value of R_0 the power for R_0 is maximal.



Answer. $B \xrightarrow{E_T} R_T \xrightarrow{A}$, $E_T = E(k+1)/(k+2)$, $R_T = R/(k+2)$,
 $P_{R_0} = (E_T/(R_T + R_0))^2 R_0$, max. power fo $R_0 = R_T$.

Problem 5. For what R_0 the energy stored in inductor L equals the energy stored in non-linear inductor L_N ?


$E = 1\text{ V}$, $J = 2\text{ mA}$, $R = 1\text{ k}\Omega$, L_N : $\psi = ai|i|$, $a = 1\text{ Wb/A}^2$, $L = \frac{4}{3}\text{ mH}$.

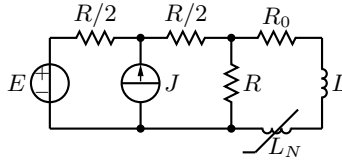

Answer. $R_0 = \frac{1}{2}\text{ k}\Omega$.

Problem 6. Find the energy stored in the inductor and the capacitor provided that resistor R_0 is matched for maximum power transfer.

$R = 1\text{ k}\Omega$, $E = 8\text{ V}$, $L = 2\text{ H}$, C_N : $q = C_0 u + \beta u|u|$, $C_0 = 1\text{ }\mu\text{F}$, $\beta = 3\text{ }\mu\text{F/V}$.

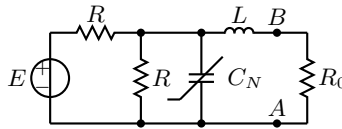

Answer. $w_L = 16\text{ }\mu\text{J}$, $w_C = 18\text{ }\mu\text{J}$.